


DC to AC Converter: Inverter



Dr. D. S. More
Department of Electrical engg
W. C. E. Sangli
E-mail => dsm.wce@gmail.com

Introduction


- DC to AC conversion

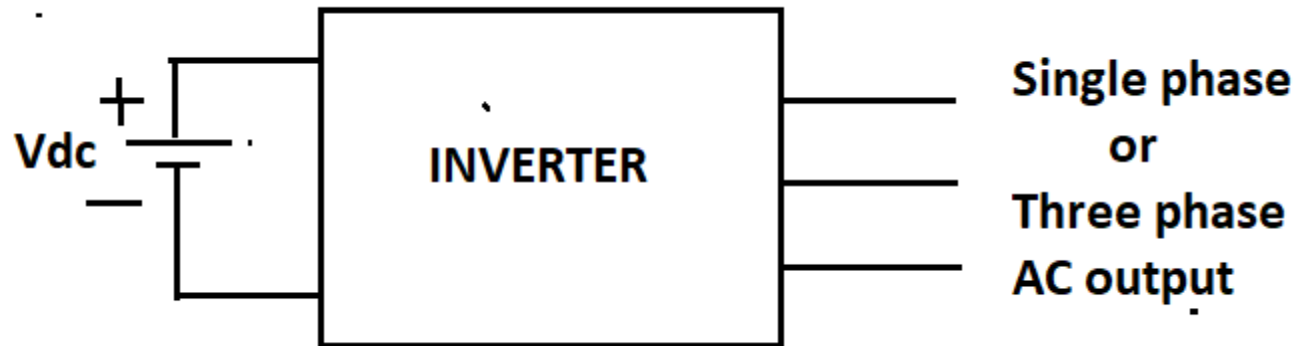

- Variable voltage variable frequency output
- Devices used are MOSFET or IGBT
- Applications : UPS, AC Drives & VSC used in power systems



Types of DC Sources

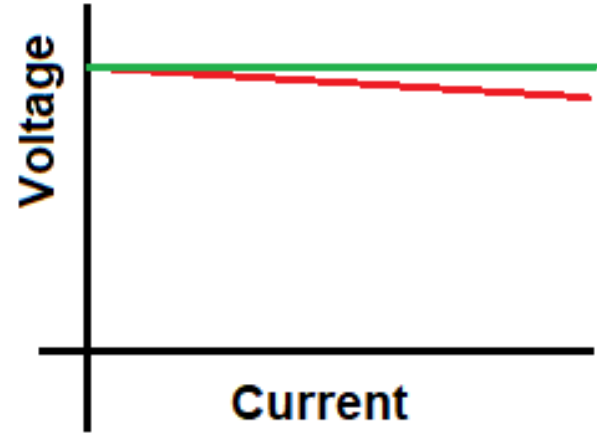- DC Voltage source
- V-I Characteristics
- Examples
 - Battery
 - Uncontrolled AC to DC converter
 - Controlled AC to DC converter
 - O/P voltage of DC shunt generators




DC Current Source

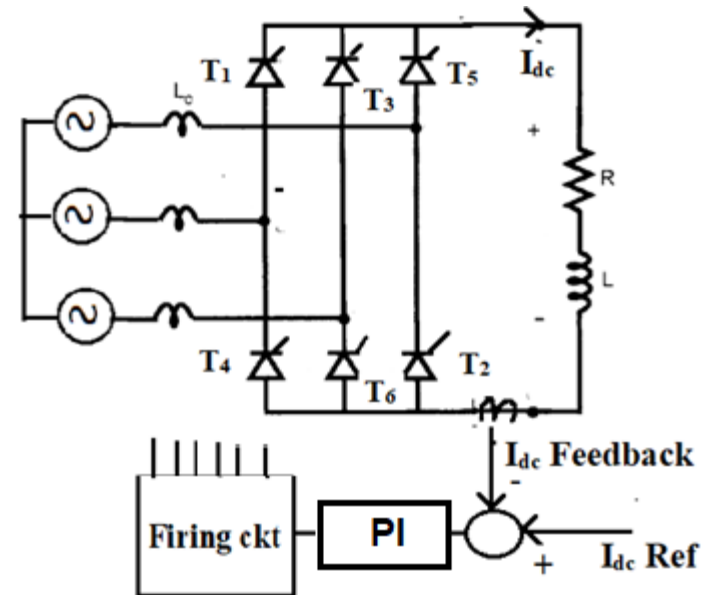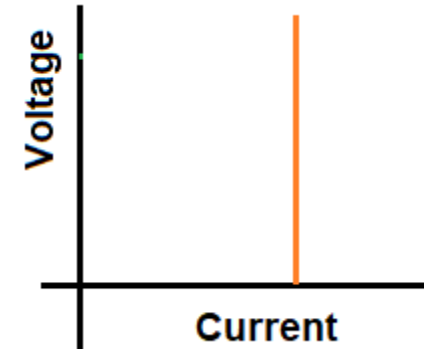- DC current source is obtained from AC to DC converter with closed loop current control
- I_{dc} is always maintained to a set value by adjusting α of the 6 pulse converter
- Voltage of the converter changes as per change in load to maintain I_{dc} constant



Types of Inverter based on DC Source

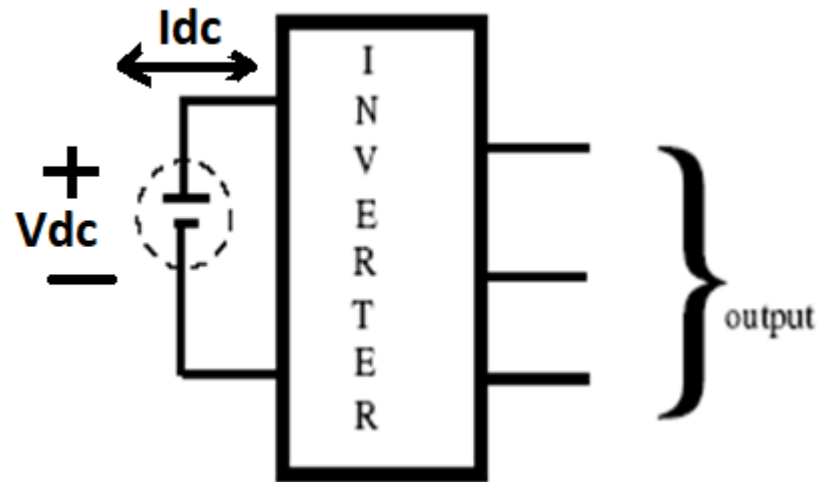
- Voltage source Inverter (VSI)
- Input to inverter is DC voltage source.
- Battery or Large C at input dc side.
- Input DC current can rev
- DC voltage polarity cant be reversed.
- Power flow can be bi-directional.



Types of Inverter based on DC Source

- **Current source Inverter (CSI)**
- Input to inverter is DC current source.
- Input DC current can't be reversed.
- DC voltage polarity can be reversed.
- Power flow can be bi-directional.

How to obtain dc current source?


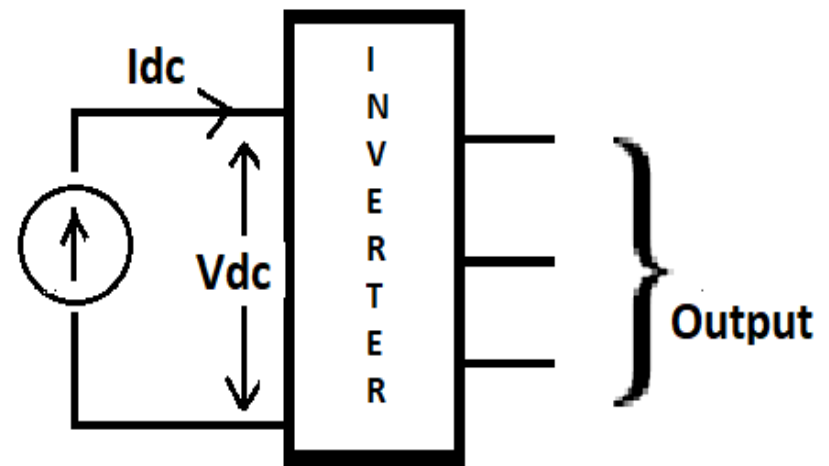


Types of Inverter based on topology

- Voltage source Inverter (VSI)
- Single phase
 - i) Half Bridge
 - ii) Full bridge
- Three phase Bridge Inverter
- 120° mode
- 180° mode
- PWM switching

1 ϕ half bridge Inverter

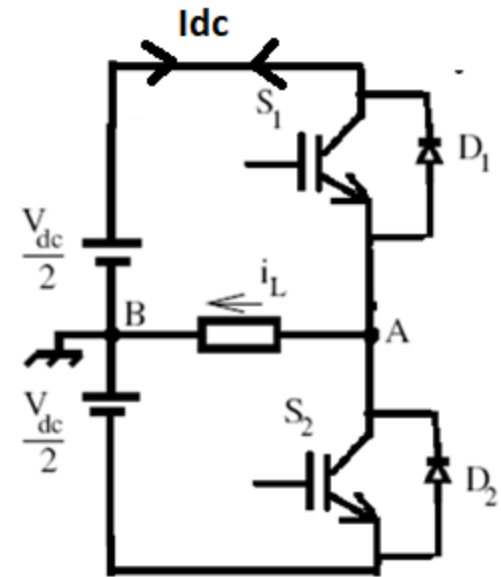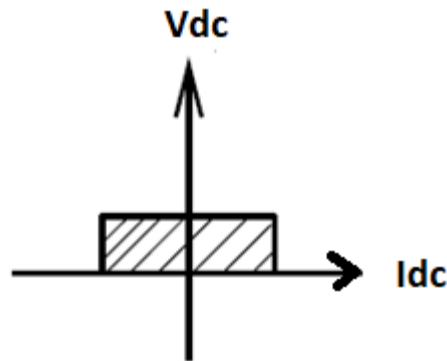- Circuit configuration
- Basic configuration : half bridge
- Switches can carry bidirectional current
- Diode antiparallel with switch
- Two quadrant operation




1 ϕ half bridge Inverter

- Output voltage waveform
- Switching signals S1 and S2
- Are complementary



■ When S1 is ON

■ $V_{AB} = +V_{DC}/2$

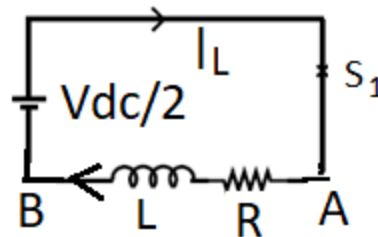

■ When S2 is ON

■ $V_{AB} = -V_{DC}/2$

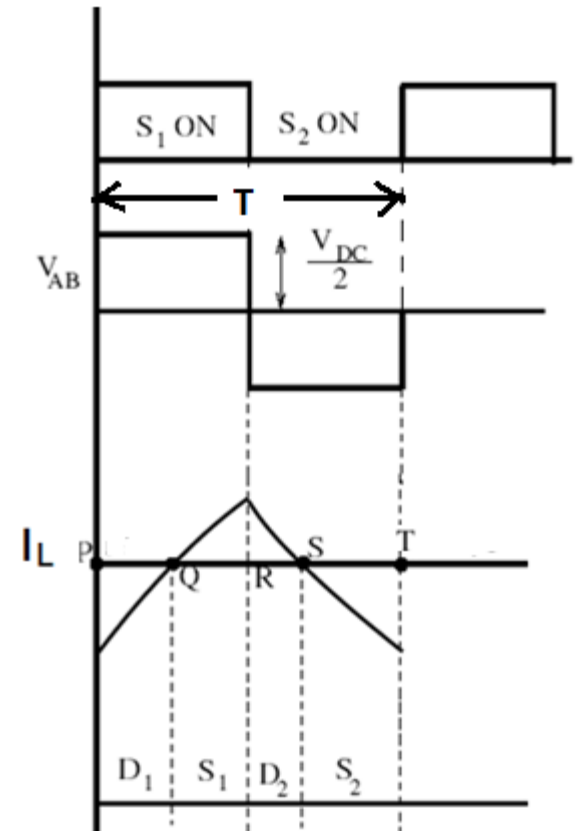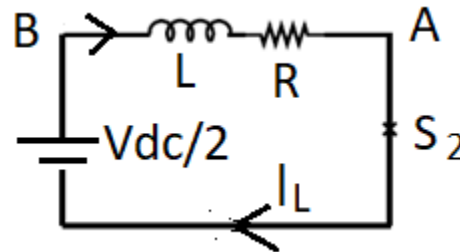

1 ϕ half bridge Inverter


- Observations
- Time for S_1 / S_2 on will determine the output frequency
- If $T/2 = 10$ msec then $F = 50$ Hz
- Similarly $T/2 = 100$ msec then $F = 5$ Hz
- Steady state operation
- PQ Period \Rightarrow applied voltage to load = +ve
 I_L is negative (flowing from B to A)
 D_1 carrying current

1 ϕ half bridge Inverter

- Period Q R \Rightarrow V and I are +ve
S1 is conducting
- Period R S \Rightarrow V is – ve and I is +ve
D2 is conducting
- Period S T \Rightarrow V and I are -ve
S2 is conducting
- If load is RL then switch should have anti-parallel diode

1 ϕ half bridge Inverter

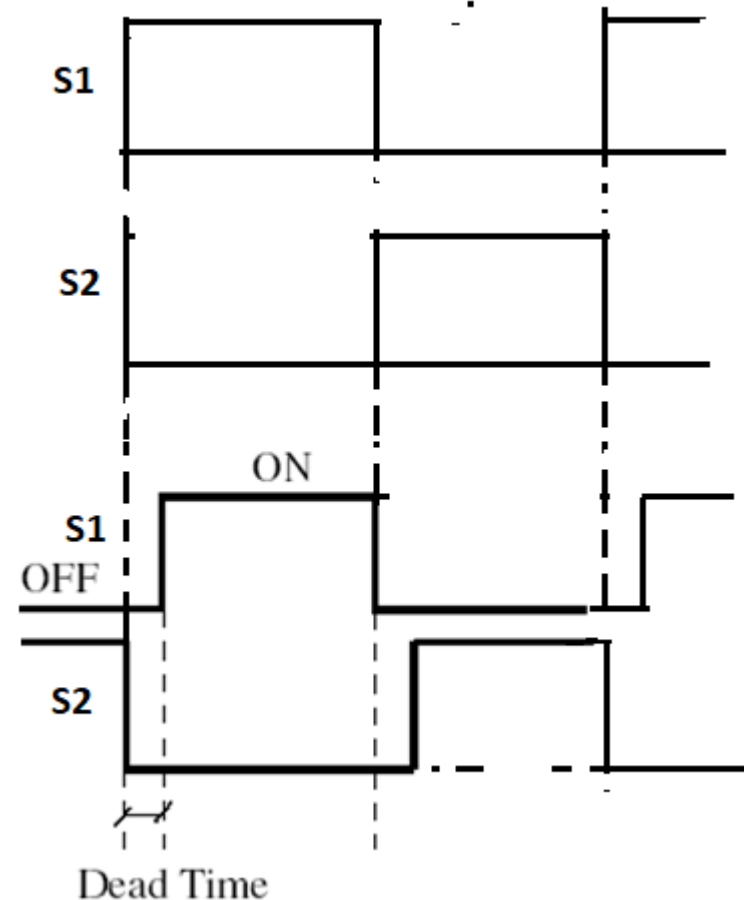- **Dead Time**
- S1 and S2 should not on simultaneously
- DC source short Circuited
- Avoid short circuit by using dead time
- Switch on instant is delayed by few μsec




Harmonics

- The relationship between rms current, fundamental current and harmonic current
- $I_{rms}^2 = I_{1rms}^2 + I_{2rms}^2 + I_{3rms}^2 + I_{4rms}^2 + I_{5rms}^2 + \dots$
- $I_{rms}^2 = I_{1rms}^2 + I_{hrms}^2$
- Where,
- Total harmonic current can be
- $I_{hrms}^2 = I_{2rms}^2 + I_{3rms}^2 + I_{4rms}^2 + I_{5rms}^2 + \dots$
- For the given waveform I_{rms}^2 and I_{1rms}^2 is computed
- $\%THD = (I_{hrms} / I_{1rms}) \times 100$

Harmonic spectrum of a waveform

■ Procedure

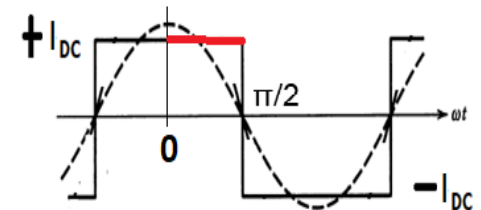- Determine the RMS value of the waveform. = I
- Determine the peak amplitude of nth harmonic
- Considering quarter wave symmetry
- $A_n = \frac{8}{2\pi} \int_0^{\pi/2} F(\theta) \cos(n\theta) d\theta$
- Where A_n = peak amplitude of nth Harmonic.
- Determine peak amplitude of fundamental and the RMS value of fundamental = I_1
- $I^2 = I_1^2 + I_h^2$
- $\%THD = (I_h/I_1) \times 100$



Harmonic spectrum of square wave

- Harmonic spectrum

- RMS value $I = I_{dc}$


- $A_n = \frac{8}{2\pi} \int_0^{\pi/2} I_{dc} \cos(n\theta) d\theta$

- $A_n = (4/n\pi) I_{dc} \sin(n\pi/2)$

- $A_1 = 4I_{dc}/\pi$ (Peak amplitude of fundamental)



- $I_1 = \frac{2\sqrt{2}}{\pi} I_{dc}$ and $I_h = I_{dc} \sqrt{1 - \frac{8}{\pi^2}}$

- $I_h/I_1 = 0.482$

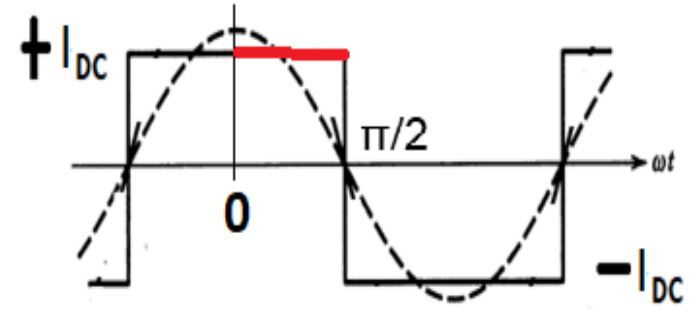

1 ϕ half bridge Inverter

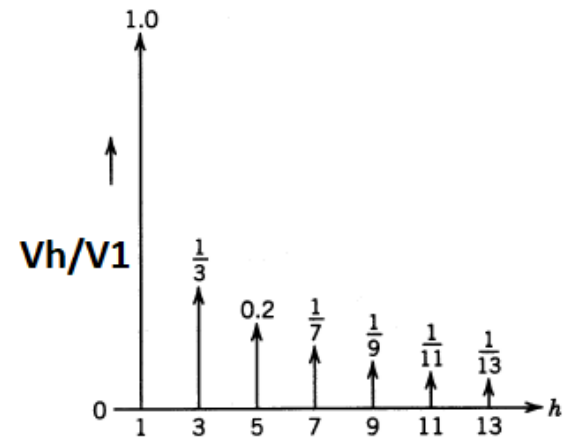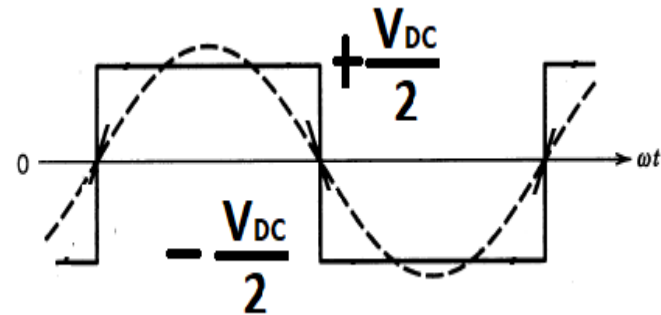- Output voltage and harmonic spectrum
- Output voltage is square wave ($V_{DC}/2$ amplitude)
- It contains all
- odd harmonics
- $V_1 \text{ peak} = 2V_{dc}/\pi$
- THD is 48 %
- $V_{rms} = V_{DC}/2$





1 ϕ half bridge Inverter

- Disadvantages
- Input voltage = V_{dc}
- Output voltage $V_{(rms)} = V_{dc}/2$
- One switch is conducting at a time
- Use full bridge inverter


1 ϕ full bridge Inverter

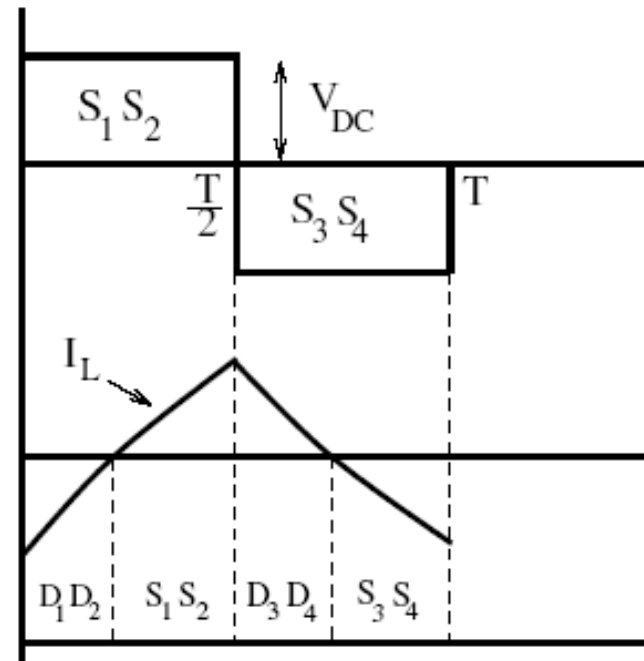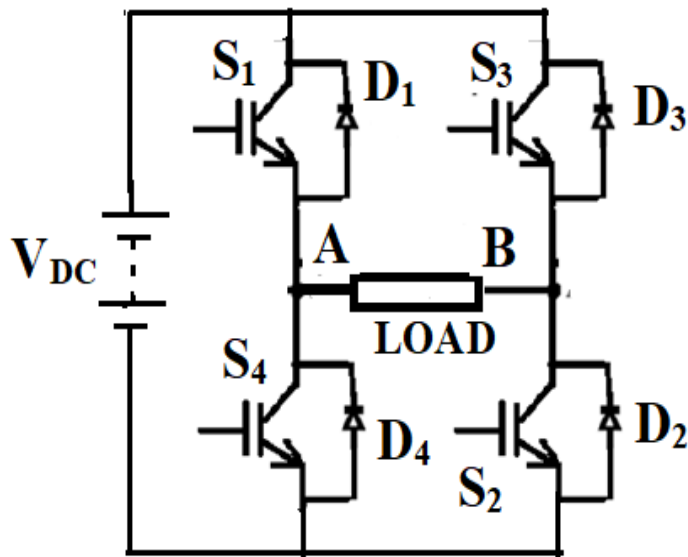- Square wave Mode
- Two devices are conducting simultaneously
- Center point of DC link is not required





1 ϕ full bridge Inverter

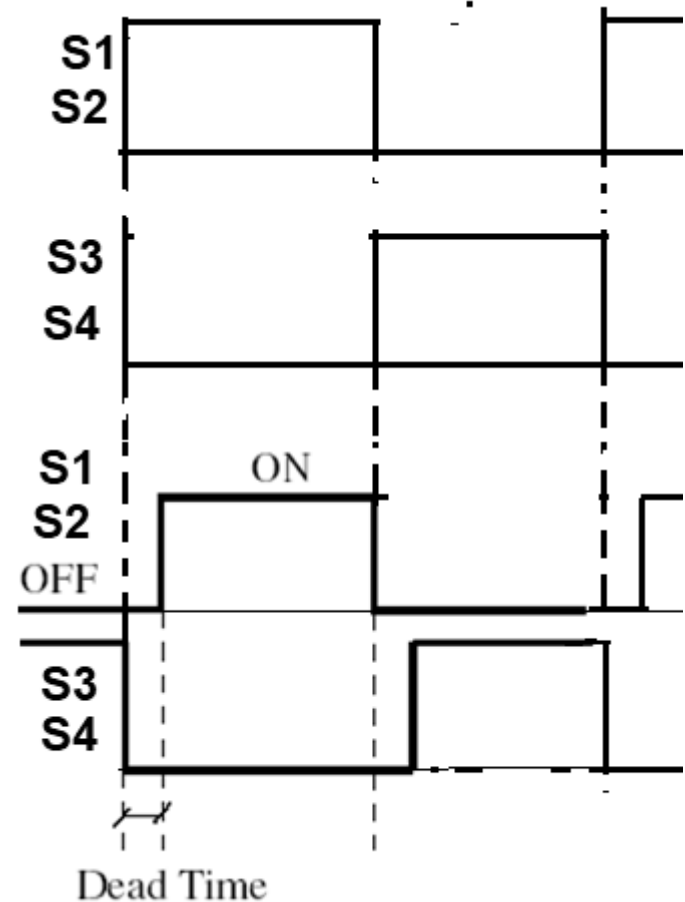- **Dead Time**
- (S1 and S4) OR (S2 & S3) should not on simultaneously
- DC source short Circuited
- Avoid short circuit by using dead time
- Switch on instant is delayed by few μsec




1 ϕ full bridge Inverter

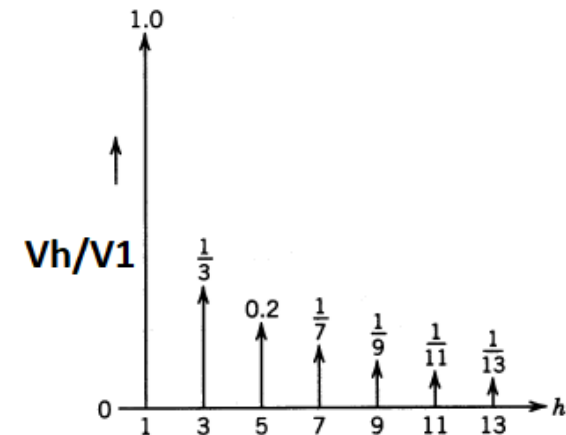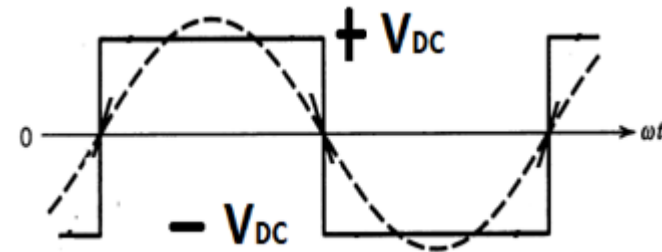- Output voltage and harmonic spectrum
- Output voltage is square wave (V_{DC} Amplitude)
- It contains all
- odd harmonics
- V_1 peak = $4V_{dc}/\pi$
- THD is 48 %
- AC o/p voltage(rms) = V_{DC}




Three Phase VSI Bridge Inverter

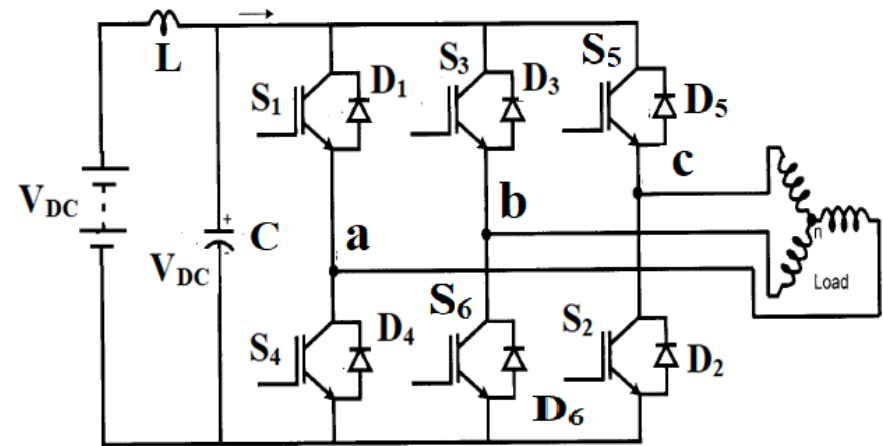- It consists of 3 legs
- Devices are named as per conducting sequence
- Controlled quantities
Voltage, frequency
and phase sequence
- Operating modes
 180° , 120° and PWM



180° mode of conduction

■ Switching signal

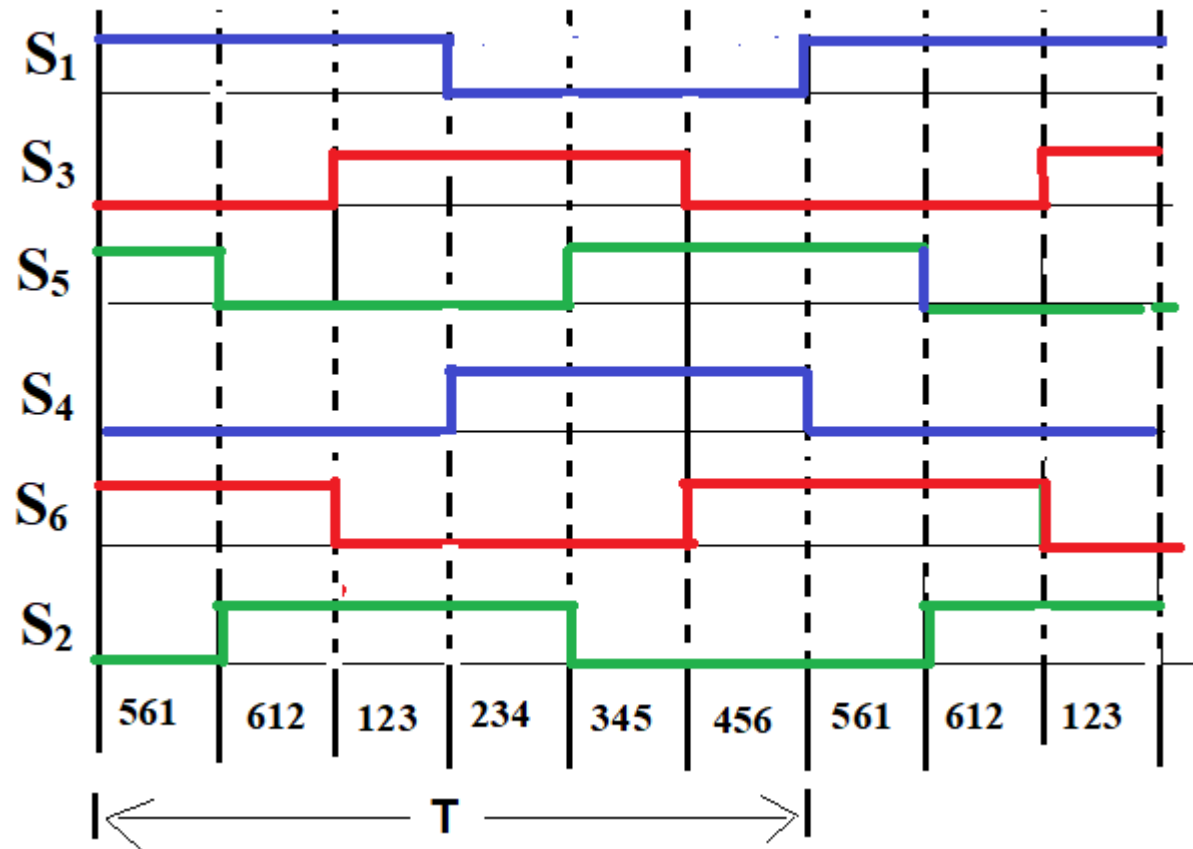

180° mode of conduction

- Each device conducts for 180°
- One device from each leg is ON
- Three devices are on simultaneously
- Devices are named as per conducting sequence
- Dead time is required to avoid the short circuit of DC link
- Phase shift between the legs is 120°.