

Cycloconverter: AC to AC converter



Dr. D. S. More
Department of Electrical engg
W. C. E. Sangli
E-mail => dsm.wce@gmail.com


Classification of AC to DC Converter

- Based on quadrant operation

- Single quadrant




- Two quadrant

- Four quadrant

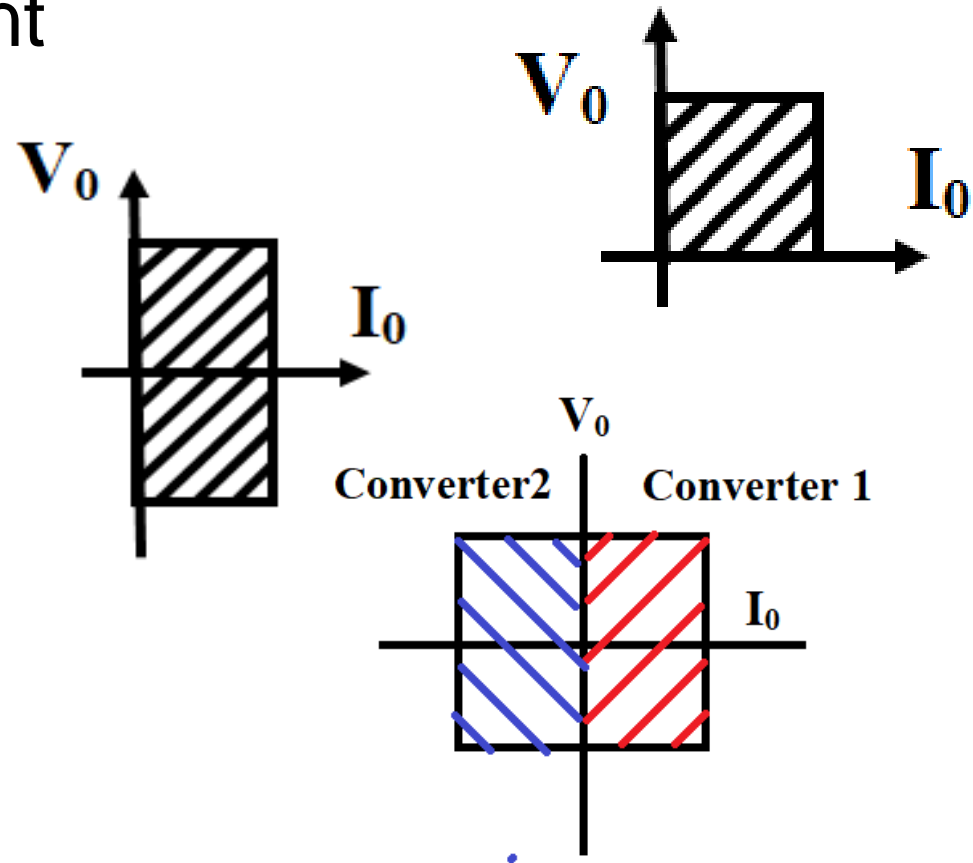

Single phase half controlled converter

■ RL load with continuous conduction

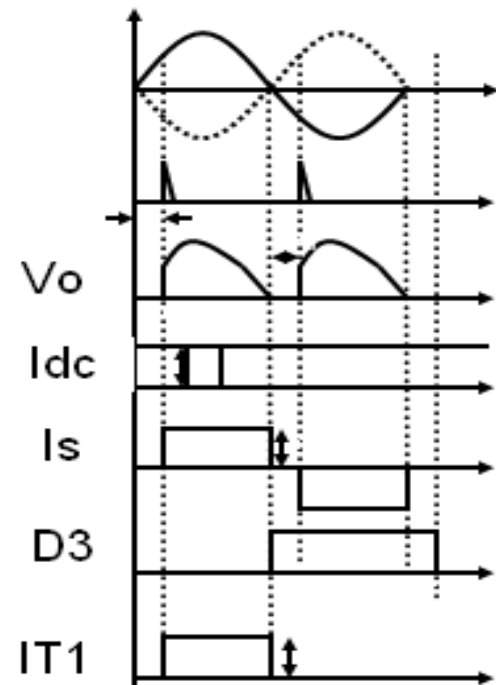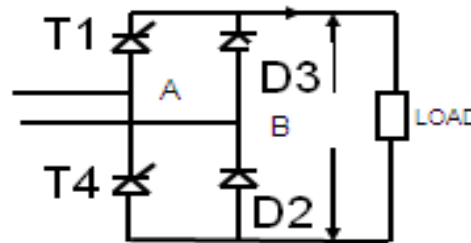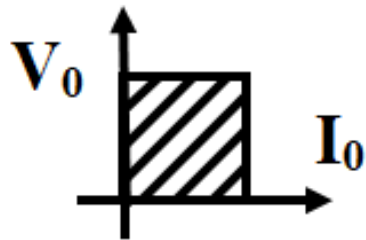



Range of $\alpha = 0$ to 180°

O/P voltage = $V_m/\pi (1+\cos\alpha)$

Conduction period of diodes
> thyristors



Single phase half controlled converter – Symmetrical configuration

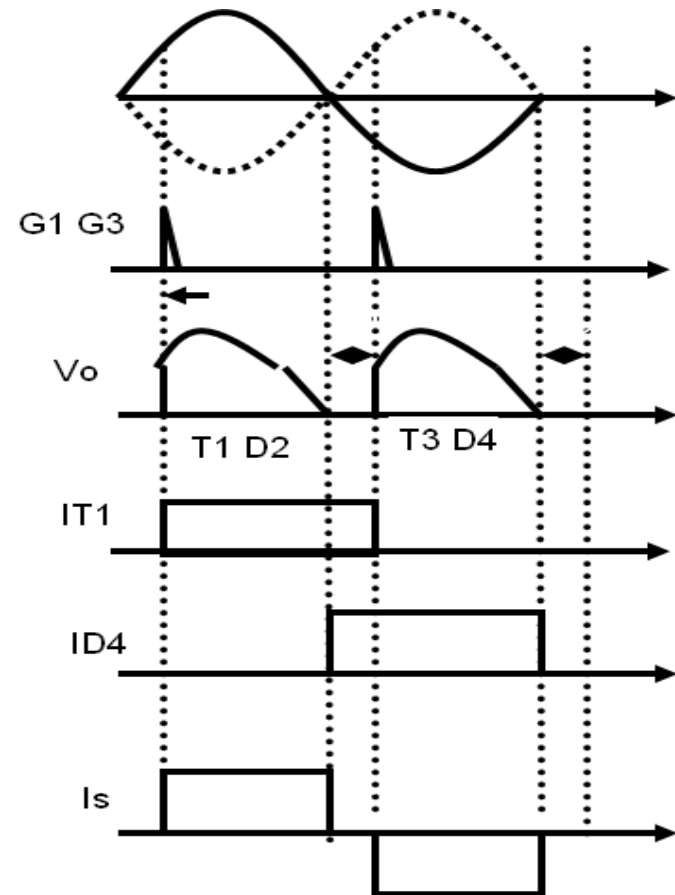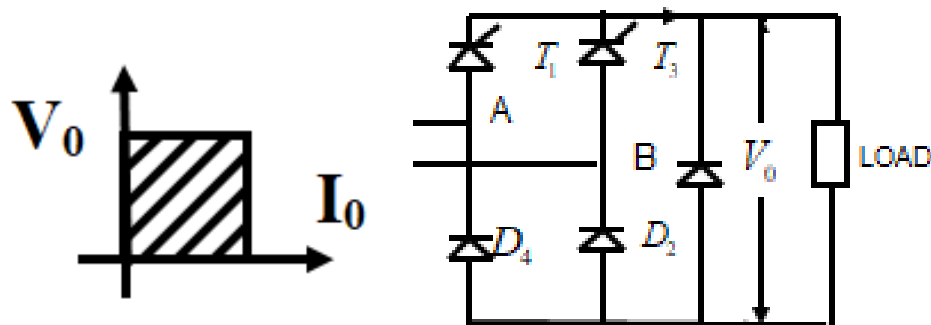Freewheeling diode across the load to avoid the half waving effect



Single phase full controlled converter


Rectifier operation

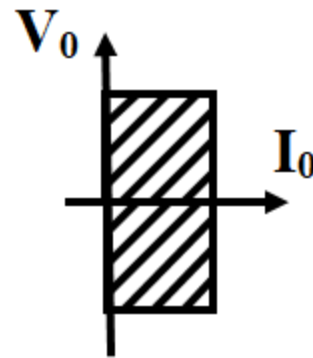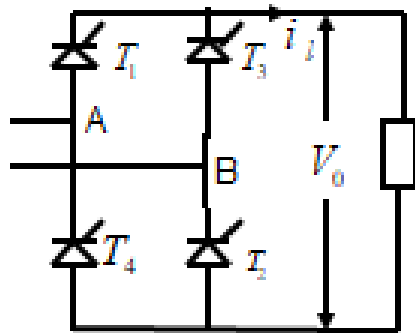


LOAD CURRENT IS CONSTANT & RIPPLE FREE

IN THE +VE HALF T1 ,T2 ARE F.B. & -VE HALF T3 T4 ARE F.B.

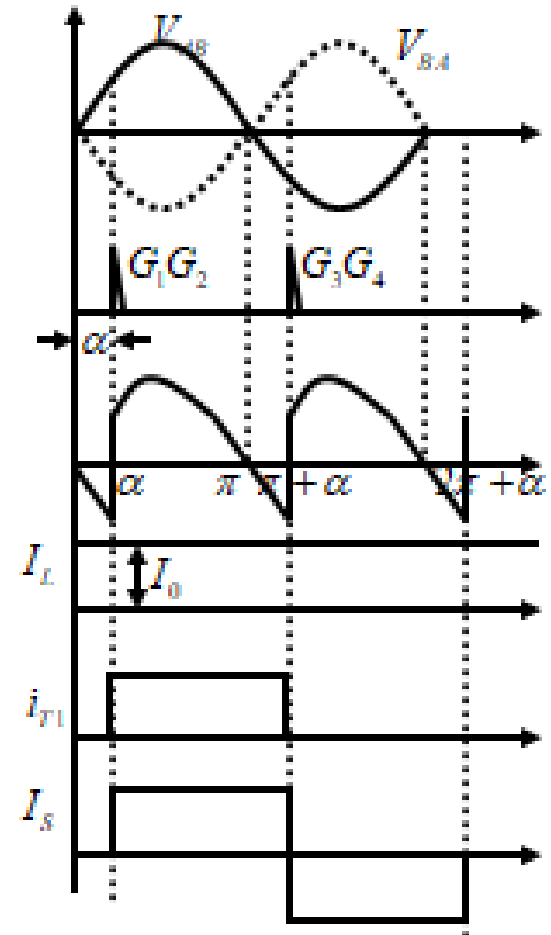**T1 ,T2 CONTINUE TO CONDUCT TILL T3 T4 ARE TRIGGERED
(Load current IS CONTINUOUS)**



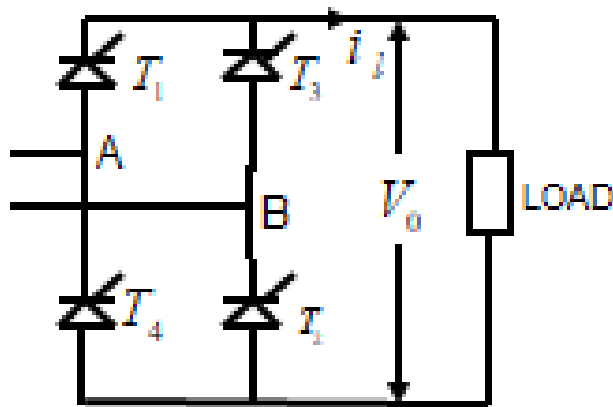Single phase full controlled converter Inverter Operation




Inverter operation- Requirements

Firing angle $> 90^\circ$,
Continuous Conduction



Active source on dc side to maintain DC current
and sufficient L for continuous conduction
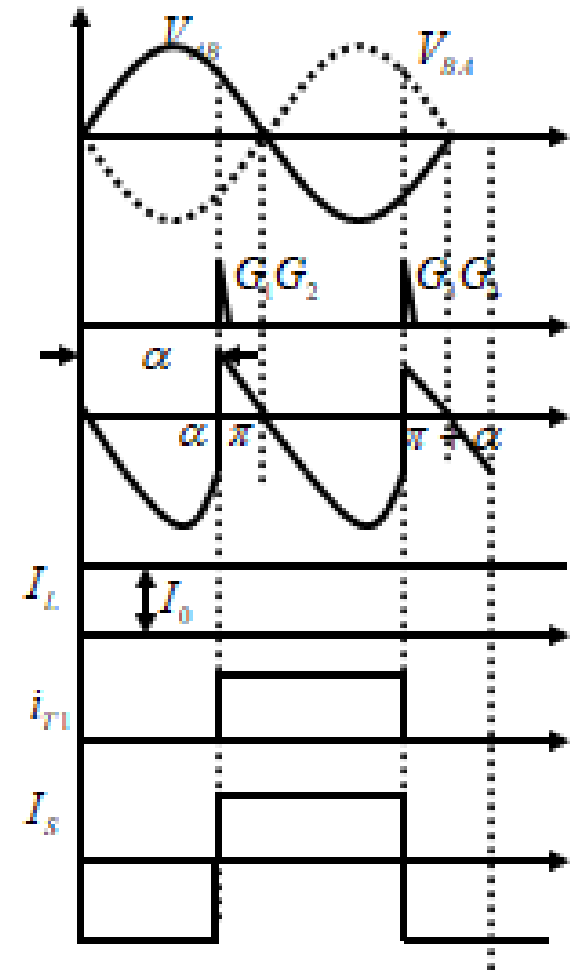
$$\text{O/P voltage} = (2 V_m \cos \alpha) / \pi$$



2 Pulse Dual Converter

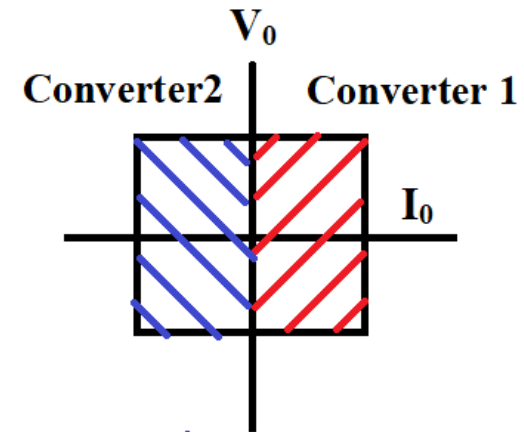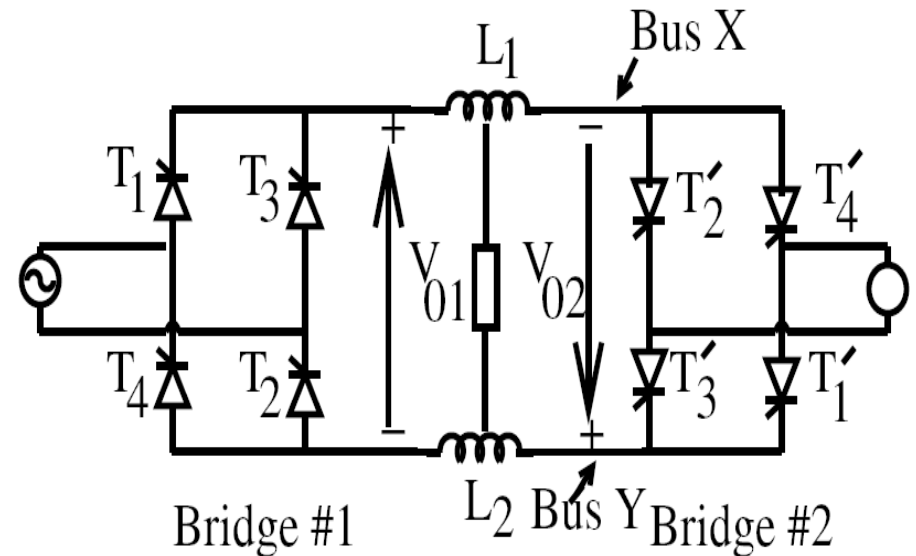- ⇒ In a 2-quadrant converter, 'V' can be reversed, but not 'i'.
- ⇒ use one more bridge.
- ⇒ Dual converter connect them back to back.
- ⇒ 'i' can be reversed and flows back to the source through the 2nd bridge.
- ⇒ All 4 quadrant operation.



2 Pulse Dual Converter

- Two full controlled converters connected antiparallel with load
- Range of α variation $\Rightarrow 0$ to 180°
- $\alpha_1 + \alpha_2 = 180^\circ$
- It consists of positive group and negative group
- One group works in rectifier mode other group works in inverter mode

2 Pulse Dual Converter

■ Four quadrant converter

Assume that both bridges are ON

Let α_1 be the triggering angle for bridge-1

Let α_2 be the triggering angle for bridge-2


$$\therefore V_{01} = \frac{2V_m}{\pi} \cos \alpha_1$$

$$V_{02} = \frac{2V_m}{\pi} \cos \alpha_2$$

KVL gives $V_{01} + V_{02} = 0$



$$[\because (L \frac{di}{dt})_{avg} = 0]$$

$$\therefore \alpha_2 = \pi - \alpha_1$$

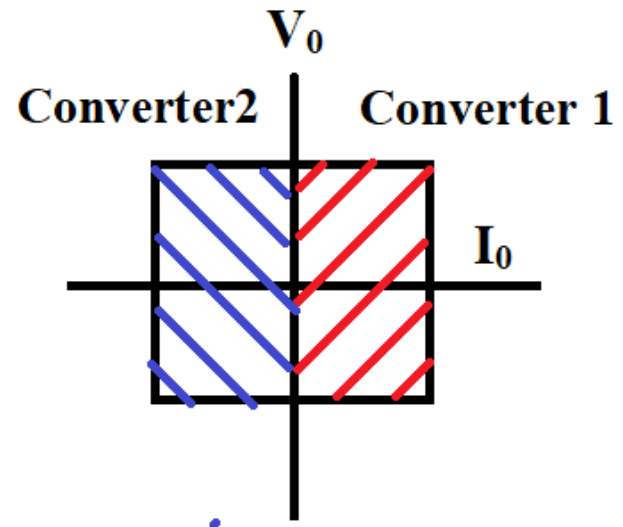

2 Pulse Dual Converter

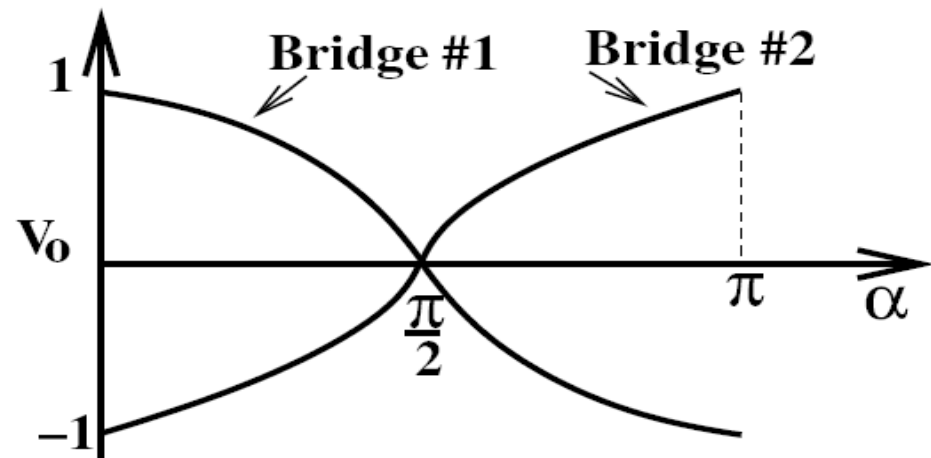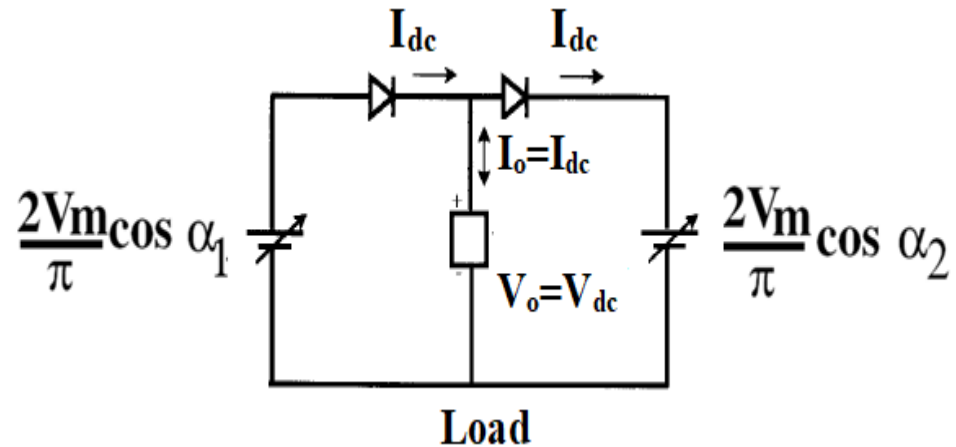- Circulating current mode
- Both converter are ON
- One works in rectifier mode other works in inverter mode




3 Pulse Dual Converter

- Circuit diagram
- Each device conducts for 120°
- Four quadrant operation
- DC O/P voltage


$$V_{dc} = (3 \sqrt{3} V_{mp} \cos \alpha) / 2\pi$$

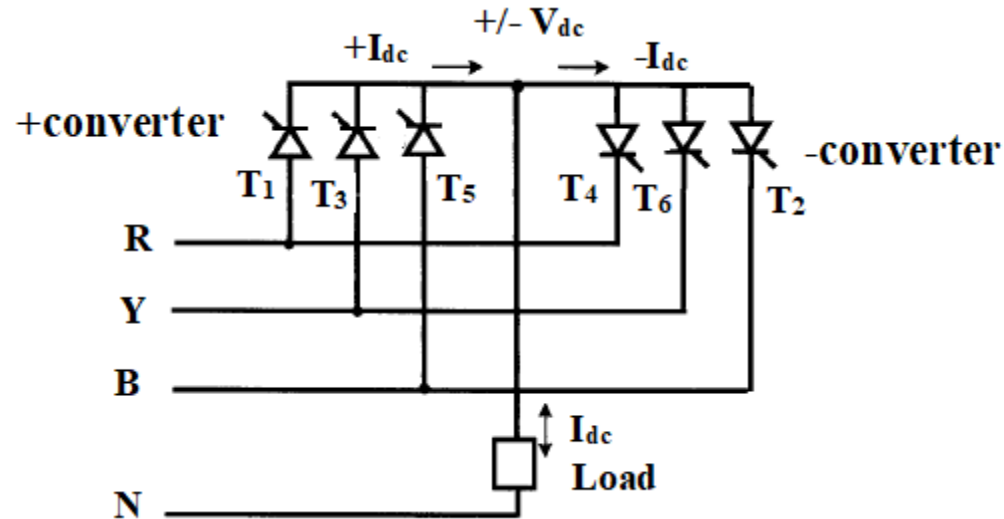where V_{mp} peak value of phase to neutral voltage



6 Pulse Dual Converter

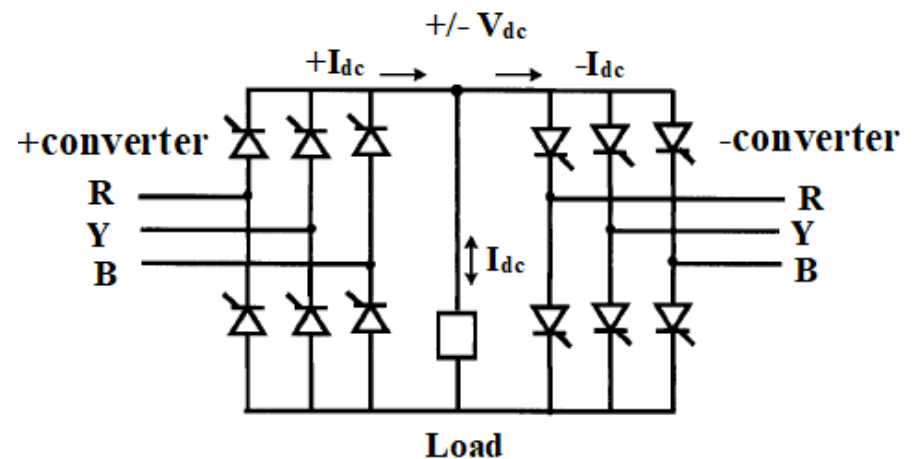- Circuit diagram
- Two full controlled converters connected anti parallel across load
- Four quadrant operation




- O/P DC Voltage

$$V_{dc} = 3 V_{ml} \cos \alpha / \pi$$

where V_{ml} is peak value of line voltage


Cycloconverter

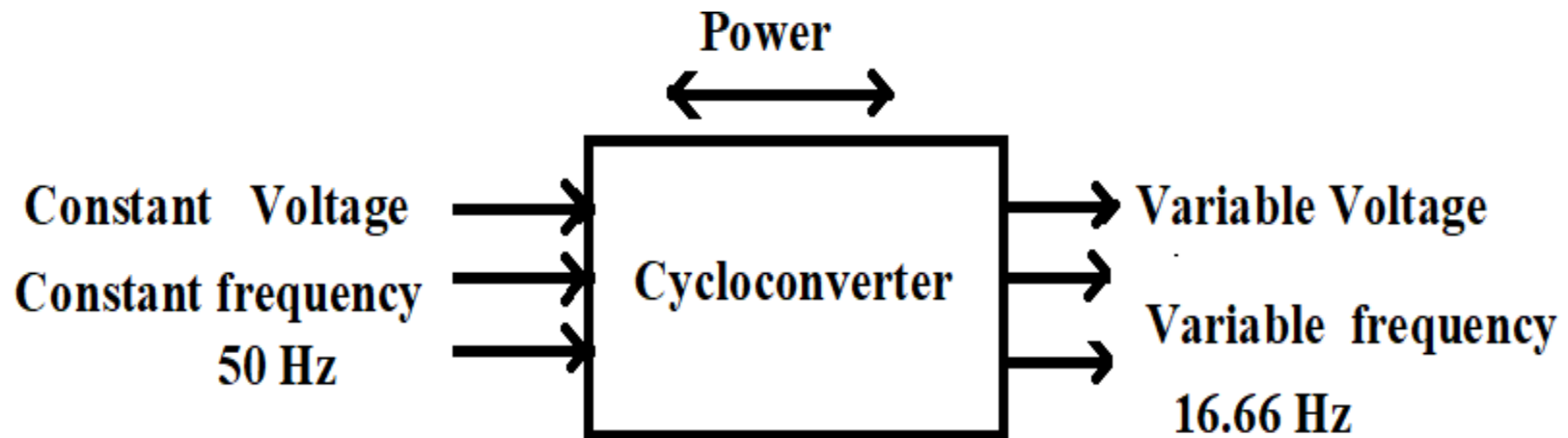- **Block diagram**
- Direct AC to AC conversion
- Power flow is bidirectional
- O/P frequency is lower than i/p frequency




Cycloconverter

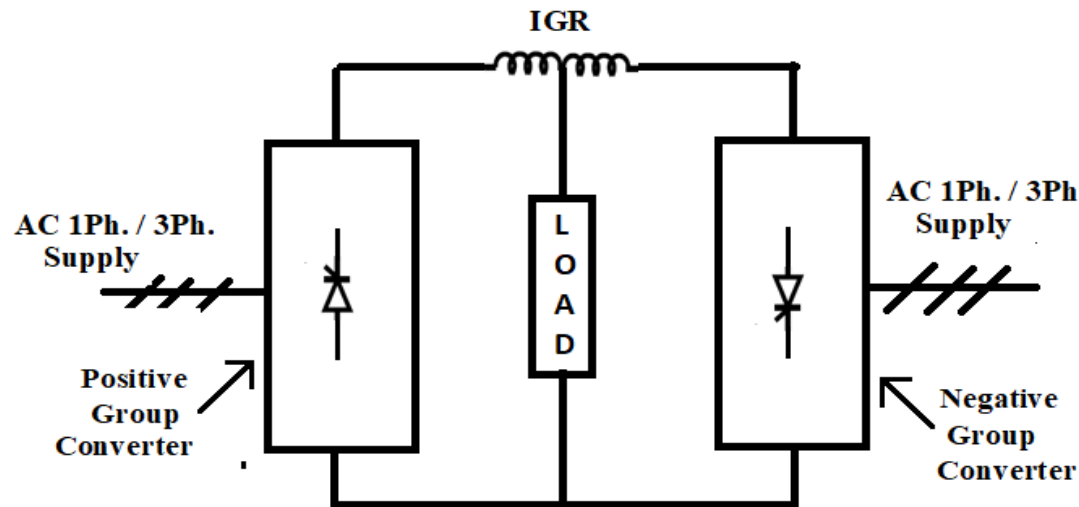- Similarity between dual converter and 1 ϕ Cycloconverter
- Power circuit diagram is same as dual converter but control is different
- It consists of +ve group and –ve groups connected anti parallel with load




Control of Cycloconverter

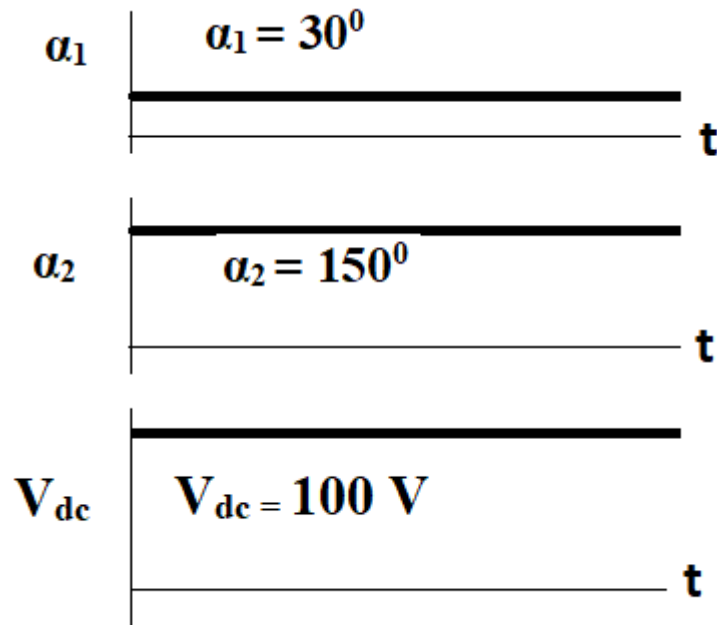- Variation of α_1 and α_2
- $\alpha_1 + \alpha_2 = \pi$
- Dual converter



Cycloconverter

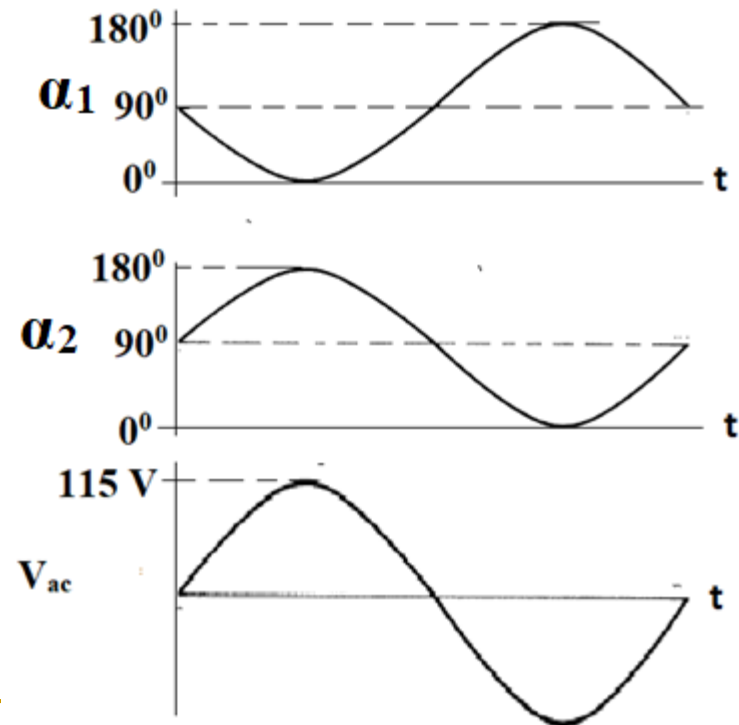


Control of Cycloconverter

- Dual Converter
- For a particular dc o/p voltage α_1 and α_2 remains constant. (not changing with time)
- For example, for 100 DC , $\alpha_1 = 30^\circ$ and $\alpha_2 = 150^\circ$ remains constant. (not changing with time)
- Cycloconverter
- For a particular AC o/p voltage α_1 and α_2 are continuously changing with time.
- For obtaining 1 cycle of AC O/P , α_1 variation
- 90-0-90-180-90

O/P Voltage Control

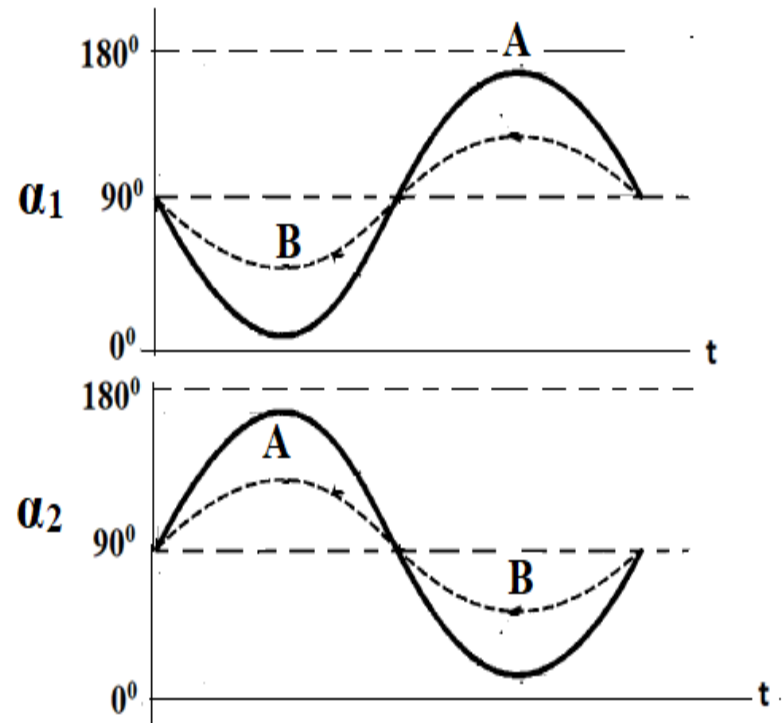- Two cases of α variation
A & B are shown.
- Case A variation
90-10-90-170-90
- Case B variation
90-60-90-120-90
- Case A variation provides more AC O/P than B case



- Range of variation of α around 90° decides the magnitude of O/P voltage O/P frequency is same


O/P Frequency Control

- For both cases α_{\min} and α_{\max} are the same

hence O/P voltage is same(equal)


- Where as T period of cyclic variation of α determines the O/P frequency

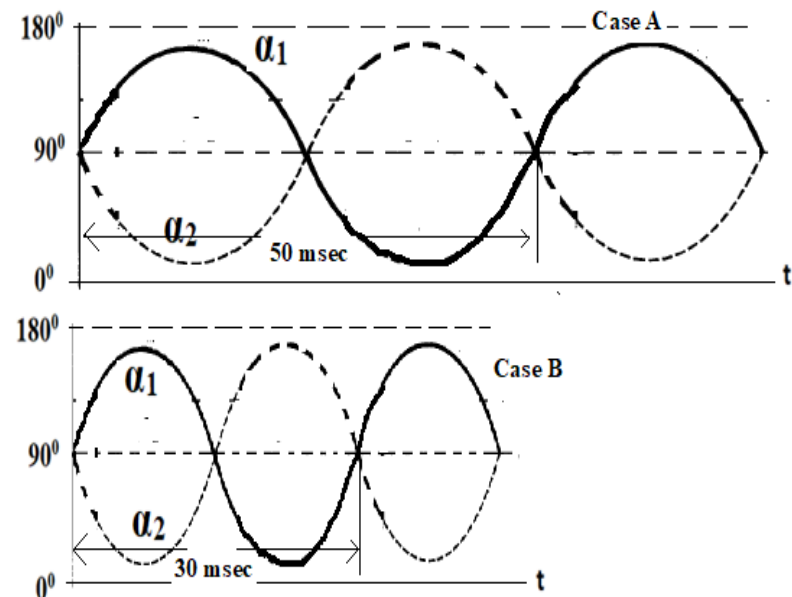- For case A O/P frequency is 20 Hz where as for case B O/P frequency is 33.33 Hz




Cycloconverter- Operation

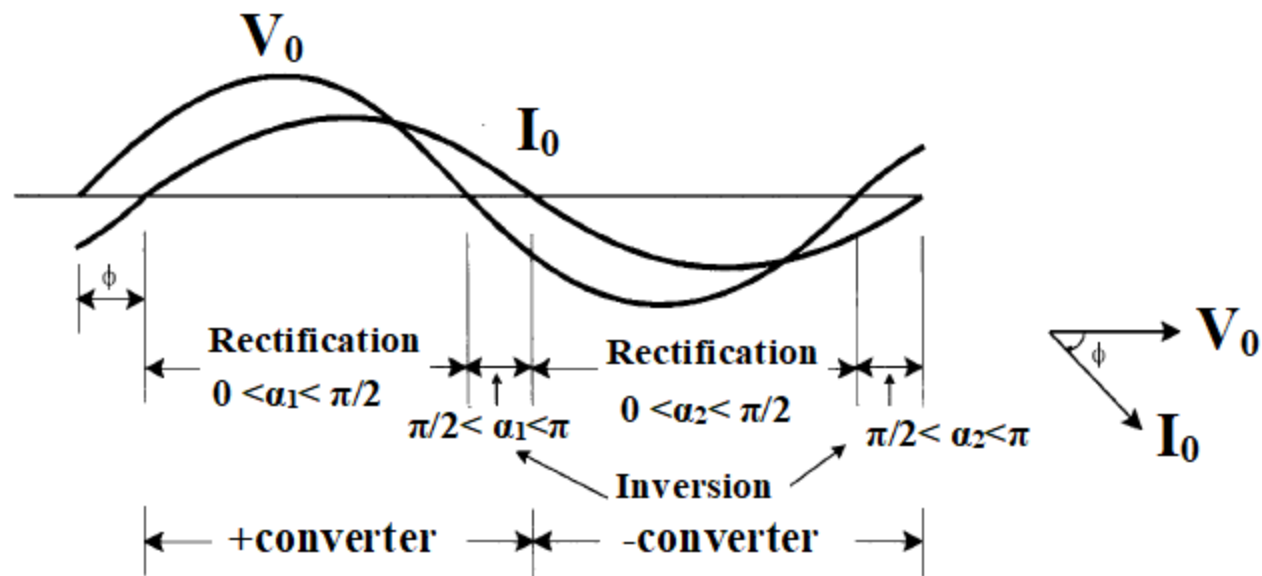- + ve converter provides +ve current to the load
- -Ve converter provides -ve current to the load
- Depending upon V_0 I_0 requirement both converter operates in rectification and inversion mode




Cycloconverter- Operation

- Power flow from load to supply

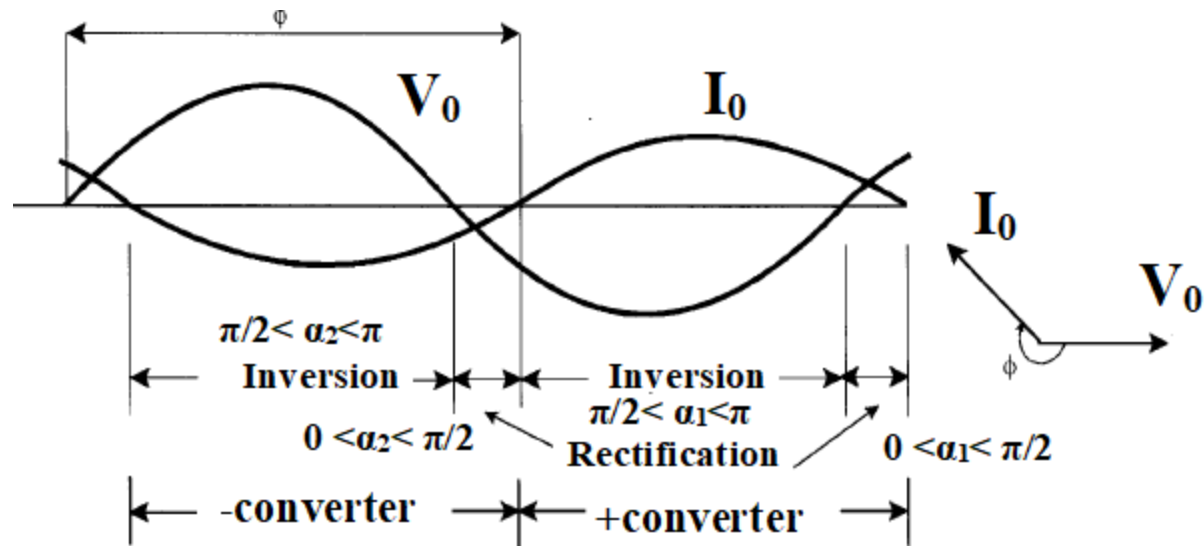



1 ϕ to 1 ϕ Cycloconverter

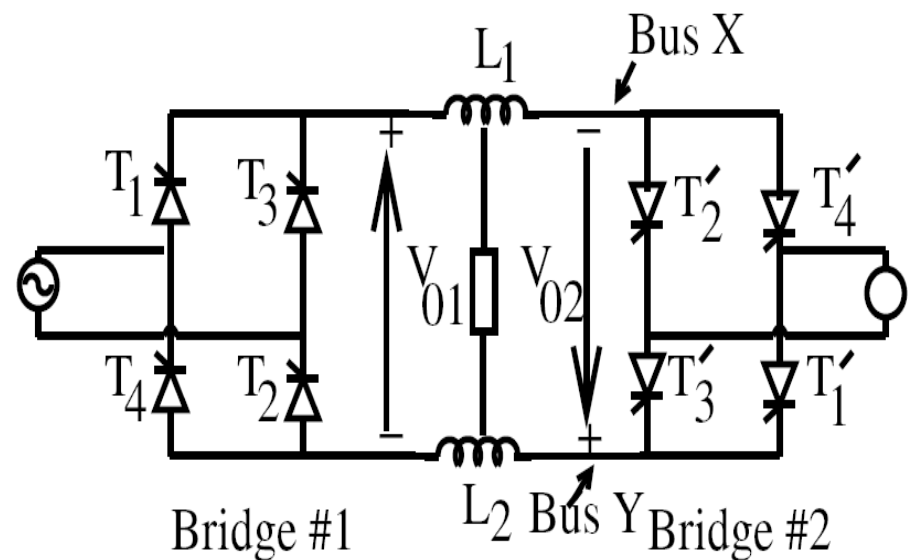- It consists of 2 pulse full controlled converter as +ve and -Ve group Circuit diagram
- The AC output voltage is given by
$$V_{ac} = (\sqrt{2} V_m / \pi) \cos \alpha_{1min}$$
- $V_m \Rightarrow$ Peak value supply voltage
- $V_{ac} \Rightarrow$ RMS value of o/p voltage



3 ϕ to 1 ϕ Cycloconverter

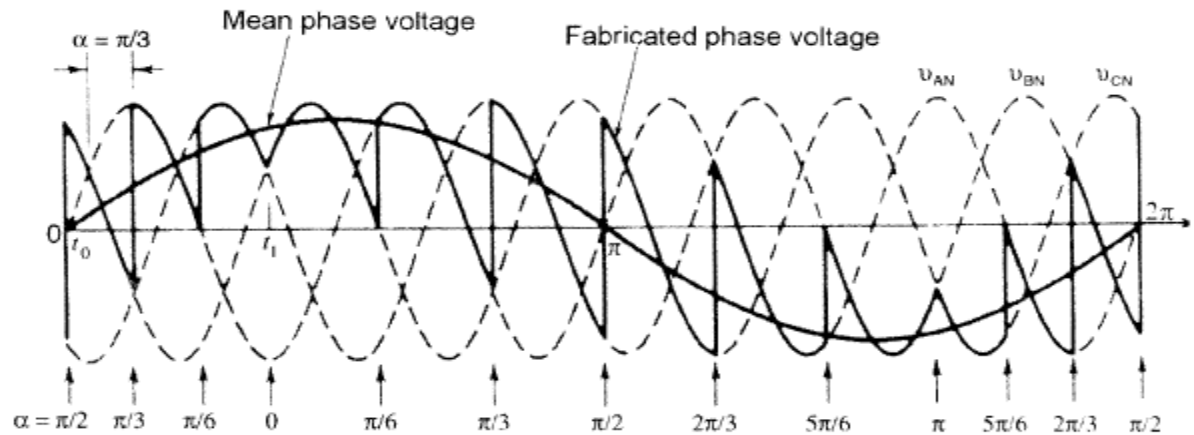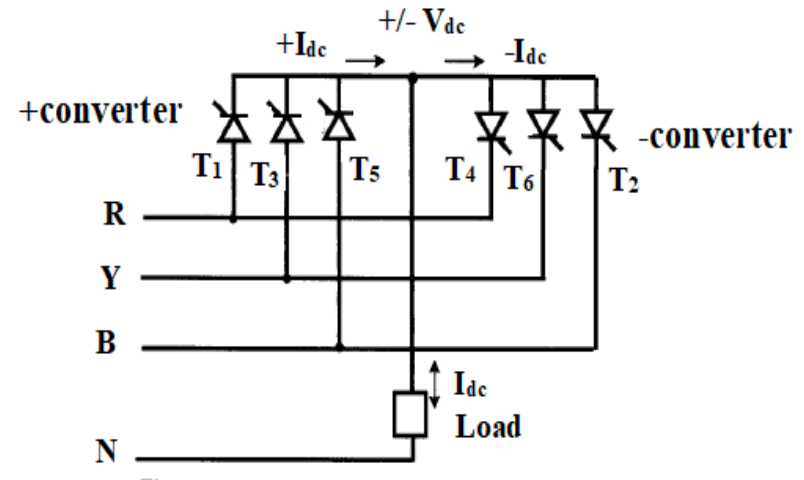- 3 pulse configuration
- α variation is 90, 60, 30, 0, 30, 60, 90, 120, 150, 180, 150, 120 and 90 in cyclic manner
- AC o/p voltage is given by
- $V_{ac} = (3 \sqrt{3} V_{mp} \cos \alpha_{1min}) / \sqrt{2} 2\pi$




3 ϕ to 1 ϕ Cycloconverter

- 6 pulse converter groups
- Firing angle of the converter are continuously varied to obtain low frequency ac at the o/p.
- Cyclic variation of α is

$$90^\circ \longrightarrow 0^\circ \longrightarrow 90^\circ \longrightarrow 180^\circ \longrightarrow 90^\circ$$



AC o/p voltage is given by
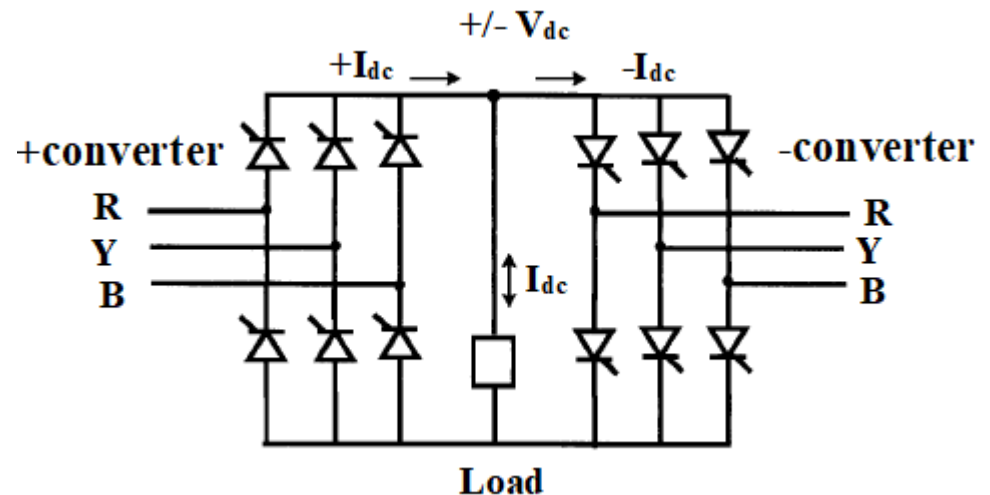
$$V_{ac} = \frac{3 V_{m1}}{\sqrt{2} \pi} \cos \alpha_{1min}$$



3 ϕ to 1 ϕ Cycloconverter

■ o/p voltage waveform

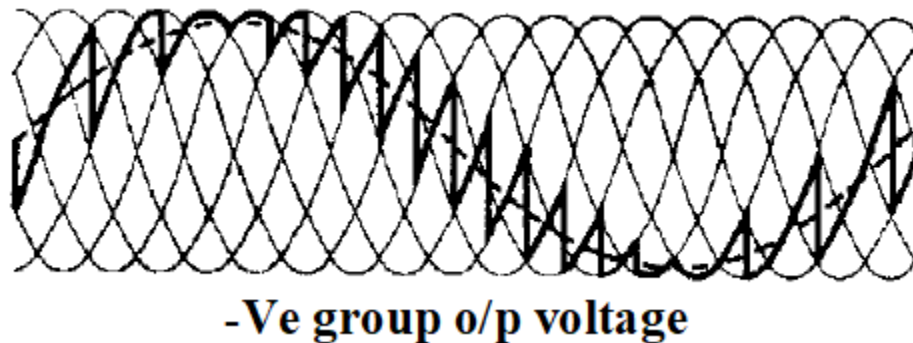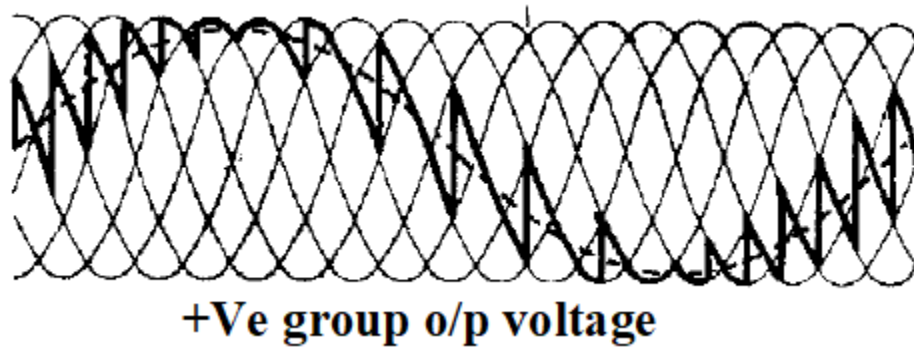


3 ϕ to 3 ϕ Cycloconverter

- 3 ϕ to 3 ϕ Cycloconverter consists of 3 numbers of 3 ϕ to 1 ϕ Cycloconverter.
- 3 numbers of 3 ϕ to 1 ϕ Cycloconverter produces 3 ac o/p which has 120 $^\circ$ phase shift
- Two circuit configurations for 3 ϕ to 3 ϕ Cycloconverter
 - +ve /-ve group using 3 pulse converter group
 - +ve /-ve group using 6 pulse converter group


3 ϕ to 3 ϕ Cycloconverter

- Using 3 pulse converter

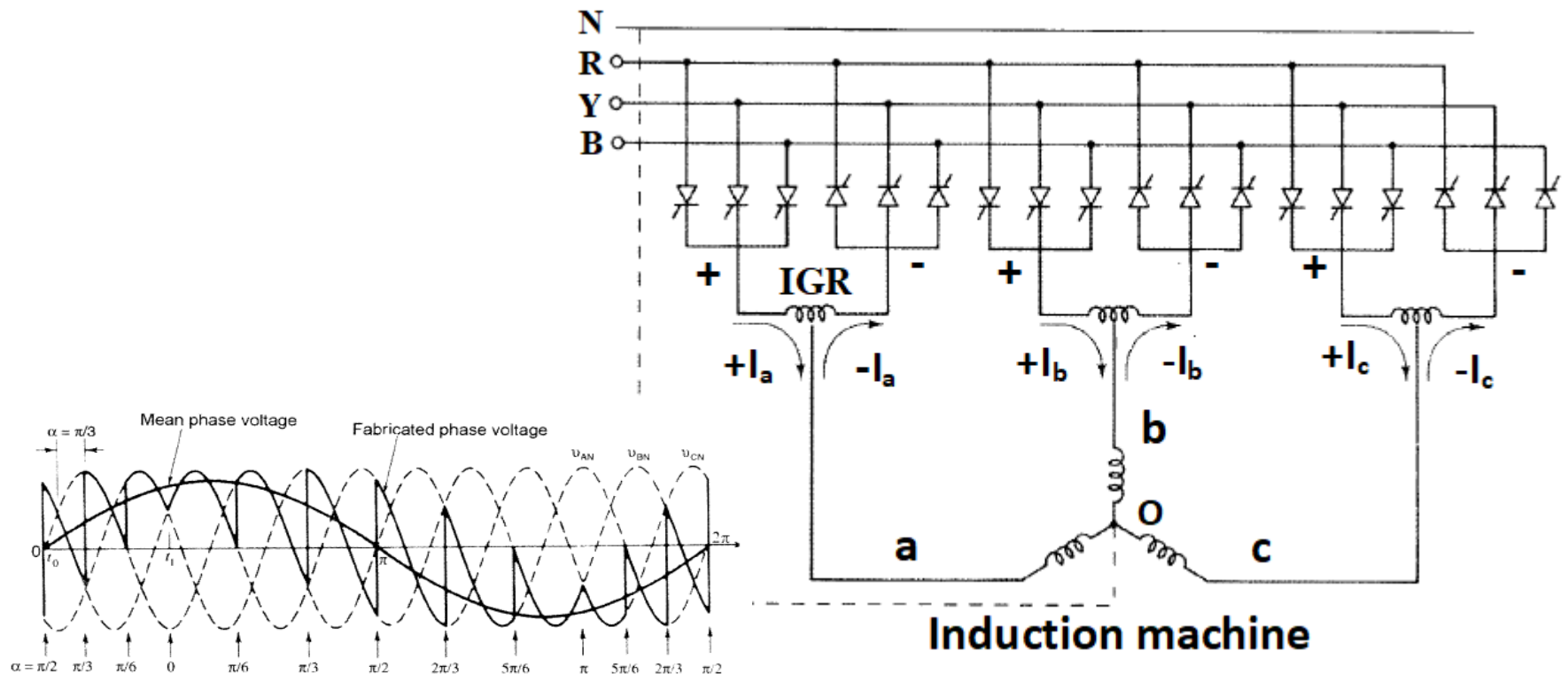


3 ϕ to 3 ϕ Cycloconverter

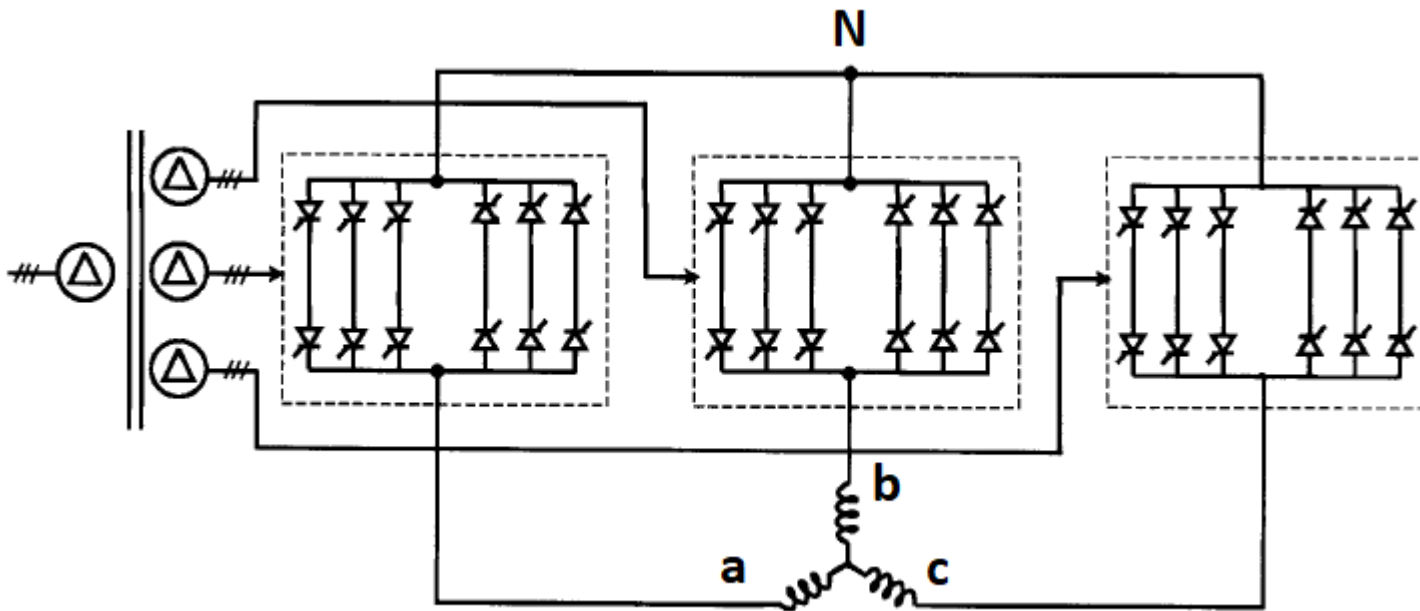- Using 6 pulse converter with non circulating current mode




Circulating current Mode

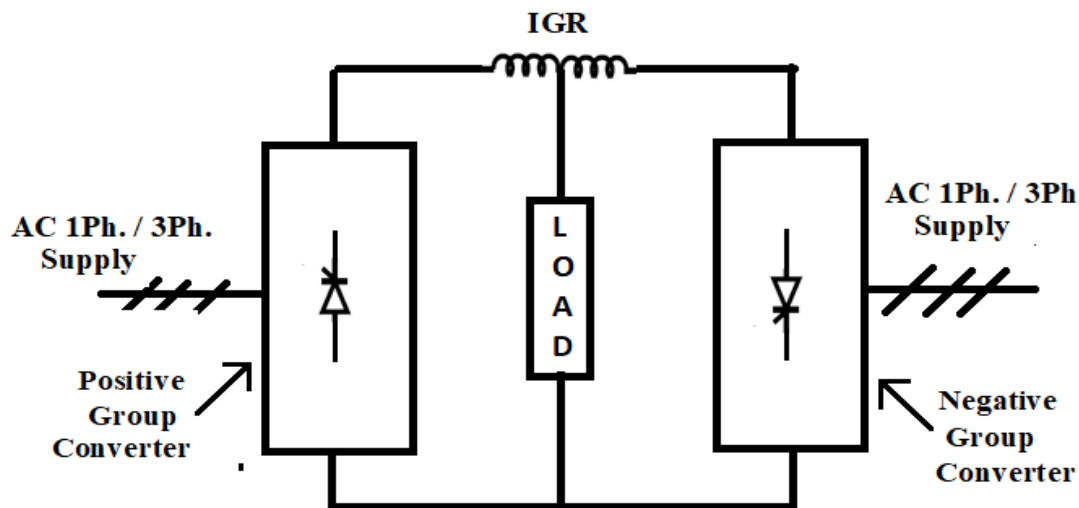- Both converter groups are simultaneously ON.
- Average voltage provided by both groups is same but instantaneous voltages are different
- To reduce circulating current IGR is required



3 ϕ to 3 ϕ Cycloconverter

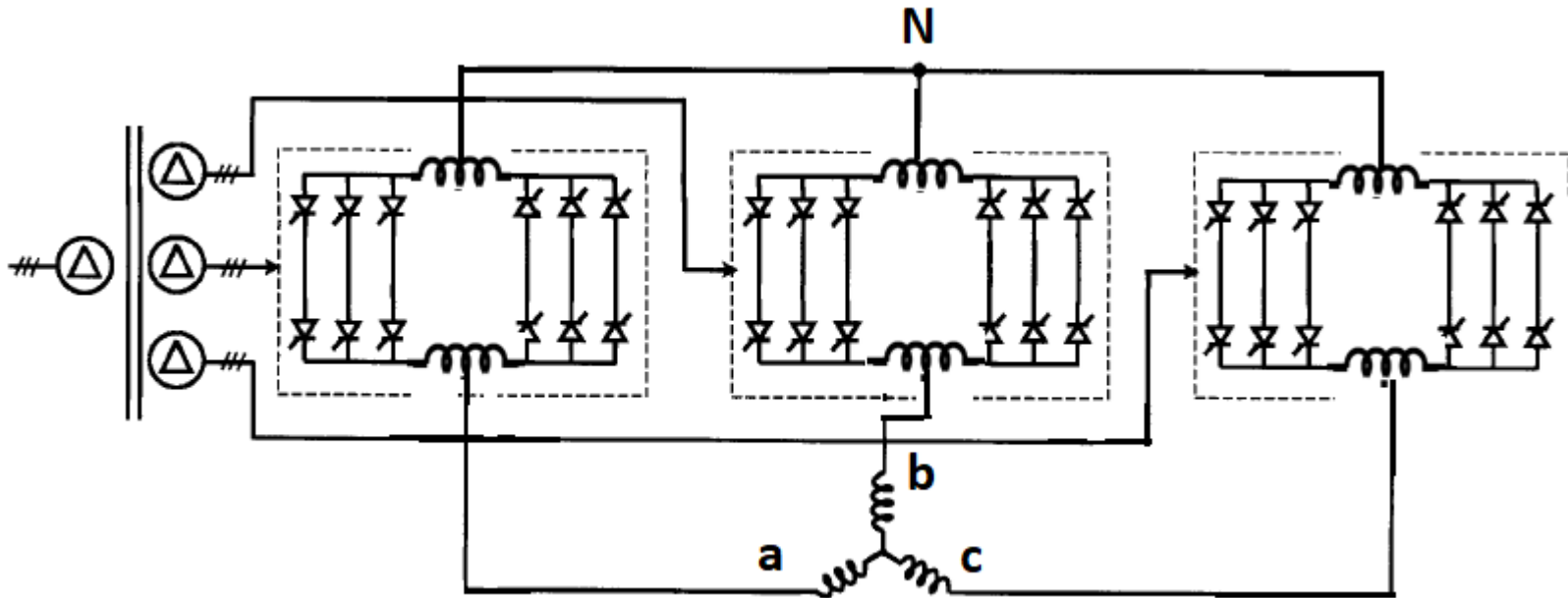- Using 6 pulse converter with circulating current mode




3 ϕ to 3 ϕ Cycloconverter


- O/P Voltage :
Circulating
Current
Mode



+Ve group o/p voltage

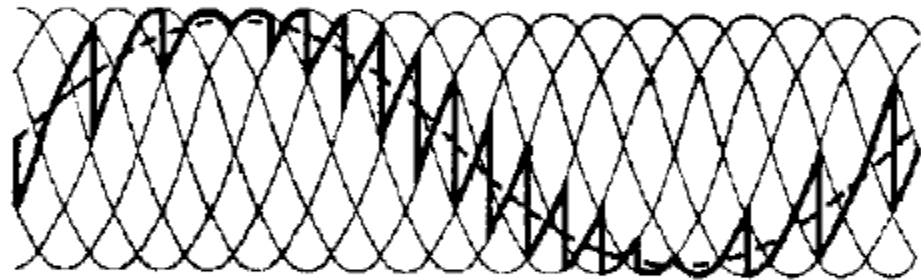

-Ve group o/p voltage

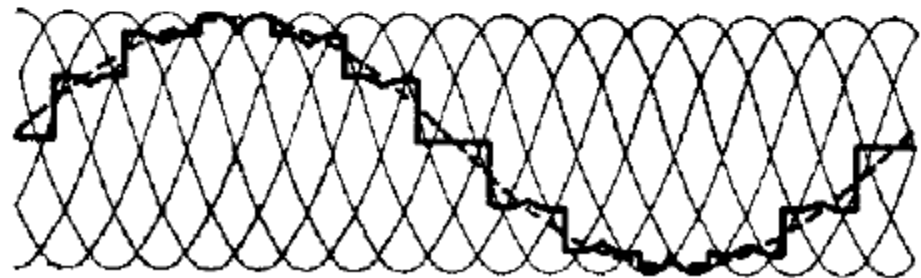

Load o/p voltage

Circulating Current Mode


- Advantages as compared to non circulating current mode
- O/P voltage has less harmonics.
- Frequency range is higher
- Less sub harmonics in the load
- Control is simple
- Less harmonics are injected into the supply
- Line displacement power factor can be controlled

Circulating Current Mode

- Disadvantages as compared to non circulating current mode
- Bulky IGR increases losses and cost
- Circulating current increases additional loading to Thyristors and increase in losses in the devices
- Overdesign increases cost

Non circulating current mode

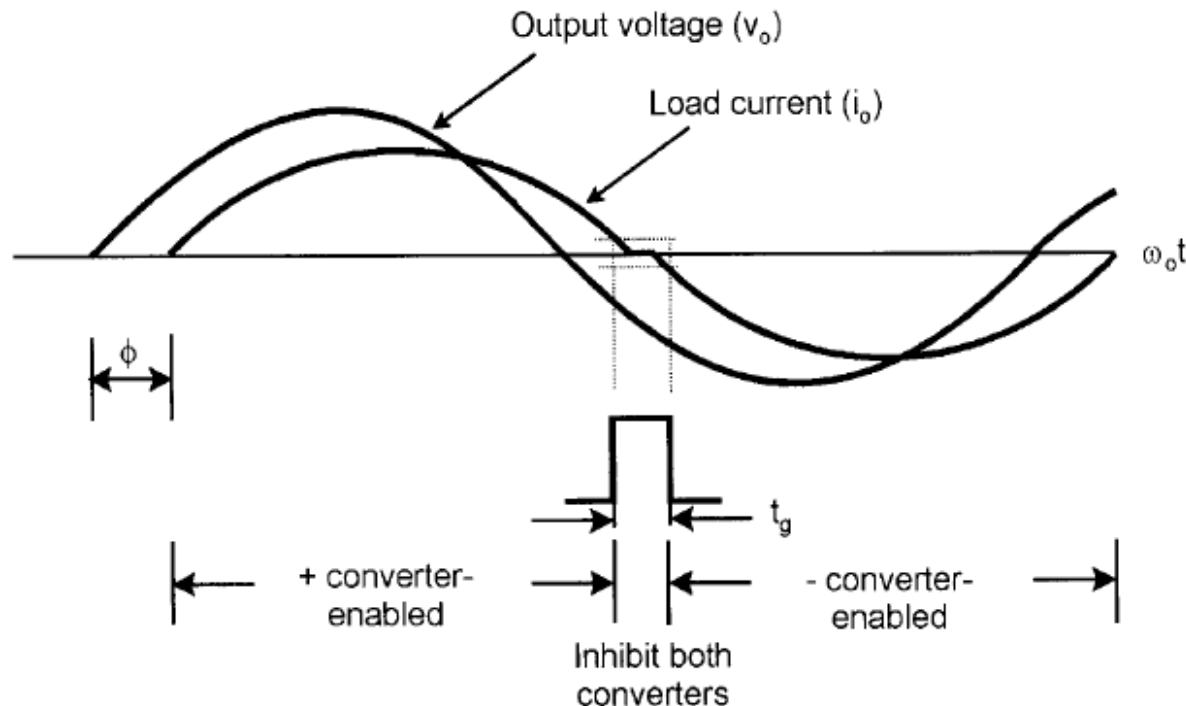- Positive group provides +ve current to the load
- Negative group provides –ve current to the load



Cycloconverter Applications

- Multi megawatt low speed IM and synchronous motor drives for following applications
- Cement and Ball mill drives
- Rolling mill drives
- Slip power recovery scherbius drives
- Variable speed constant frequency power generation for aircraft

THANKS !

Any Questions?