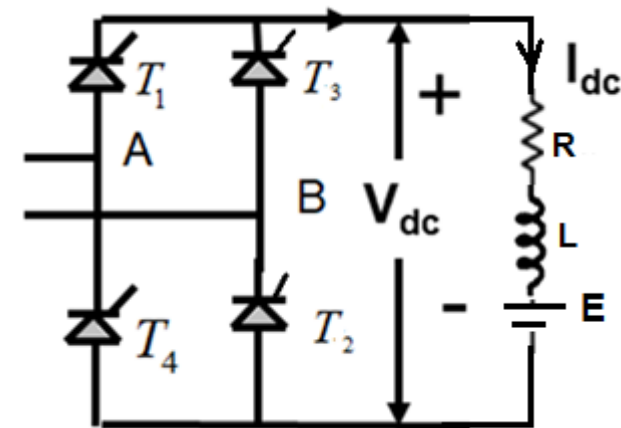



RLE load with continuous conduction

- Supply voltage = 230 V , $E = 100$ V
- $\alpha = 45^\circ$ $R = 5 \Omega$ & $L = \text{large}$
- Power dissipated in R load
- Source current & supply pf
- % ripple in DC O/P voltage



- RLE load with continuous conduction avg $V_L = 0$
- $V_{dc} (av) = I_{dc} \times R + E$

$$I_{dc} = \frac{V_{dc} (av) - E}{R}$$

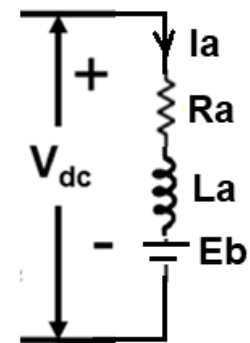

RLE load with continuous conduction

$$V_{dc}(avg) = \frac{2V_m}{\pi} \cos \alpha = \frac{2\sqrt{2} \times 230}{\pi} \cos 45^\circ$$

$$\therefore V_{dc}(avg) = 146.42 \text{ V}$$

$$I_{dc} = \frac{V_{dc}(avg) - E}{R} = \frac{146.42 - 100}{5.0} = 9.284 \text{ A}$$

$$\begin{aligned} \text{Power dissipated in R load} &= I_{dc}^2 \times R \\ &= 9.284^2 \times 5 = 430.96 \text{ W} \end{aligned}$$

$$\text{Source current } I_s(\text{rms}) = 9.284 \text{ A}$$

RLE load with continuous conduction

$$\text{Power factor} = \frac{2\sqrt{2}}{\pi} \cos \alpha = \frac{2\sqrt{2}}{\pi} \cos 45^\circ = 0.636 \text{ lag.}$$

$$V_{dc(\text{av})} = 146.42$$

$$V_{dc(\text{rms})} = 230.0$$


$$FF = \frac{V_{dc(\text{rms})}}{V_{dc(\text{av})}} = \frac{230}{146.42} = 1.5708$$

$$\begin{aligned} \therefore \text{Ripple factor} &= \sqrt{FF^2 - 1} \\ &= 1.211 \end{aligned}$$

$$\therefore \% \text{ Ripple} = 121.1\%$$


Dual converter

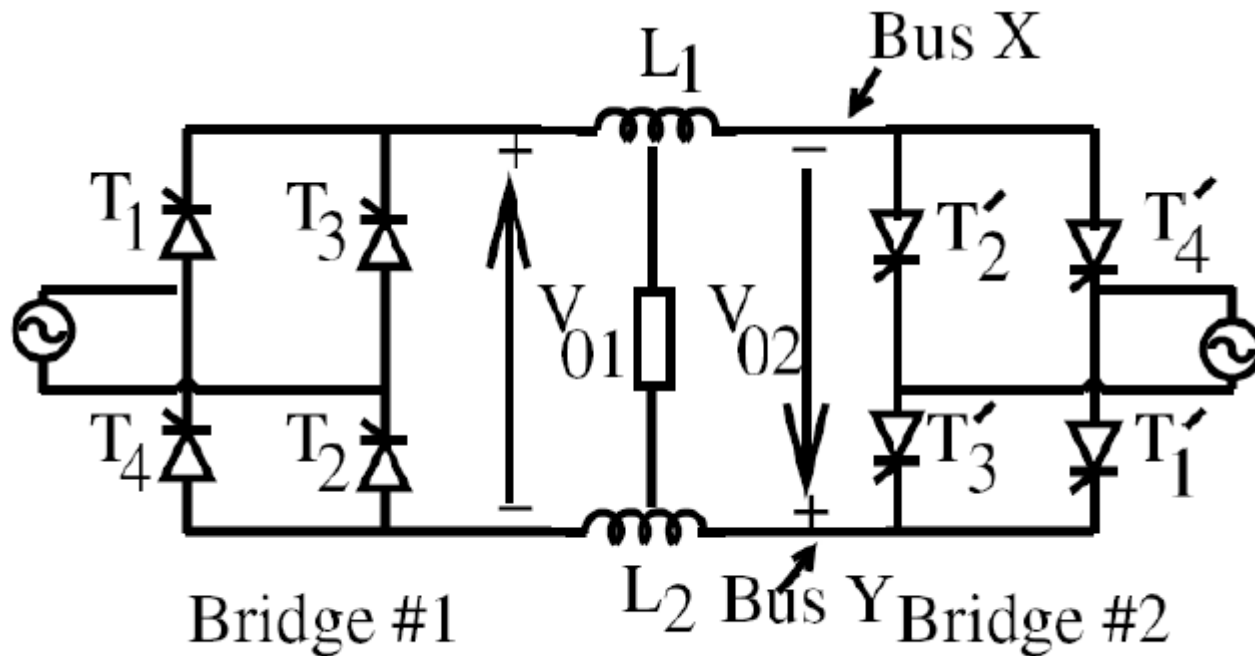- Two full controlled converters connected anti-parallel



Dual converter

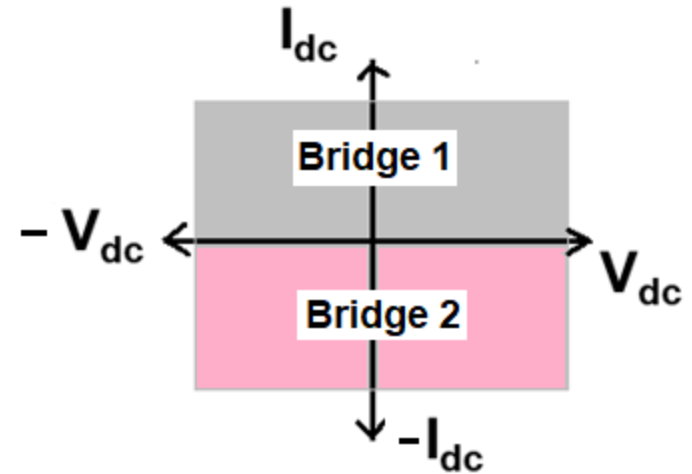- Quadrant operation
- Bridge 1 = I and II
- Bridge 2 = III and IV



- Bridge 1 provides +ve current to load and provides +ve and -ve voltage.

- Bridge 1 $\Rightarrow \alpha_1$


$$V_{o1} = \frac{2V_m}{\pi} \cos \alpha_1$$

- Bridge 2 $\Rightarrow \alpha_2$

$$V_{o2} = \frac{2V_m}{\pi} \cos \alpha_2$$

Dual converter

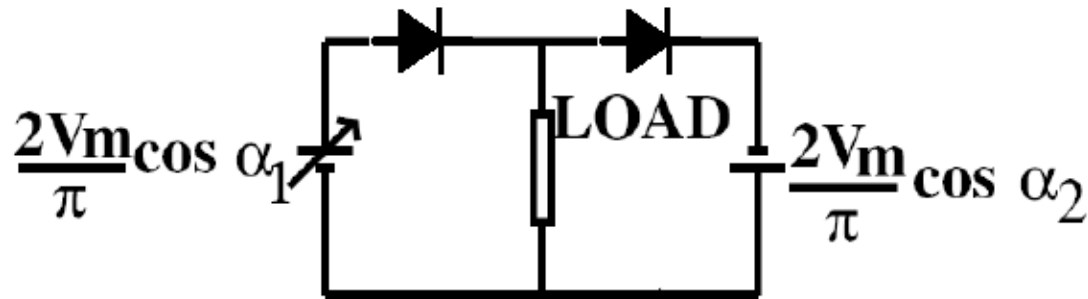
- Average voltage provided by both converters are same



- Applying KVL gives $V_{O1} + V_{O2} = 0$
- $\cos \alpha_1 + \cos \alpha_2 = 0$
- $\cos \alpha_1 = -\cos \alpha_2 \Rightarrow \cos \alpha_1 = \cos(\pi - \alpha_2)$
- $\alpha_1 + \alpha_2 = \pi$

Dual converter


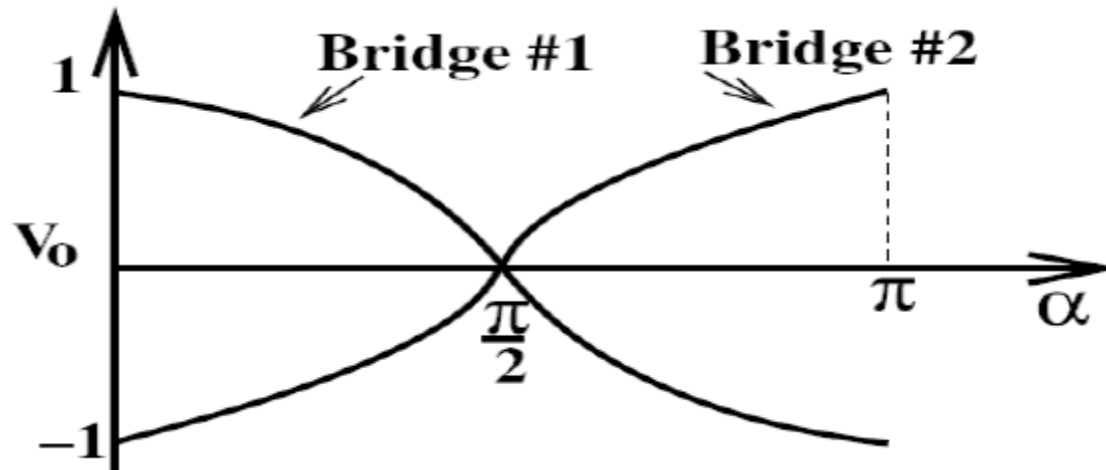
- Circulating mode and non circulating mode



- Inductors L_1 and L_2 are required to limit the circulating current
- Dual converter for speed control of DC Motor



Speed control of sep. excited DC Motor

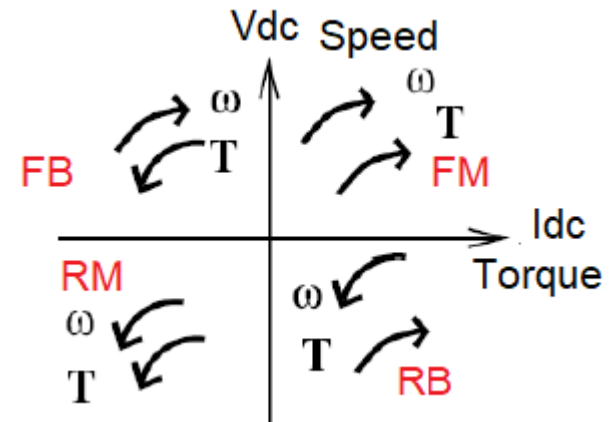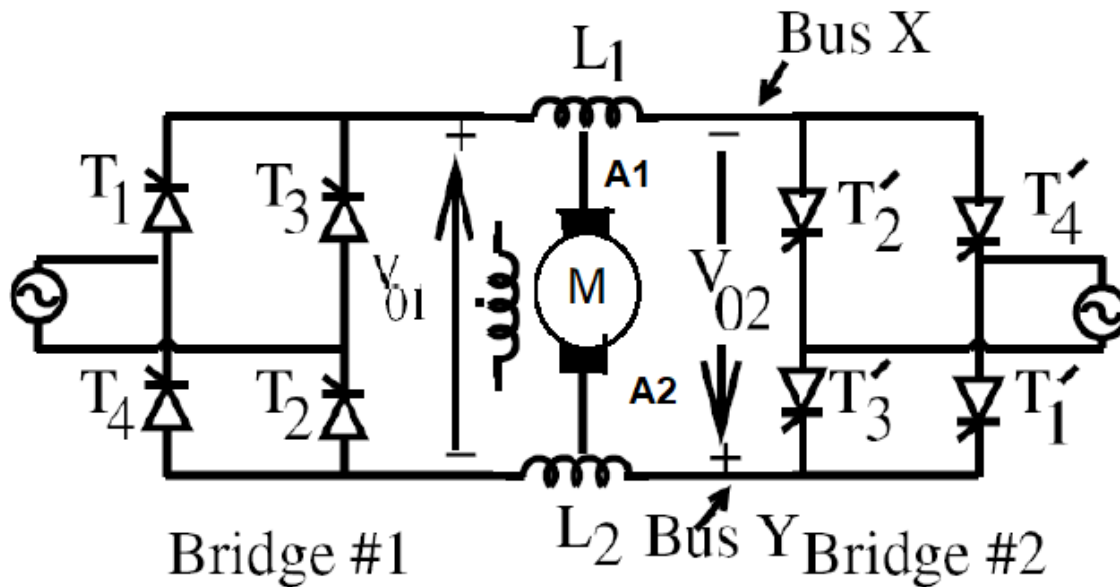- 4 quadrant DC drive
- Armature voltage control



Three phase half wave rectifier

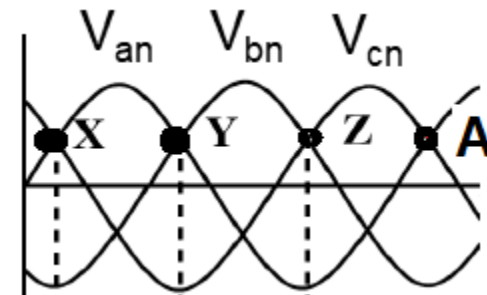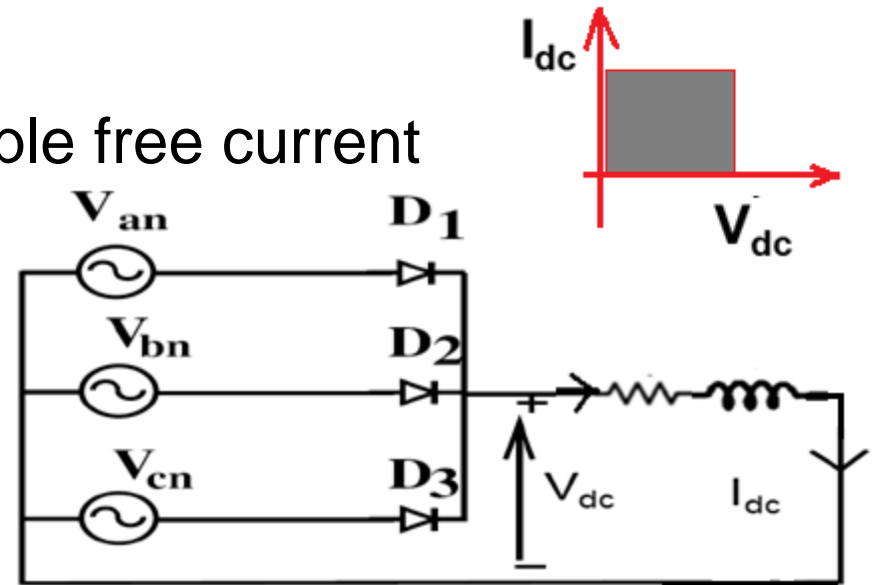- Half wave rectification
- RL load => Smooth and ripple free current
- Between X and Y, V_{an} is maximum positive so D_1 conducts
- Between YZ D_2 conducts
- During ZA period D_3 conducts
- Diode conduction = 120°
- Conduction is continuous



Three phase half wave rectifier


- V_{mp} = Peak value of phase voltage

- $V_{dc} (av) = \frac{3}{2\pi} \int_{\pi/6}^{5\pi/6} V_{mp} \sin\theta d\theta$

- Diode avg current = $I_{dc}/3$


- Diode RMS current = $I_{dc}/\sqrt{3}$

- 3 pulse rectifier

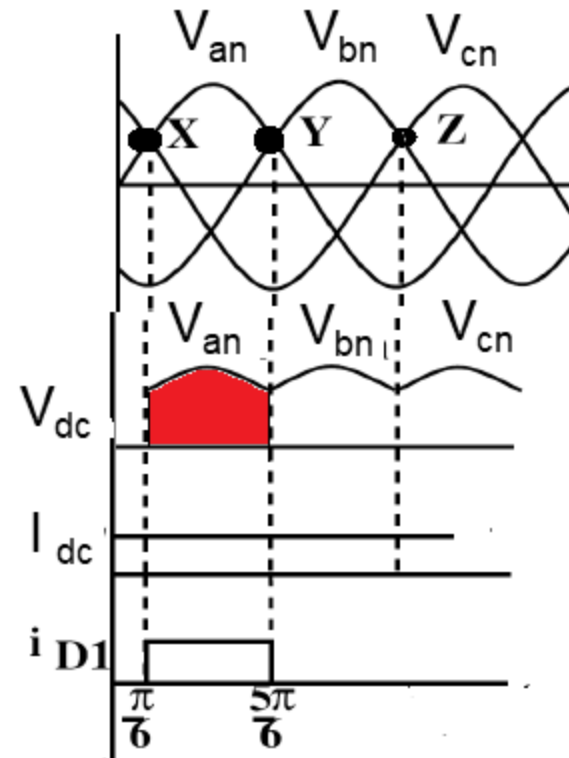


Three phase half wave rectifier
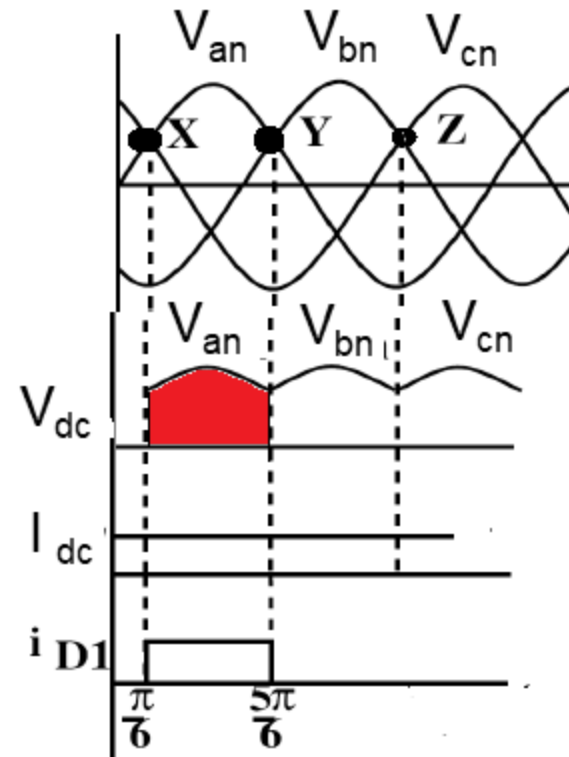
$$\begin{aligned} V_{dc(av)} &= \frac{3}{2\pi} \int_{30}^{150} V_{mp} \sin \theta \cdot d\theta \\ &= \frac{3 V_{mp}}{2\pi} \left[-\cos \theta \right]_{30}^{150} \\ &= \frac{3 V_{mp}}{2\pi} \left[-\cos 150 + \cos 30 \right] \\ &= \frac{3 V_{mp}}{2\pi} \left[\frac{\sqrt{3}}{2} + \frac{\sqrt{3}}{2} \right] \\ &= \frac{3\sqrt{3} V_{mp}}{2\pi} \end{aligned}$$



Three phase half wave rectifier

■ V_{dc}(rms)

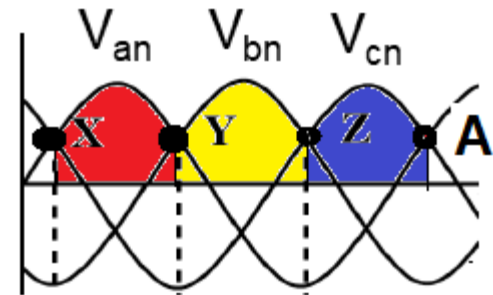

$$V_{dc}(rms) = \left[\frac{3}{2\pi} \int_{30}^{150} V_{mp}^2 \sin^2 \theta \cdot d\theta \right]^{1/2}$$

$$V_{dc}(rms) = \left[\frac{3 V_{mp}^2}{2\pi} \int_{30}^{150} \left(\frac{1 - \cos 2\theta}{2} \right) d\theta \right]^{1/2}$$

$$= \left[\frac{3 V_{mp}^2}{4\pi} \left\{ \int_{30}^{150} d\theta - \int_{30}^{150} \cos 2\theta \cdot d\theta \right\} \right]^{1/2}$$

$$= \left[\frac{3 V_{mp}^2}{4\pi} \left\{ \theta \Big|_{\pi/6}^{5\pi/6} - \frac{1}{2} (\sin 2\theta) \Big|_{30}^{150} \right\} \right]^{1/2}$$

Three phase half wave rectifier

■ Vdc(rms)

$$= \left[\frac{3 V_{mp}^2}{4\pi} \left\{ \left(\frac{5\pi}{6} - \frac{\pi}{6} \right) - \frac{1}{2} (\sin 300^\circ - \sin 60^\circ) \right\} \right]^{\frac{1}{2}}$$

$$= \left[\frac{3 V_{mp}^2}{4\pi} \left\{ \frac{2\pi}{3} - \frac{1}{2} (-0.866 - 0.866) \right\} \right]^{\frac{1}{2}}$$

$$V_{dc(rms)} = \left[\frac{3 V_{mp}^2}{4\pi} \left(\frac{2\pi}{3} + \frac{\sqrt{3}}{2} \right) \right]^{\frac{1}{2}}$$

$$V_{dc(rms)} = 0.8406 V_{mp}$$

Three phase half wave rectifier

- % ripple in the O/P

$$V_{dc(rms)} = 0.8406 V_{mp}$$

$$V_{dc(av)} = 0.82699 V_{mp}$$

$$\therefore FF = \frac{V_{dc(rms)}}{V_{dc(av)}} = 1.01645$$


$$FF^2 = 1.03317$$

$$\therefore \% \text{ Ripple} = \sqrt{1.03317 - 1} = \sqrt{0.3317} \times 100$$

$$\therefore \% \text{ Ripple} = 18.21\%$$

Three phase half wave rectifier

■ VA rating of the transformer

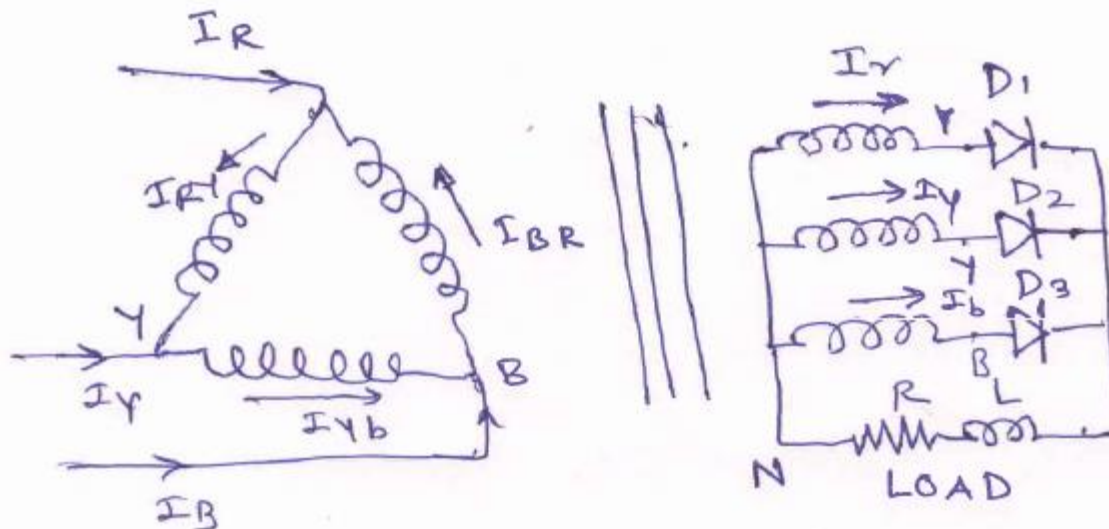


$$I_R = I_{RY} - I_{BR}$$

$$I_Y = I_{YB} - I_{RY}$$

$$I_B = I_{BR} - I_{YB}$$

Three phase half wave rectifier

■ Transformer currents

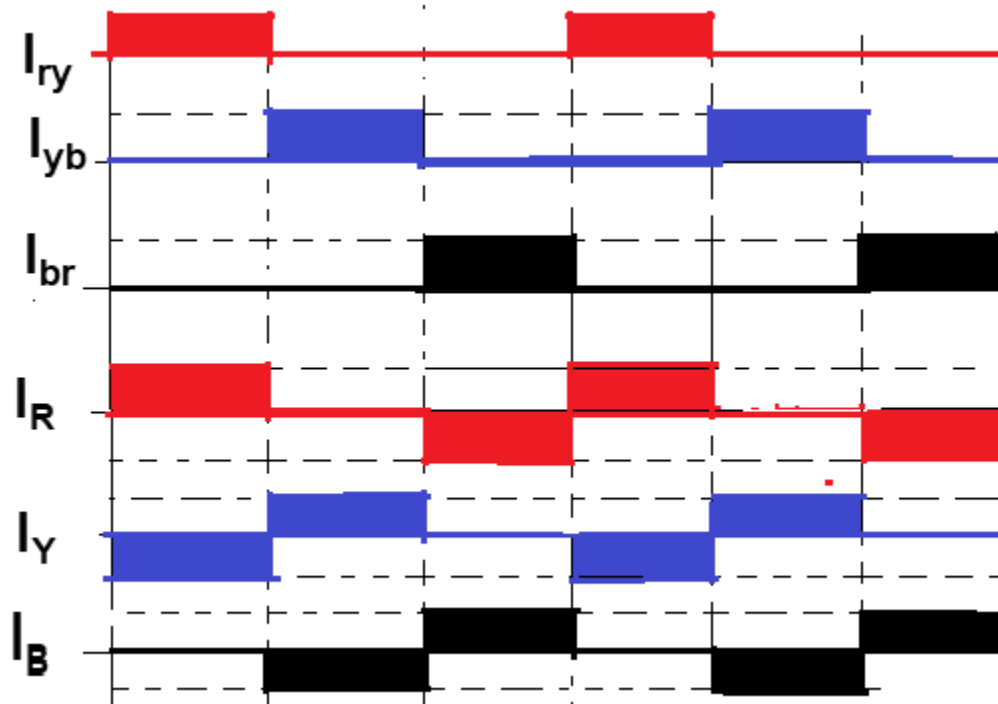

Three phase half wave rectifier

- Assume turns ratio=1, V =phase voltage

- Secondary VA Rating = $3 V_{ph} I_{ph}$

See. VA Rating = $3 \cdot V \times I_{ph} = 3 \times V \times I_{dc} / \sqrt{3}$

But $V_{dc(av)} = \frac{3\sqrt{3}}{2\pi} \times \sqrt{2} V$

$$\therefore V = \frac{V_{dc} \times 2\pi}{3\sqrt{6}}$$

$$\therefore \text{See. VA Rating} = 3 \times \frac{2\pi}{3\sqrt{6}} V_{dc} \cdot \frac{I_{dc}}{\sqrt{3}}$$

$$\text{See. VA rating} = 1.48 V_{dc} \cdot I_{dc}$$

Three phase half wave rectifier

■ Primary VA rating

$$\text{Primary VA Rating} = \sqrt{3} \times V \times \sqrt{\frac{2}{3}} \cdot I_{dc}$$

$$\therefore \text{Primary VA} = \sqrt{2} \times V \cdot I_{dc} = \frac{2\pi}{3\sqrt{6}} V_{dc} \times \sqrt{2} \times I_{dc}$$

$$\therefore \text{Primary VA} = \frac{2\pi}{3\sqrt{6}} \times \sqrt{2} \cdot \frac{V_{dc}}{I_{dc}} = 1.209 V_{dc} \cdot I_{dc}$$

Three phase half wave rectifier

■ Transformer utilization factor

$$\text{Average VA Rating} = \frac{\text{Primary VA} + \text{Sec VA}}{2}$$

$$\begin{aligned}\therefore \text{VA Rating of Tx} &= 1.48 V_{dc} \cdot I_{dc} + 1.209 V_{dc} \cdot I_{dc} \\ &= 1.34 V_{dc} \cdot I_{dc}\end{aligned}$$


$$\text{Tx. Utilization Factor} = \frac{V_{dc} \cdot I_{dc}}{1.34 V_{dc} \cdot I_{dc}} = 0.746$$

Three phase half wave rectifier

- Delta /star transformer is required.
- Transformer secondary current are unidirectional
- Transformer secondary VA rating $= 1.48 V_{dc} I_{dc}$
- Transformer primary VA rating $= 1.209 V_{dc} I_{dc}$
- Transformer VA rating $= 1.34 V_{dc} I_{dc}$
- Disadvantage : transformer VA rating is high
- VA rating of primary and secondary is different


Three phase half wave controlled converter

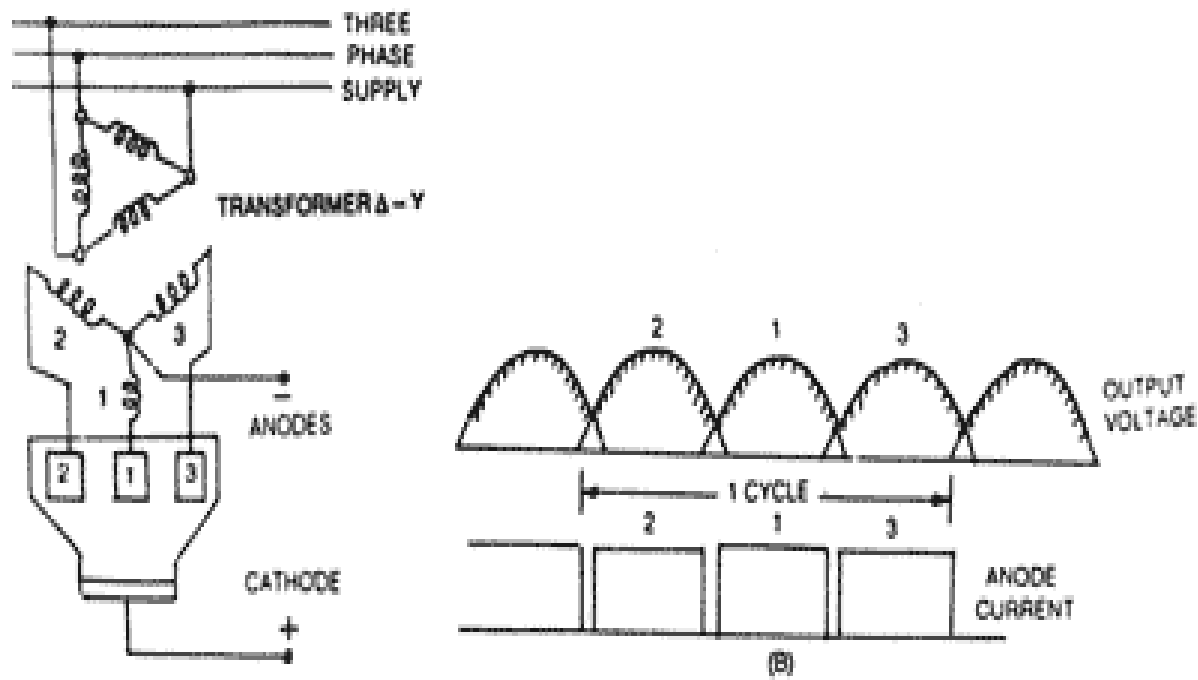- Mercury Arc Rectifier
- 1960 steel plants are established



Mercury Arc Rectifier

- photo

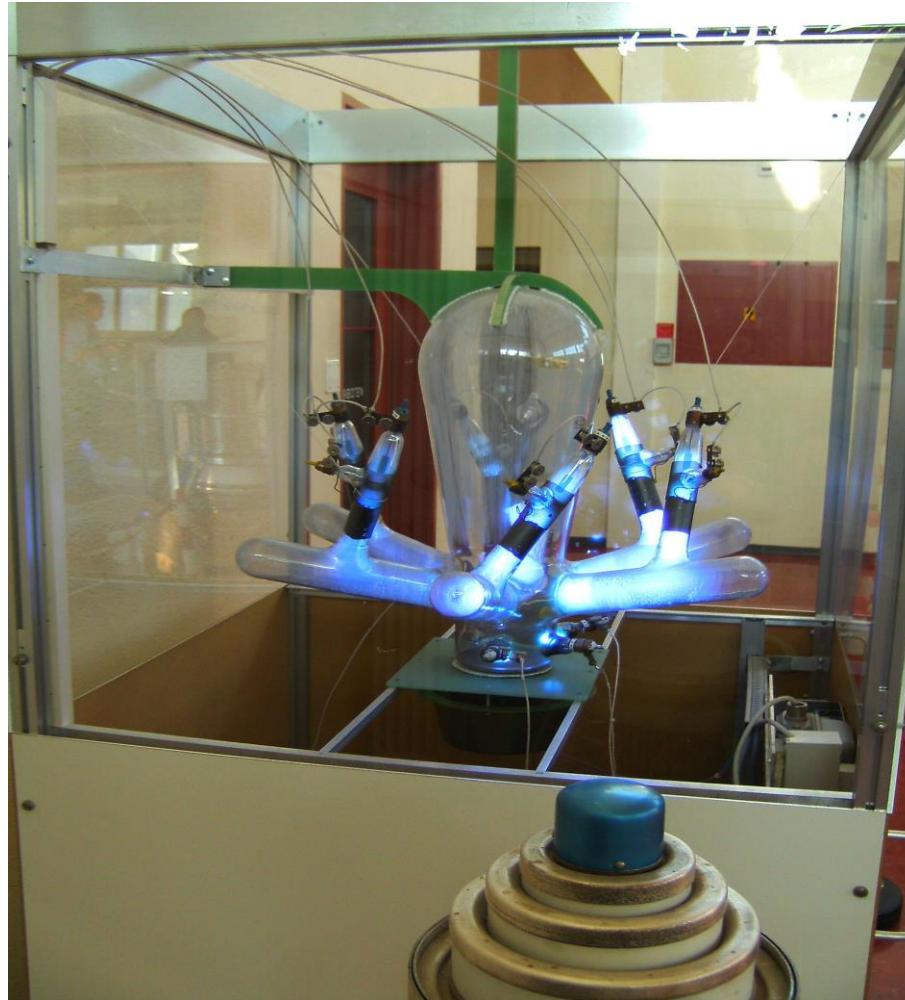


Three phase half wave rectifier

- RL load – Power dissipation
- Phase voltage = 230 V
- $R=10\ \Omega$, L large so I_{dc} smooth and ripple free
- determine power dissipation in R load. Diode average and RMS Current
- I_{dc} is determined from $V_{dc(av)}$

- $$V_{dc(av)} = \frac{3\sqrt{3} V_{mp}}{2\pi}$$

- $$V_{mp} = \sqrt{2} \ 230\text{ V}$$

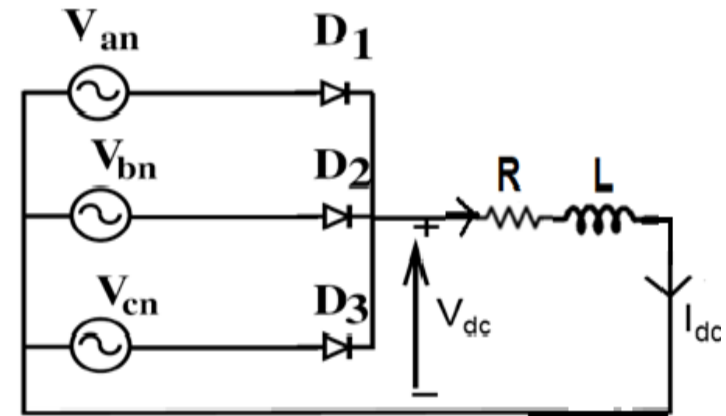


RL load power dissipation

- $V_{dc(av)} = 269 \text{ V}$
- $I_{dc} = V_{dc(av)} / R = 269 / 10 = 26.9 \text{ A}$
- $P_{dc} = V_{dc(av)} \times I_{dc} = 7.236 \text{ kW}$
- Diode $I_{(av)} = I_{dc} / 3 = 26.9 / 3 = 8.96 \text{ A}$
- Diode $I_{(rms)} = I_{dc} / \sqrt{3} = 26.9 / \sqrt{3} = 15.53 \text{ A}$



Three phase half wave rectifier

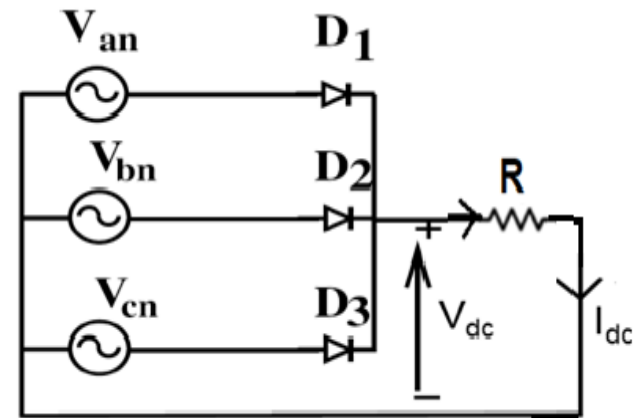- Power dissipation in R load
- Phase voltage = 230 V
- $R = 10 \Omega$,
- For power dissipation
- $V_{dc}(rms)$
- $P_{dc} = [V_{dc}(rms)]^2 / R$
- $V_{dc}(rms) = 0.8406 V_{mp}$
- $V_{dc}(rms) = 0.8406 \times \sqrt{2} \times 230 = 273.42 \text{ V}$
- $P_{dc} = 7.476 \text{ KW}$




Three phase half wave controlled converter with R load

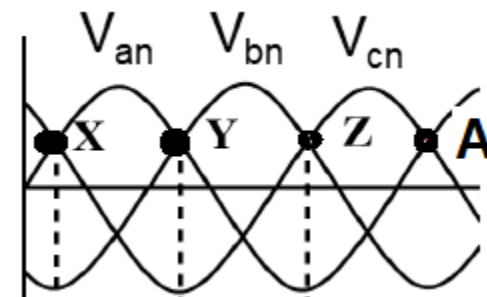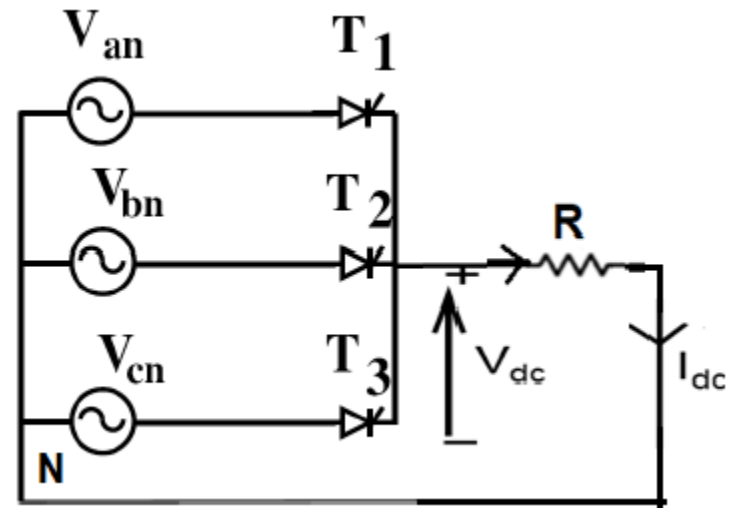- Circuit configuration
- Three phase 4 wire
- Delta / star Tx
- X, Y and Z points
- Represents $\alpha = 0$
- R load $\Rightarrow 0$ to 150°




Waveforms with R load


■ Voltage waveforms at various α

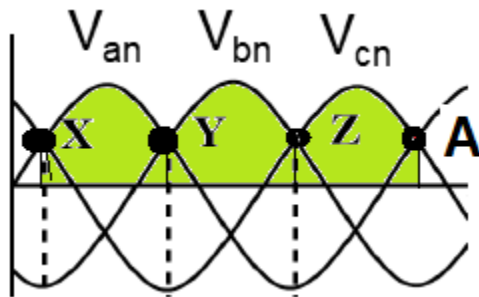


■ $\alpha = 0^\circ$

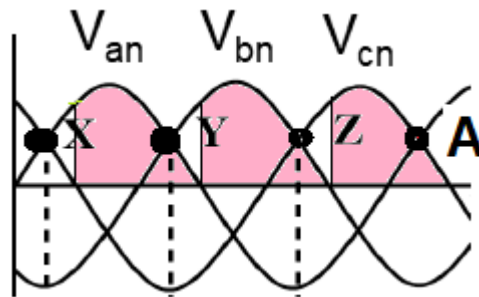


$\alpha = 30^\circ$

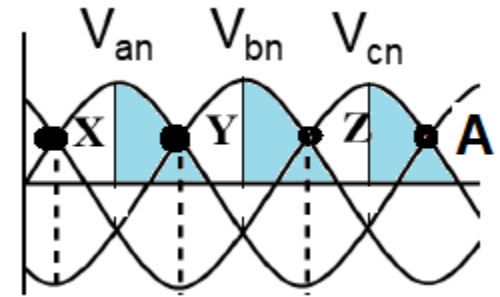


$\alpha = 60^\circ$

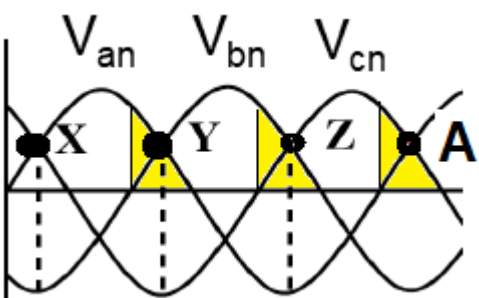

■ $\alpha = 90^\circ$


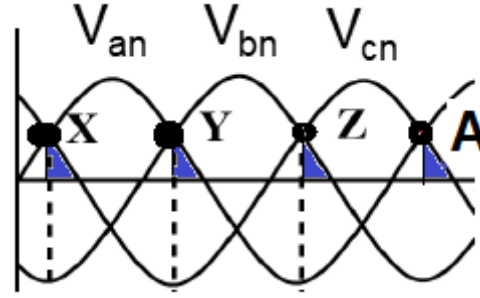


$\alpha = 120^\circ$

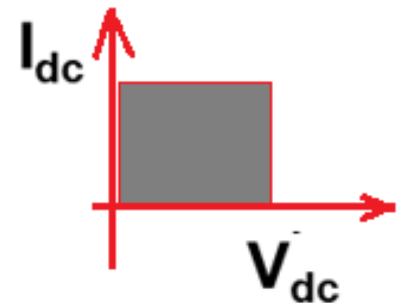

Three phase half wave controlled converter with R load

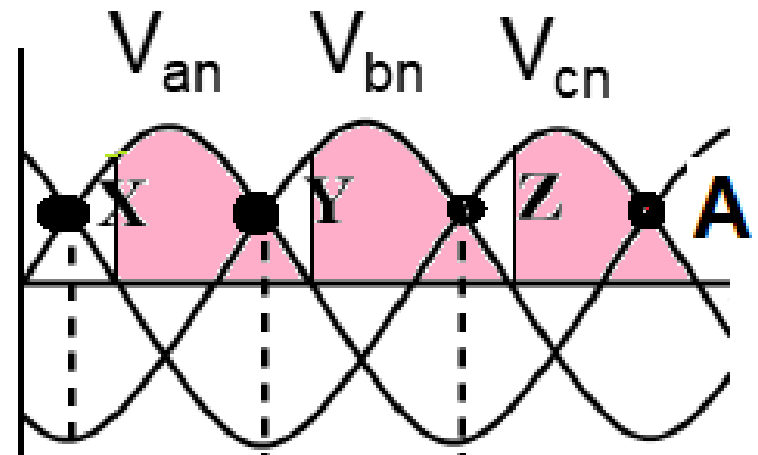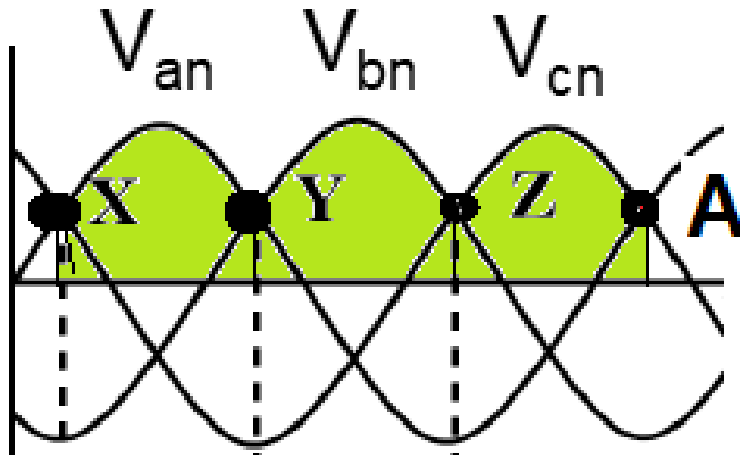
- Continuous conduction= $0 < \alpha < 30^\circ$
- Each device conducts for 120°
- $V_{dc(av)} = \frac{3\sqrt{3}}{2\pi} V_{mp} \cos \alpha$



Three phase half wave controlled converter with R load

■ Continuous conduction
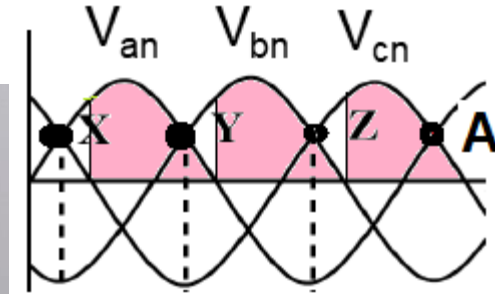
$$\begin{aligned} V_{dc(av)} &= \frac{3}{2\pi} \int_{30+\alpha}^{150+\alpha} V_{mp} \sin \theta \cdot d\theta \\ &= \frac{3 V_{mp}}{2\pi} \int_{30+\alpha}^{150+\alpha} \sin \theta \cdot d\theta \\ &= \frac{3 V_{mp}}{2\pi} \left[-\cos \theta \right]_{30+\alpha}^{150+\alpha} \\ &= \frac{3 V_{mp}}{2\pi} \left[-\cos(150+\alpha) + \cos(30+\alpha) \right] \end{aligned}$$



Three phase half wave controlled converter with R load

■ Continuous conduction

$$= \frac{3V_{mp}}{2\pi} [-\cos 150 \cos \alpha + \sin 150 \sin \alpha + \cos 30 \cos \alpha - \sin 30 \sin \alpha]$$

$$= \frac{3V_{mp}}{2\pi} [-\cos 150 \cos \alpha + \cos 30 \cos \alpha]$$

$$= \frac{3V_{mp}}{2\pi} \left[\frac{\sqrt{3}}{2} \cos \alpha + \frac{\sqrt{3}}{2} \cos \alpha \right]$$


$$= \frac{3V_{mp}}{2\pi} \sqrt{3} \cos \alpha$$

$$= \frac{3\sqrt{3} V_{mp}}{2\pi} \cos \alpha$$

Three phase half wave controlled converter with R load



- Discontinuous conduction = $30^\circ < \alpha < 150^\circ$
- Each device conducts for $150^\circ - \alpha^\circ$
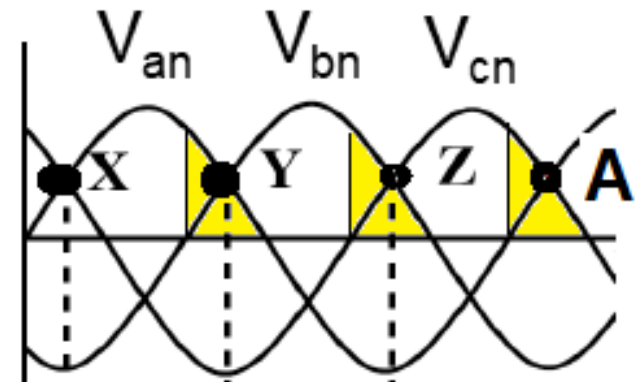
$$\begin{aligned} V_{dc(av)} &= \frac{3}{2\pi} \int_{30+\alpha}^{\pi} V_{mp} \sin \theta \cdot d\theta \\ &= \frac{3 V_{mp}}{2\pi} \left[-\cos \theta \right]_{30+\alpha}^{\pi} \\ &= \frac{3 V_{mp}}{2\pi} \left[-\cos \pi + \cos (30+\alpha) \right] \\ &= \frac{3 V_{mp}}{2\pi} (1 + \cos (30+\alpha)) \end{aligned}$$



R load Power Dissipation

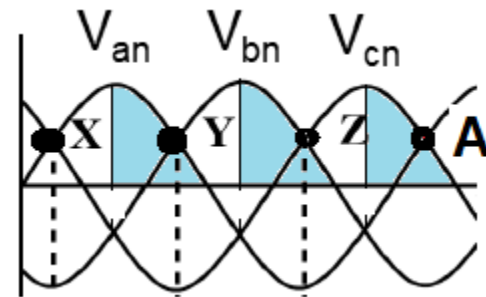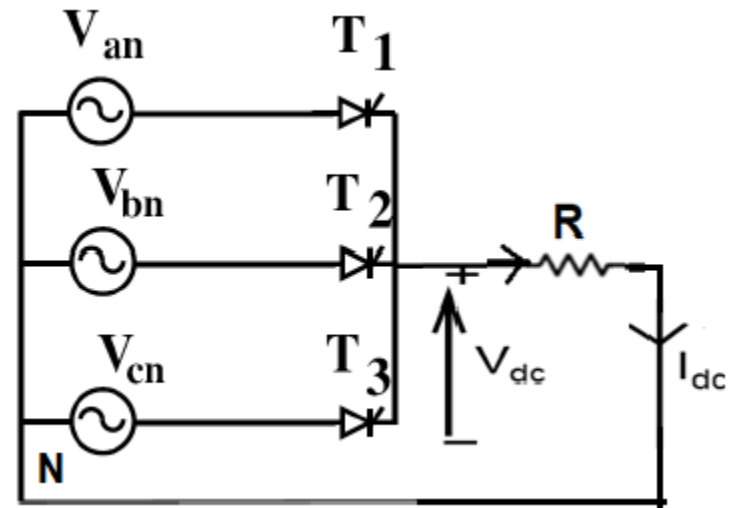- $V_{\text{ph}} = 230 \text{ V}$, $\alpha = 60^\circ$
- $R = 10 \Omega$ determine
- Power dissipated in R
- $V_{\text{dc}}^2(\text{rms}) / R = P_{\text{dc}}$
- $V_{\text{dc}}(\text{rms}) = 228.7$
- $P_{\text{dc}} = 5230.69 \text{ W}$



R load Power Dissipation

$$V_{dc}(rms) = \left[\frac{3}{2\pi} \int_{90}^{180} V_{mp}^2 \sin^2 \theta \cdot d\theta \right]^{1/2}$$

$$= \left[\frac{3 V_{mp}^2}{2\pi} \int_{90}^{180} \left(\frac{1 - \cos 2\theta}{2} \right) \cdot d\theta \right]^{1/2}$$

$$= \left[\frac{3 V_{mp}^2}{4\pi} \left\{ \int_{90}^{180} d\theta - \int_{90}^{180} \cos 2\theta \cdot d\theta \right\} \right]^{1/2}$$

$$V_{dc}(rms) = \left[\frac{3 V_{mp}^2}{4\pi} \left\{ \theta \Big|_{\pi/2}^{\pi} - \frac{1}{2} \sin 2\theta \Big|_{\pi/2}^{\pi} \right\} \right]^{1/2}$$

R load Power Dissipation

$$\begin{aligned} V_{dc(rms)} &= \left[\frac{3 V_{mp}^2}{4\pi} \left\{ \int_{\pi/2}^{\pi} \left(1 - \frac{1}{2} \sin 2\omega \right) d\omega \right\} \right]^{1/2} \\ &= \left[\frac{3 V_{mp}^2}{4\pi} \left\{ \left(\pi - \frac{\pi}{2} \right) - \frac{1}{2} (\sin \pi - \sin \frac{\pi}{2}) \right\} \right]^{1/2} \\ &= \left[\frac{3 V_{mp}^2}{4\pi} \left\{ \pi/2 + \frac{1}{2} \right\} \right]^{1/2} \end{aligned}$$



Putting values,

$$= \left[\frac{3 \times (\sqrt{2} \times 230)^2}{4\pi} \left(\frac{\pi}{2} + \frac{1}{2} \right) \right]^{1/2}$$

$$V_{dc(rms)} = 228.7 \text{ V}$$

Numerical Problem Battery charging

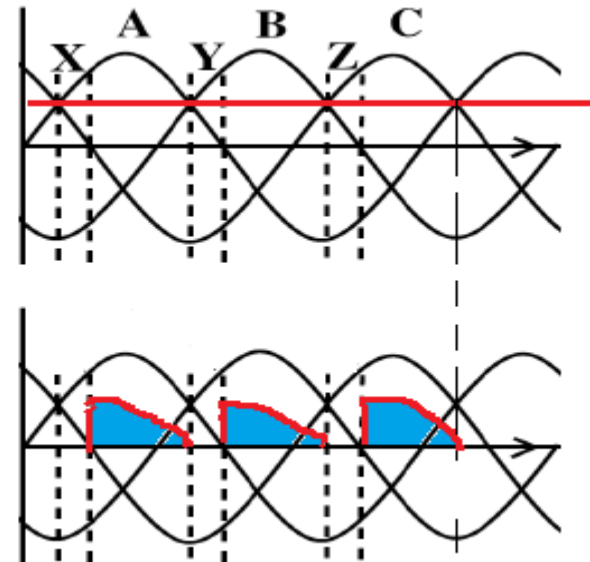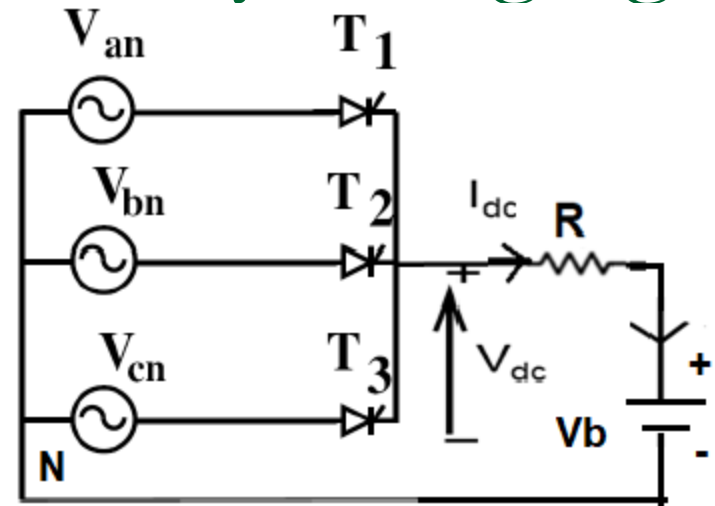- $V_{\text{ph}} = 230 \text{ V}$ $R = 5 \Omega$
- $V_b = 150 \text{ V}$, $\alpha = 30^\circ$
- Determine the average
- Charging current



Numerical Problem Battery charging

$$\begin{aligned} V_{mp} \sin \theta_1 &= V_b \quad \therefore \sin \theta_1 = \frac{V_b}{V_{mp}} \\ \sin \theta_1 &= \frac{150}{\sqrt{2} \times 230} \quad \theta_1 = \sin^{-1}(0.4611) = 27.45^\circ \\ \therefore \theta_2 &= 180 - 27.45 = 152.55^\circ \\ i &= \frac{V_{mp} \sin \theta - V_b}{R} \\ \text{Average charging current} \\ I_{dc} &= \frac{3}{2\pi} \int_{\theta_1}^{\theta_2} \frac{V_{mp} \sin \theta - V_b}{R} \cdot d\theta \\ I_{dc} &= \frac{3}{2\pi R} \left[\int_{60}^{152.55} V_{mp} \sin \theta \cdot d\theta - \int_{60}^{152.55} V_b \cdot d\theta \right] \end{aligned}$$

Numerical Problem Battery charging

$$I_{dc} = \frac{3}{2\pi R} \left[V_{mp}(-\cos\theta) \Big|_{60}^{152.55} - V_b \left(\frac{152.55}{180} \pi - \frac{\pi}{3} \right) \right]$$



$$I_{dc} = \frac{3}{2\pi R} \left[\sqrt{2} \times 230 (-\cos 152.55 + \cos 60) - 150 (1.61) \right]$$

$$I_{dc} = \frac{3}{2\pi \times 5} \left[\sqrt{2} \times 230 \times 1.3874 - 150 \times (1.61) \right]$$

$$\therefore I_{dc} = 20.031 \text{ A}$$

Three phase half wave controlled converter with R L load

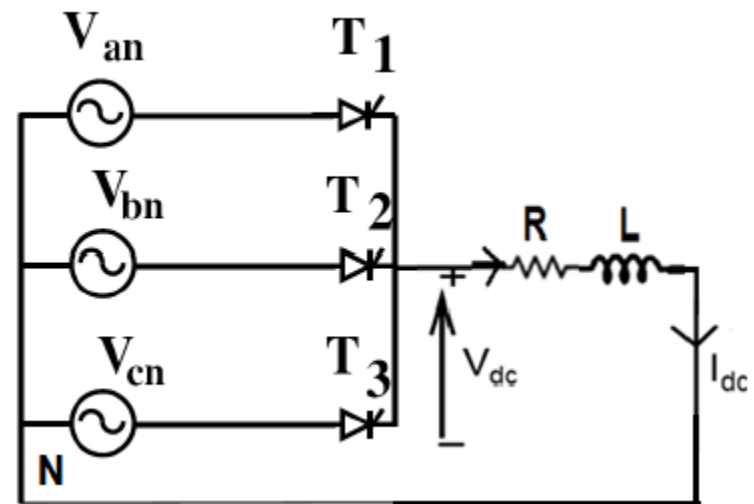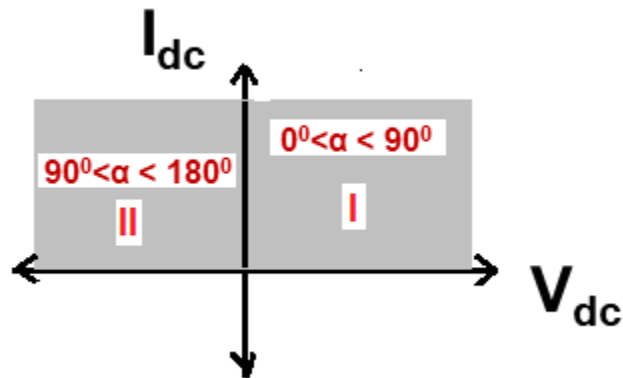
- 3 pulse full controlled converter
- 2 quadrant converter



- Quadrant 1 \Rightarrow Rectifier operation
- Quadrant 2 \Rightarrow Inverter operation


Three phase half wave controlled converter with R L load

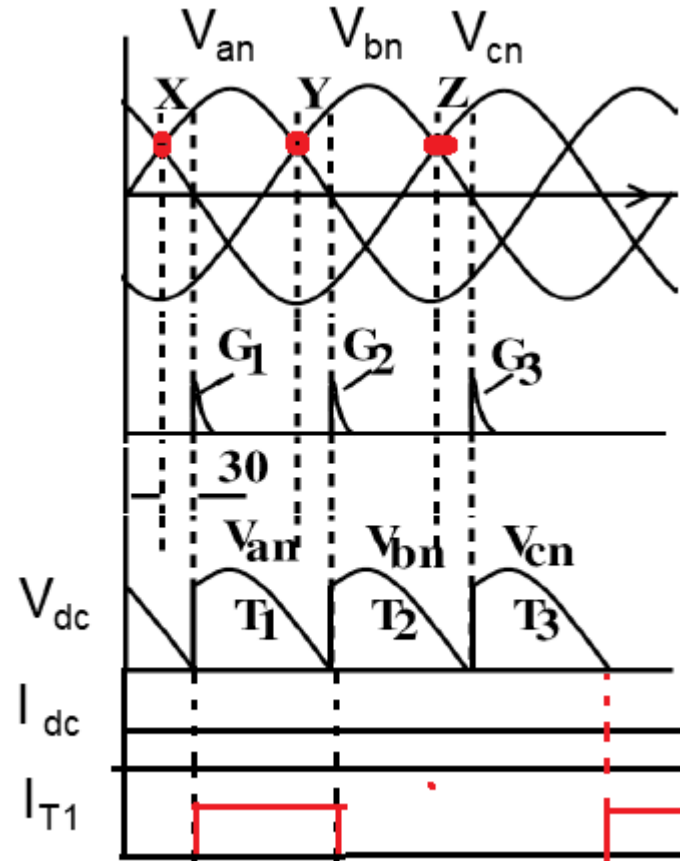- Rectifier operation
- $0^\circ < \alpha < 90^\circ$
- $V_d(\text{av}) = \frac{3\sqrt{3}}{2\pi} V_{mp} \cos \alpha$
- Power flow from AC to DC
- Side
- Device conduction = 120°
- DC current is smooth & ripple free




Waveforms with R L load


■ Voltage waveforms at various α

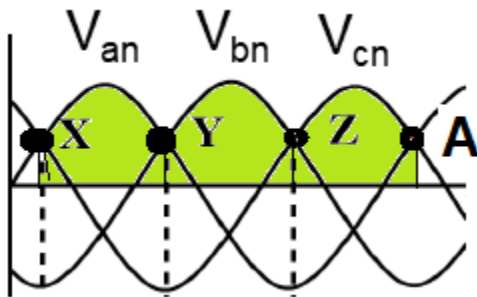


■ $\alpha = 0^\circ$

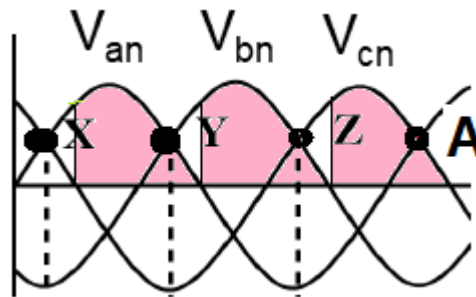


$\alpha = 30^\circ$

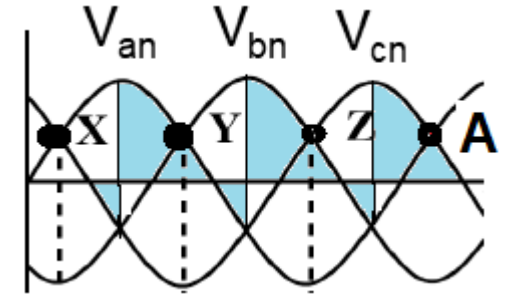


$\alpha = 60^\circ$

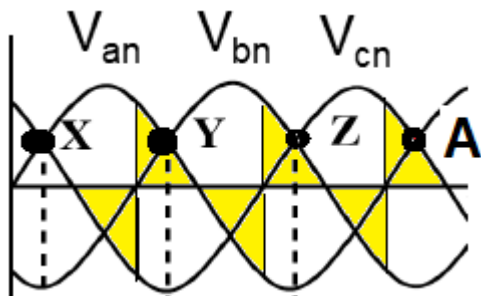

■ $\alpha = 90^\circ$

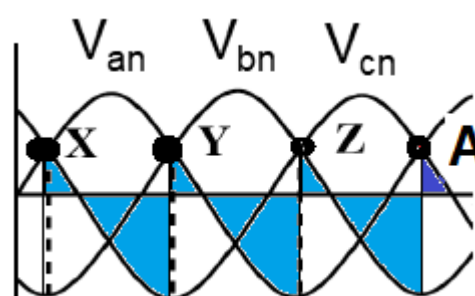

$\alpha = 120^\circ$

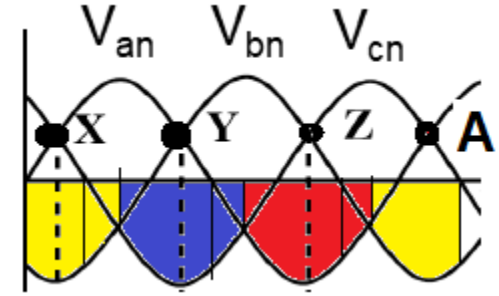

$\alpha = 180^\circ$

Three phase half wave controlled converter with R L load

■ Inverter operation

■ $90^\circ < \alpha < 180^\circ$

■ $V_d(\text{av}) = \frac{3\sqrt{3}}{2\pi} V_{mp} \cos \alpha$



■ Power flow from dC to AC

■ Side

■ Device conduction = 120°



■ DC current is smooth
& ripple free

$I_{dc} = [V_b - V_{dc}(\text{av})]/R$

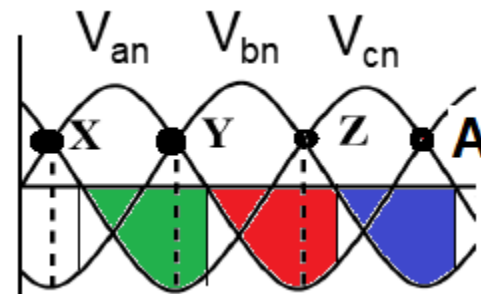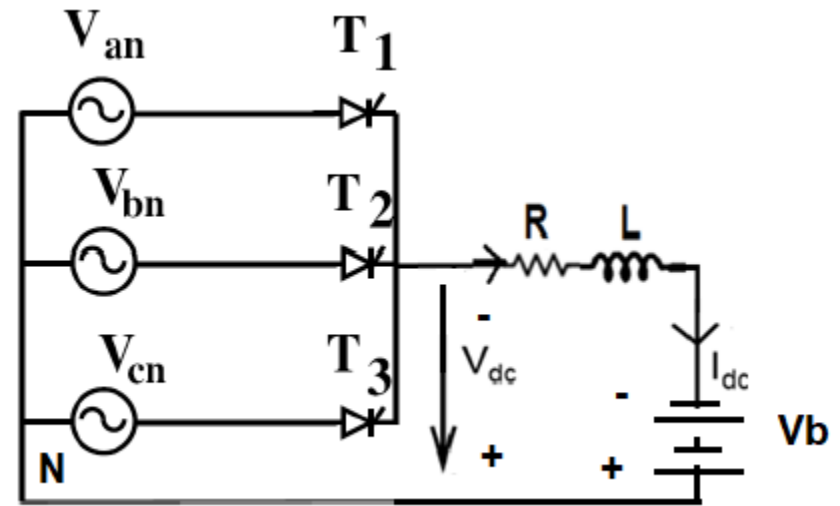



3 phase full wave diode bridge

- 3 pulse rectifier

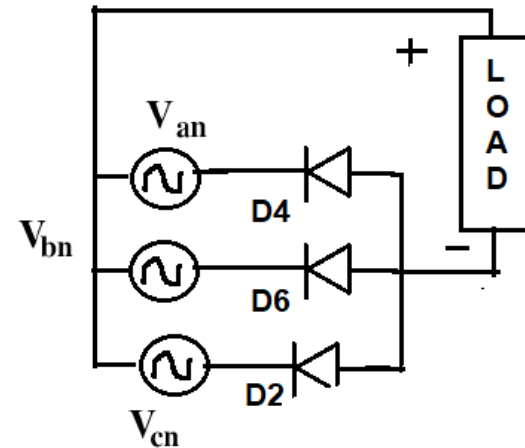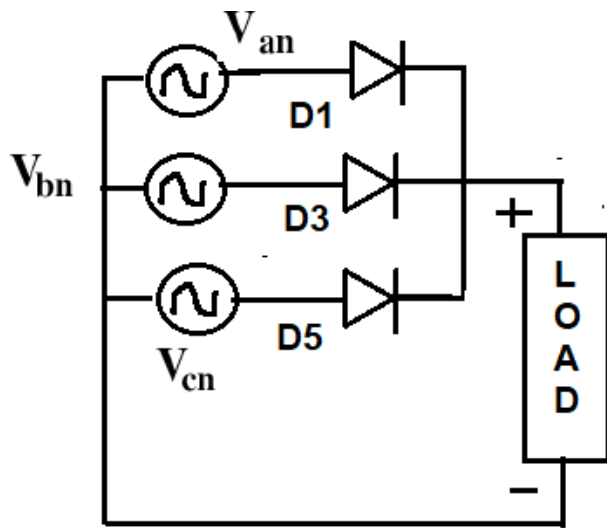

3 phase full wave diode bridge



■ 6 pulse Rectifier

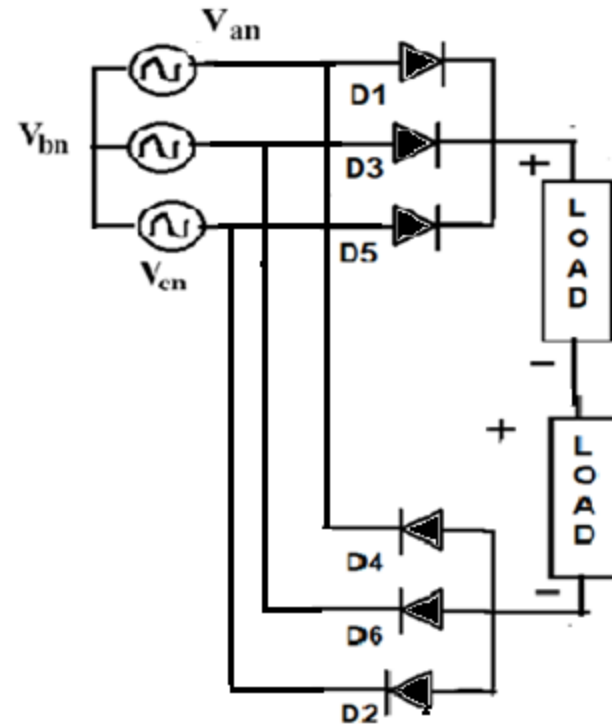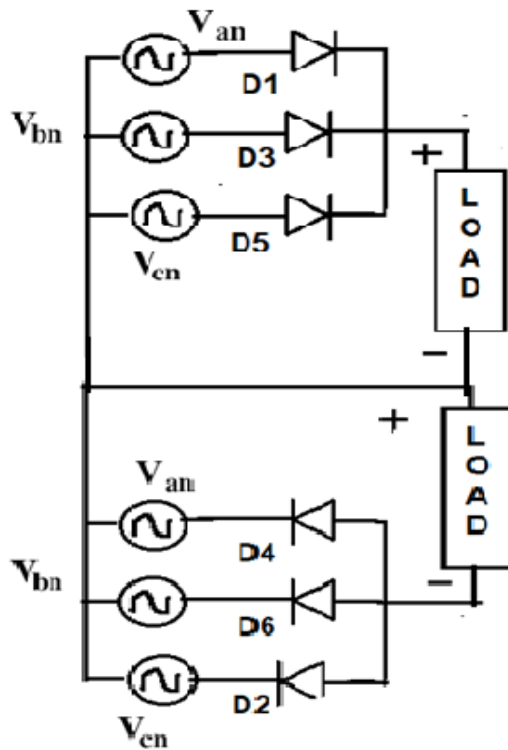

- Outputs is connected in series where as input are connected in parallel

3 phase full wave diode bridge


- 6 pulse Rectifier

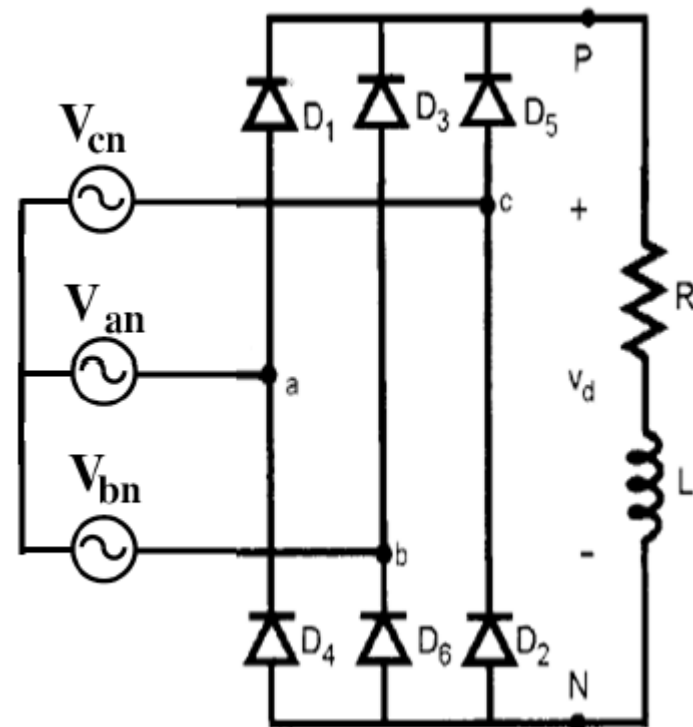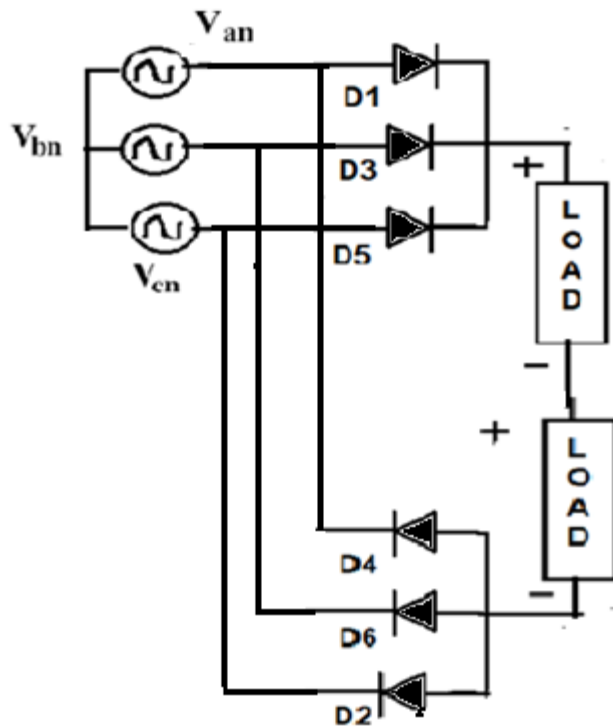

- Outputs is connected in series where as input are connected in parallel

3 phase full wave diode bridge


■ 6 pulse rectifier

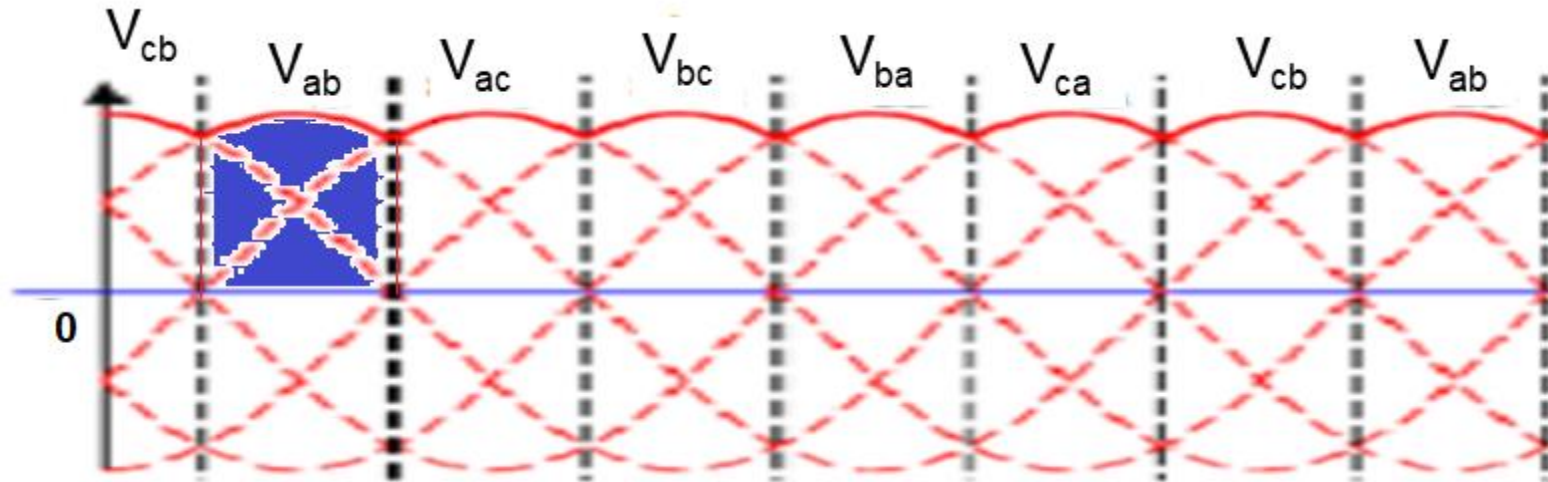


- Draw the three line voltage waveform V_{ab} V_{bc} and V_{ca}
- Invert V_{ab} V_{bc} and V_{ca} to obtain V_{ba} V_{cb} and V_{ac}

3 phase full wave diode bridge

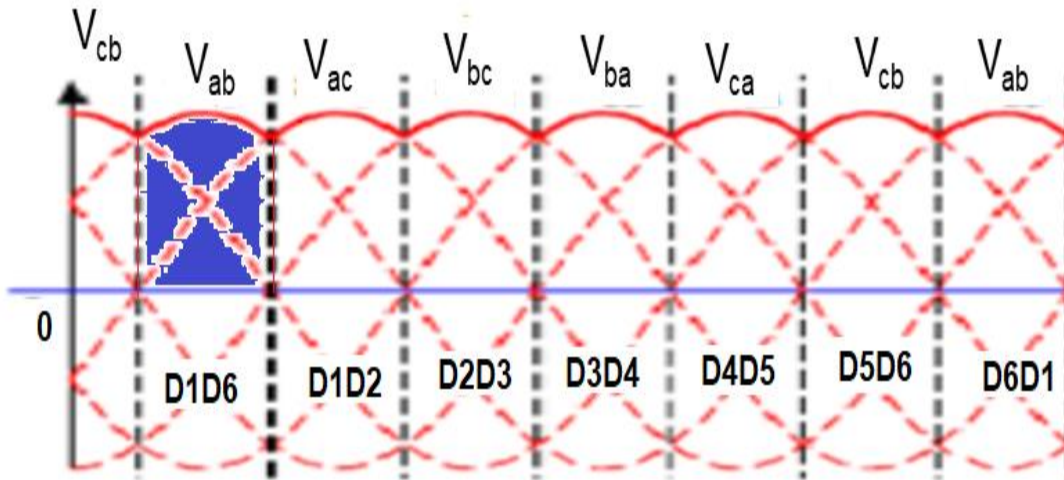- Devices are named as per conducting sequence




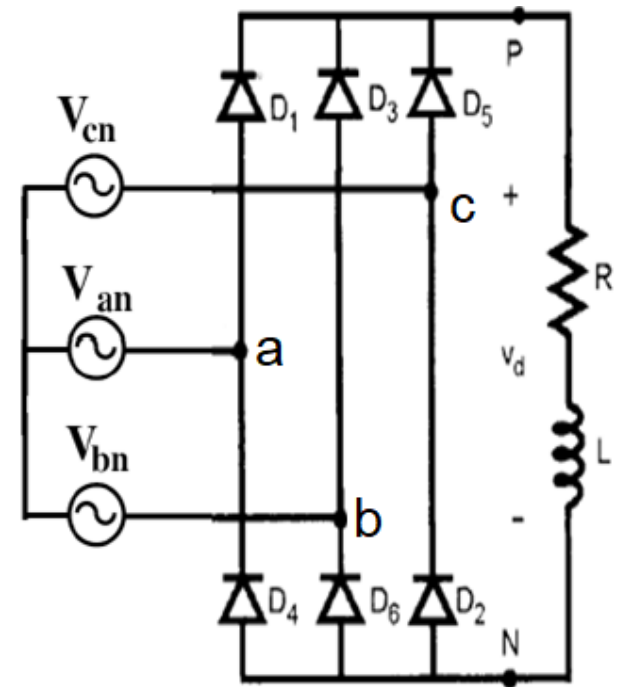- One device from upper group &
- one device from lower group is on
- Each device conducts for 120°



3 phase full wave diode bridge

■ Vdc (av)

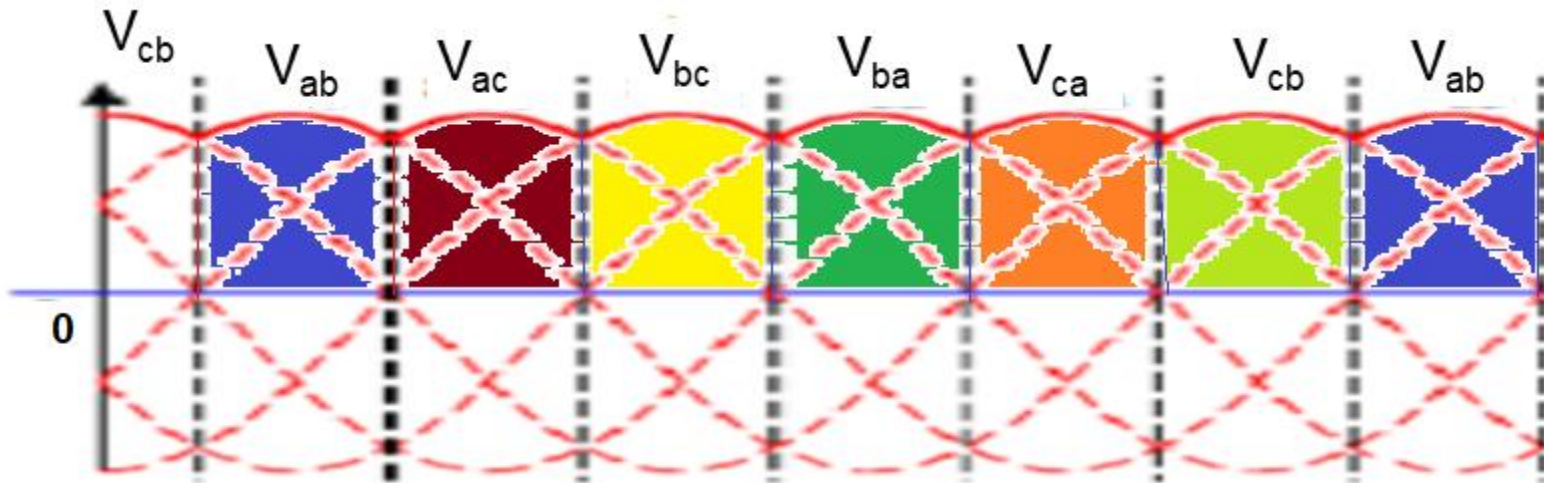


$$■ \quad V_{dc(av)} = \frac{6}{2\pi} \int_{60}^{120} V_{ml} \sin\theta \, d\theta = \frac{3V_{ml}}{\pi}$$

■ $V_{ml} \Rightarrow$ peak amplitude of line voltage

3 phase full wave diode bridge

■ V_{dc}(rms)

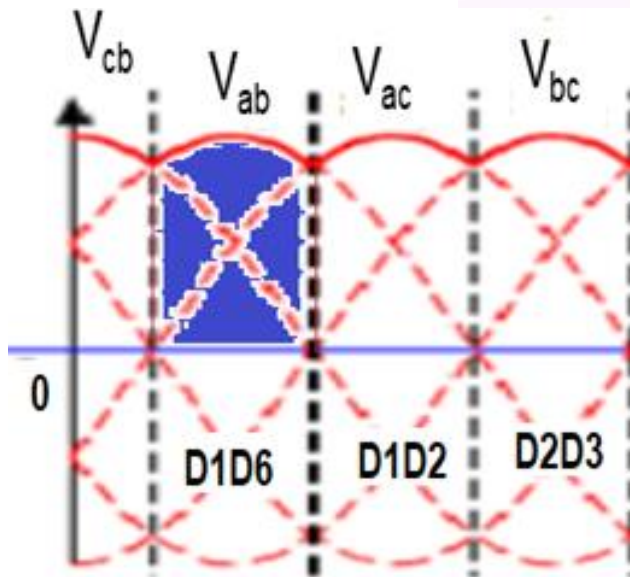

$$V_{dc(rms)} = \left[\frac{6}{2\pi} \int_{60}^{120} V_{mL}^2 \sin^2 \theta \cdot d\theta \right]^{1/2}$$

$$= \left[\frac{3V_{mL}^2}{2\pi} \int_{60}^{120} \left(\frac{1 - \cos 2\theta}{2} \right) \cdot d\theta \right]^{1/2}$$

$$= \left[\frac{3V_{mL}^2}{2\pi} \left\{ \int_{60}^{120} d\theta - \int_{60}^{120} \cos 2\theta \cdot d\theta \right\} \right]^{1/2}$$

$$= \left[\frac{3V_{mL}^2}{2\pi} \left\{ \theta \Big|_{\pi/3}^{2\pi/3} - \frac{1}{2} \sin 2\theta \Big|_{60}^{120} \right\} \right]^{1/2}$$

3 phase full wave diode bridge

■ Vdc (rms)

$$V_{dc(rms)} = \left[\frac{3 V_{mL}^2}{2\pi} \left\{ \left(\frac{2\pi}{3} - \frac{\pi}{3} \right) - \frac{1}{2} (\sin 240^\circ - \sin 120^\circ) \right\} \right]^{\frac{1}{2}}$$

$$= \left[\frac{3 V_{mL}^2}{2\pi} \left\{ \frac{\pi}{3} - \frac{1}{2} \left(-\frac{\sqrt{3}}{2} - \frac{\sqrt{3}}{2} \right) \right\} \right]^{\frac{1}{2}}$$



$$= \left[\frac{3 V_{mL}^2}{2\pi} \left\{ \left(\frac{\pi}{3} + \frac{\sqrt{3}}{2} \right) \right\} \right]^{\frac{1}{2}}$$

$$V_{dc(rms)} = 0.95577 V_{mL}$$

3 phase full wave diode bridge


- O/P voltage ripple
- $V_{dc(av)} = 0.95492 V_{ml}$
- $V_{dc(rms)} = 0.95577 V_{ml}$
- $FF = V_{dc(rms)} / V_{dc(av)} = 1.00089$
- $\% ripple = \sqrt{(FF^2 - 1)} \times 100$
- $\% ripple = 4.21\%$

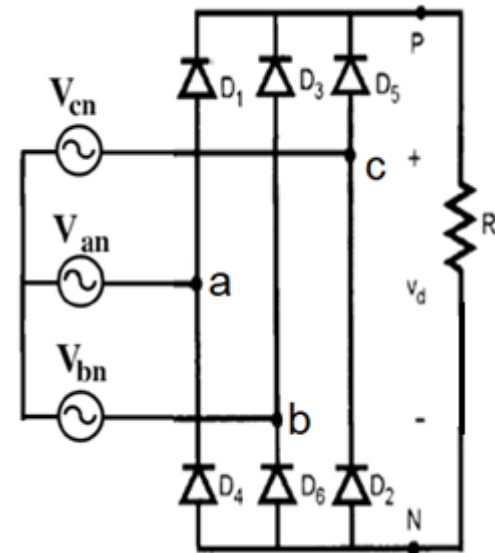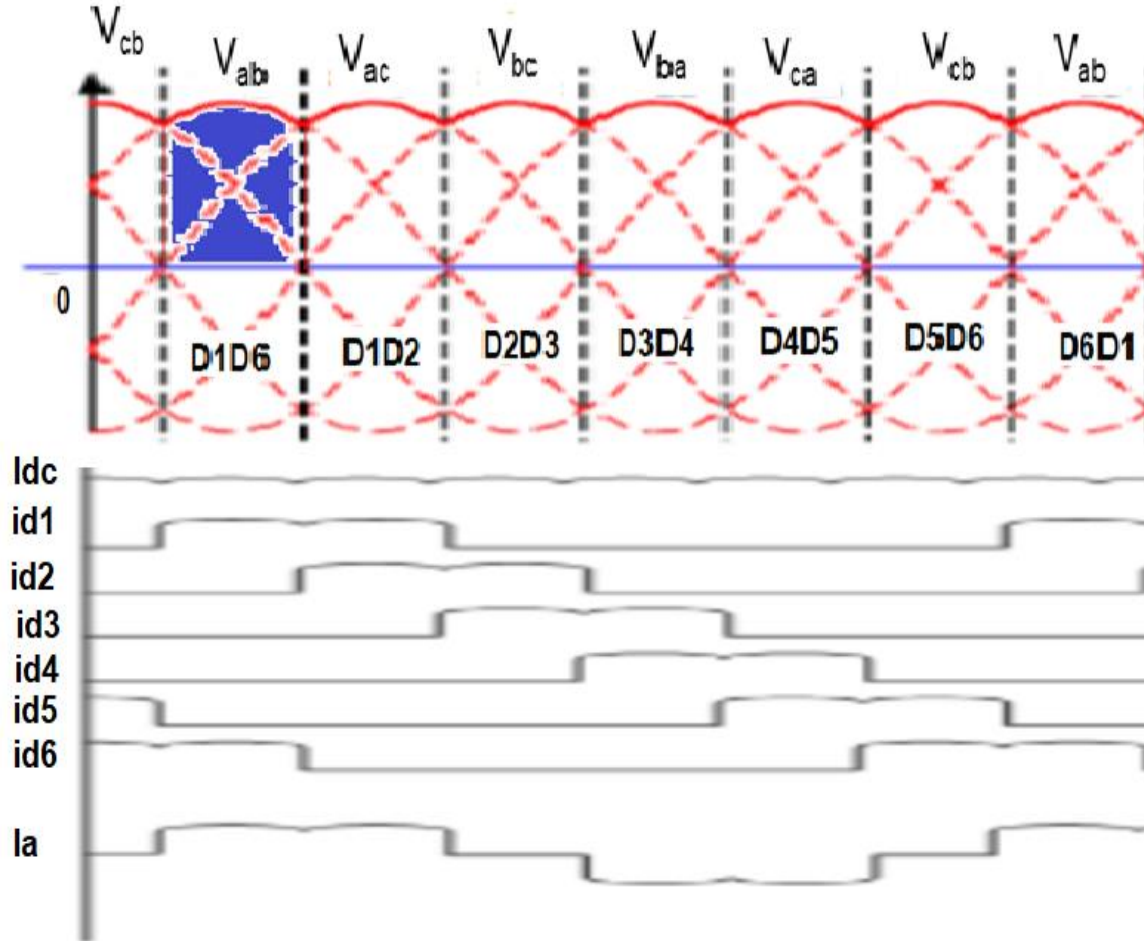3 phase full wave diode bridge with R load





3 phase full wave diode bridge

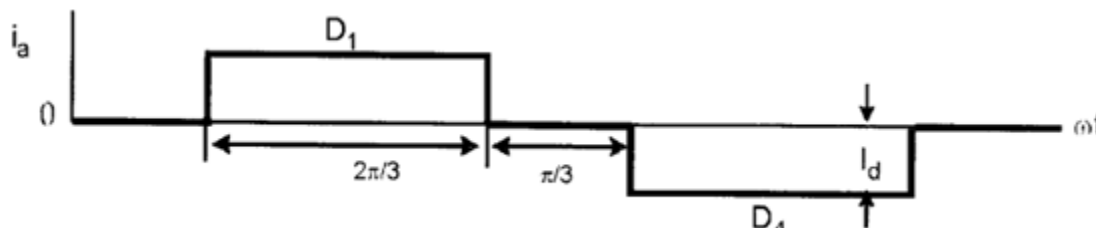
- Salient features for R and RL load
- Load current is continuous
- Each device conducts for 120°
- Names are given as per conducting sequence.
- DC voltage ripple is 4.2%
- Conducting sequence of devices: D1D2D3 D4 D5 D6
- Every pair (D1D2, **D2D3**, D3D4, **D4D5**, D5D6, **D6D1**) conducts for 60°
- Source current is quasi square wave



Diode bridge with RL load

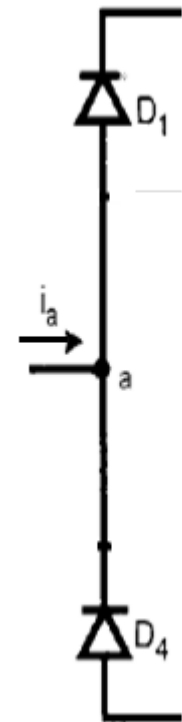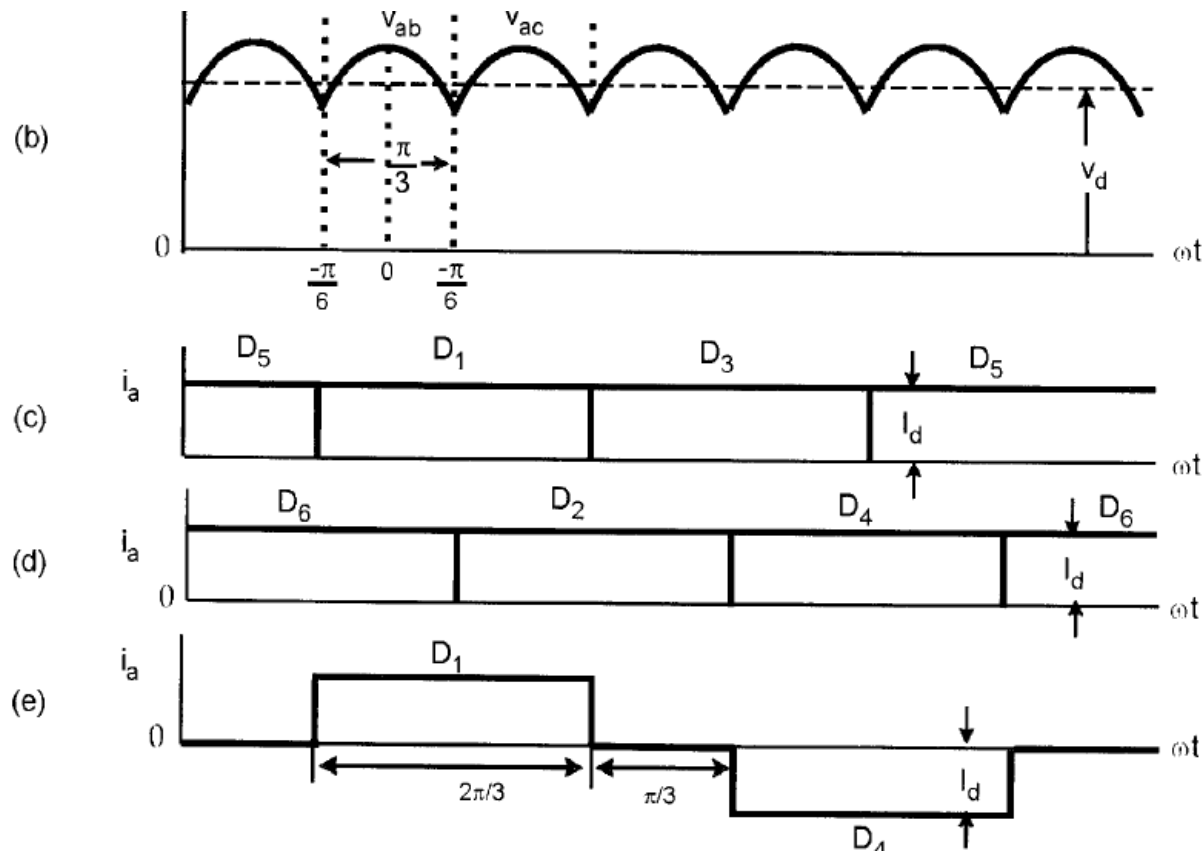

Voltage and current relationship

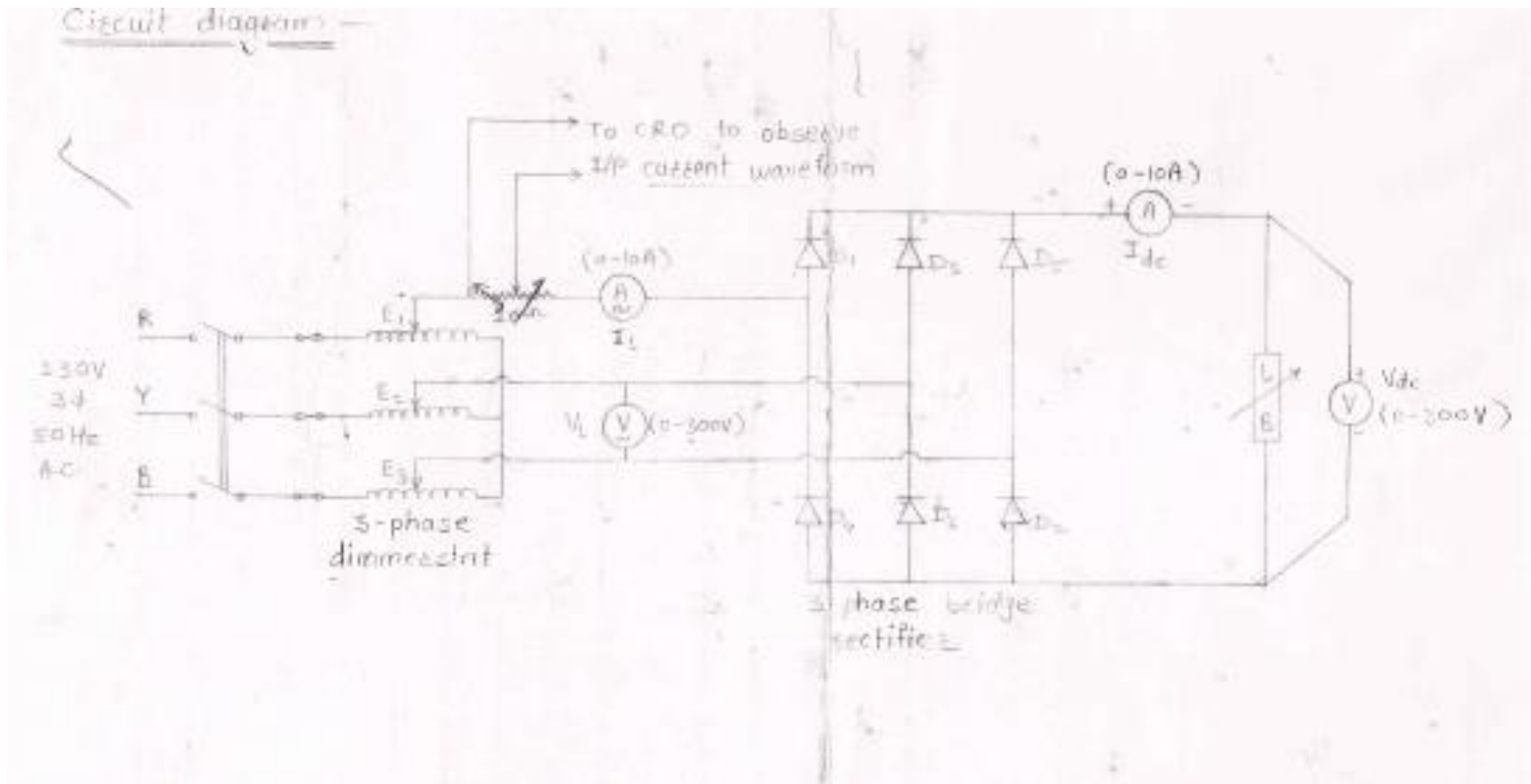

3 phase diode bridge

A) Voltage Relationship

Sr. No	Supply voltage VL	DC Output Voltage Vdc	Supply current IL	DC current Idc	Vdc/ VL	Theritical Vdc/ VL
1						
2						
3						
10						



3 phase diode bridge

B) Current Relationship

Sr. No	Supply voltage V_L	DC output Voltage V_{dc}	Supply current I_L	DC current I_{dc}	I_{dc}/I_L	Theoretical I_{dc}/I_L
1						
2						
3						
10						

3 phase diode bridge

Graphs: Draw the following graphs

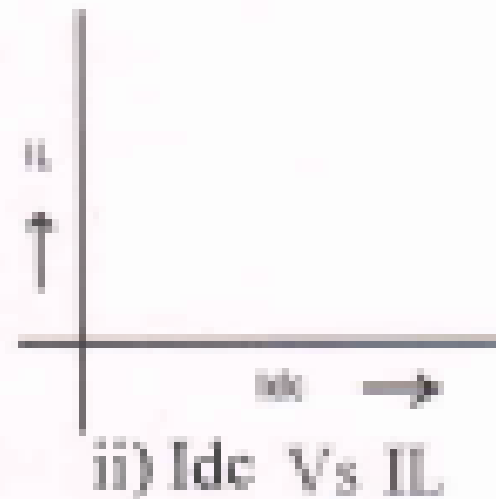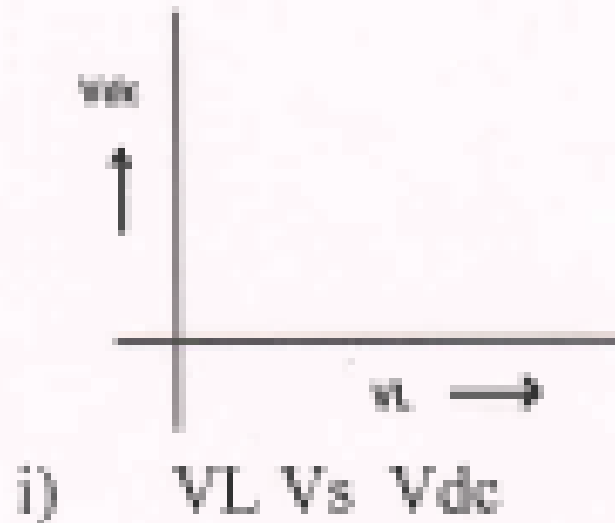


Harmonic spectrum of a waveform

■ Procedure

- Determine the RMS value of the waveform. = I
- Determine the peak amplitude of n th harmonic
- Considering quarter wave symmetry
- $$A_n = \frac{8}{2\pi} \int_0^{\pi/2} F(\theta) \cos(n\theta) d\theta$$
- Where A_n = peak amplitude of n th Harmonic.
- Determine peak amplitude of fundamental and the RMS value of fundamental = I_1
- $I^2 = I_1^2 + I_h^2$
- $\%THD = (I_h/I_1) \times 100$

Harmonic spectrum of a waveform

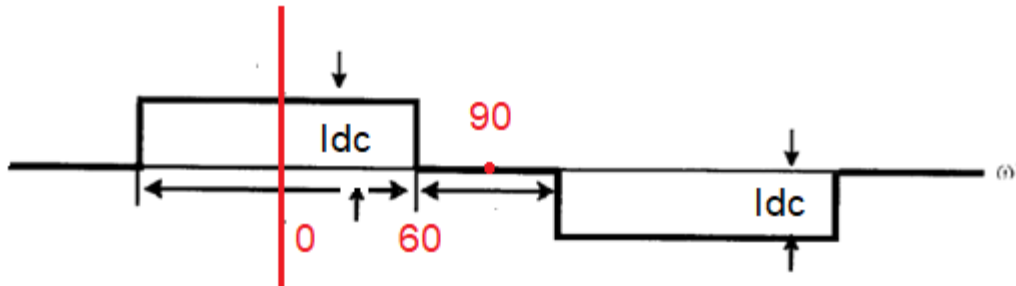- $A_n = \frac{8}{2\pi} \int_0^{\pi/2} F(\theta) \cos(n\theta) d\theta$



- $A_n = \frac{8}{2\pi} \int_0^{\pi/3} Idc \cos(n\theta) d\theta$

- $A_n = (4/n\pi) I_{dc} \sin(n\pi/3)$

- $I^2 = I_1^2 + I_h^2$

- $A_1 = \frac{2\sqrt{3}}{\pi} I_{dc} \quad I_1 = \frac{\sqrt{6}}{\pi} I_{dc}$

Harmonic spectrum of a waveform



■ I = RMS value of source current

■ $I = \sqrt{(2/3)} I_{dc}$ $I^2_h = I^2 - I_1^2$

$$\begin{aligned} I_h &= \sqrt{I^2 - I_1^2} \\ I_h &= \sqrt{\frac{2}{3} I_{dc}^2 - \frac{6}{\pi^2} I_{dc}^2} \\ I_h &= I_{dc} \sqrt{\frac{2}{3} - \frac{6}{\pi^2}} \\ I_h &= 0.24236 I_{dc} \end{aligned}$$

$$\begin{aligned} \% \text{ THD} &= \frac{I_h}{I_1} \times 100 \\ &= \frac{0.24236 I_{dc}}{\frac{\sqrt{6}}{\pi} I_{dc}} \times 100 \\ \% \text{ THD} &= 31.08\% \end{aligned}$$

Three phase diode Bridge- RL Load

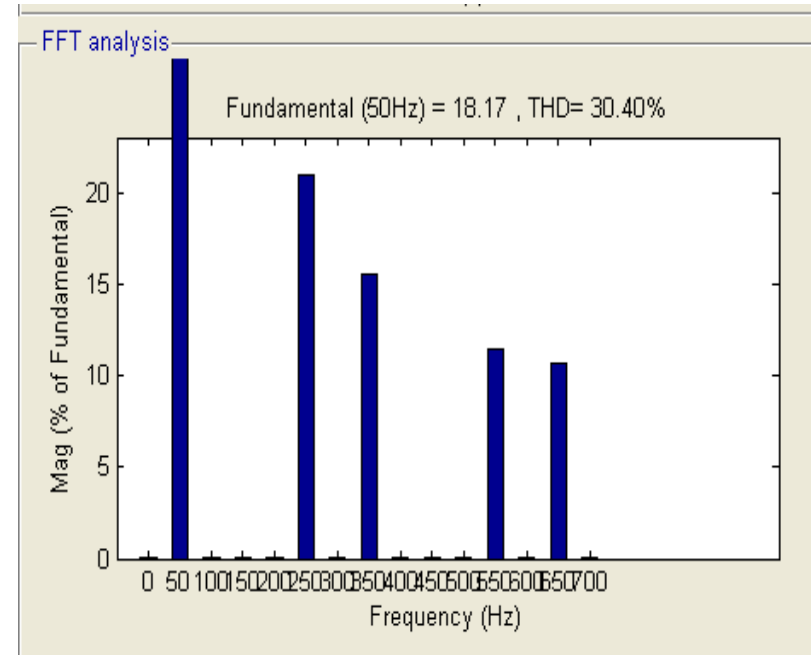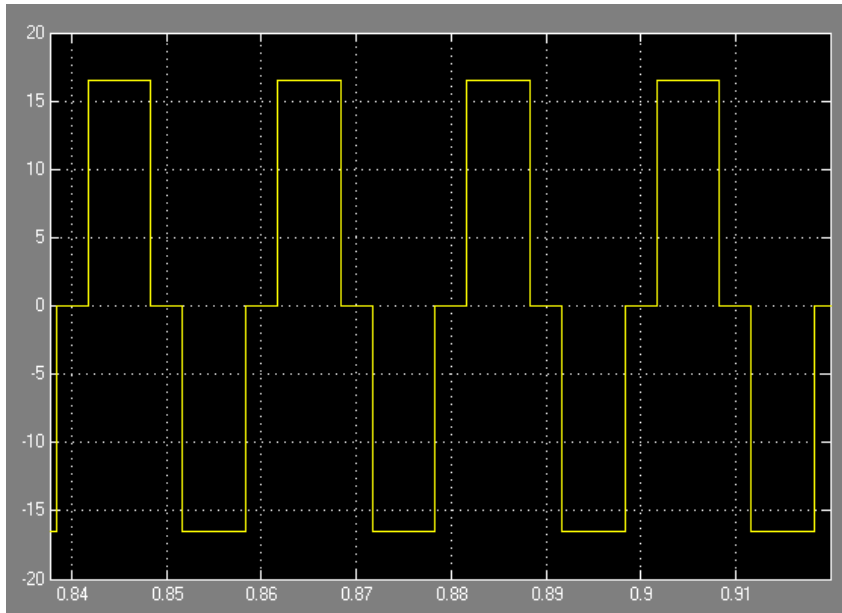


- Peak value of harmonic component
- $A_n = (4/n\pi) I_{dc} \sin(n\pi/3)$
- All odd harmonics except triplen harmonics, $(6m+1 \text{ \& } 6m-1)$

$$\%THD = (I_h / I_1) \times 100$$


THD in current = 30.40%

Three phase diode bridge -RC load

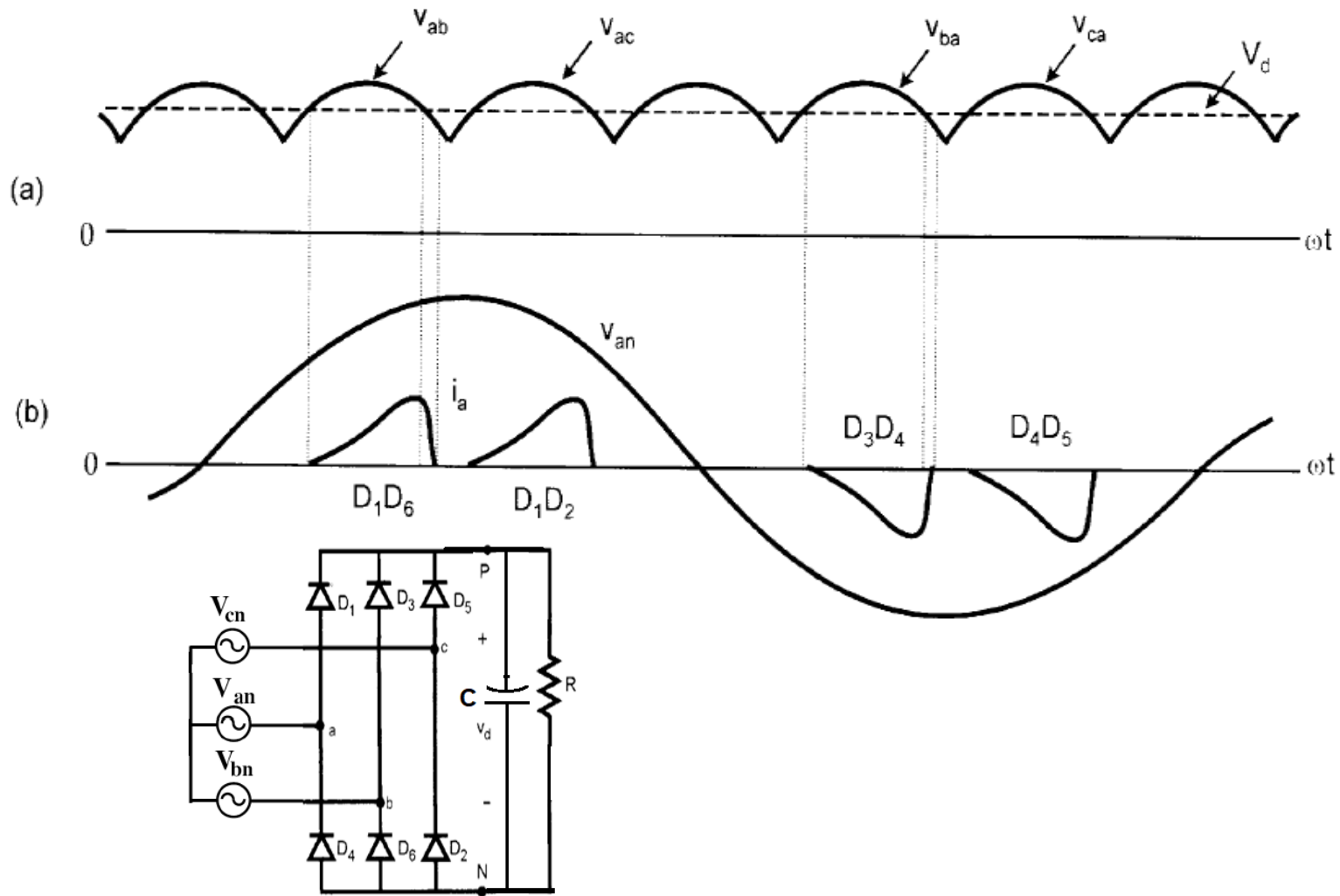



Three phase diode bridge -RC load

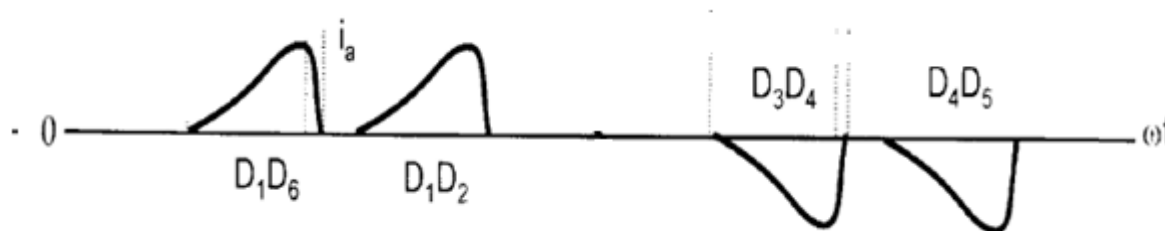- Salient features for RC load
- Capacitor is used to remove voltage ripple
- Due to capacitor voltage, conduction period of each device is less than 120°
- Every pair ($D_1D_2, D_2D_3, D_3D_4, D_4D_5, D_5D_6, D_6D_1$) conducts for less than 60°
- Source current : Harmonic spectrum is same as




Diode bridge with RC parallel load

■ Source current

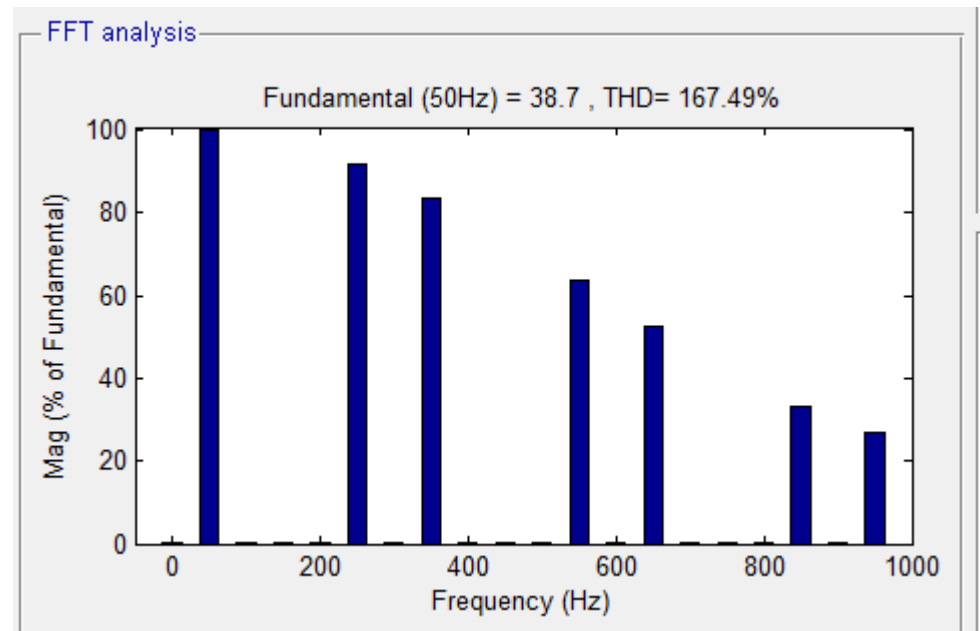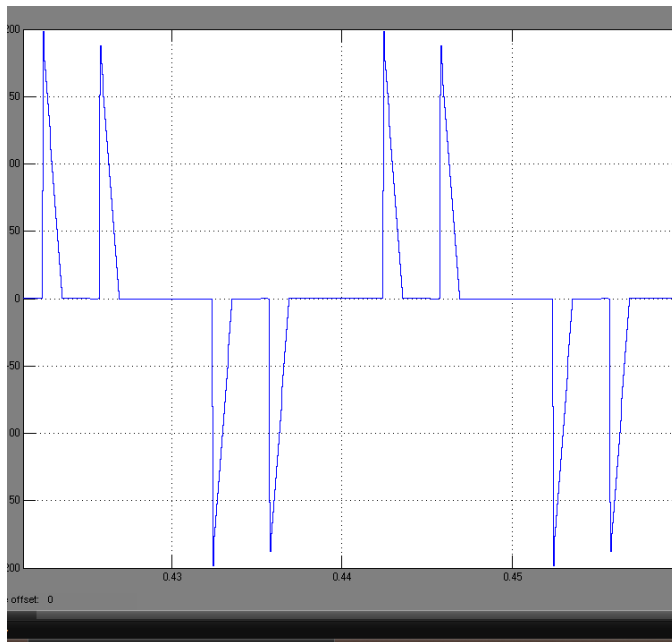

3 phase diode bridge

Transformer utilization factor

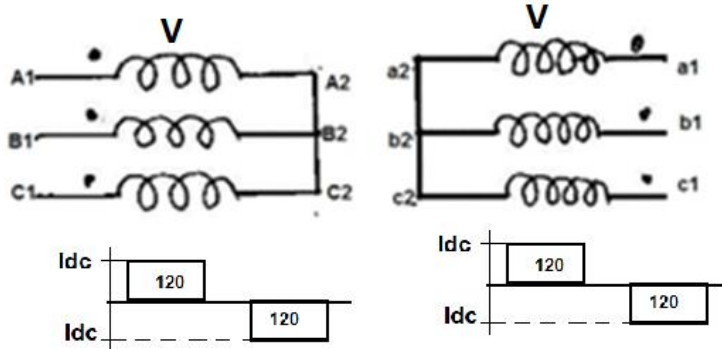

- Transformer primary and secondary currents are quasi square wave

- $$I_{dc} = \sqrt{\frac{2}{3}} I_{dc}$$


- $$V_{dc} = (3/\pi)v_{ml} = (3/\pi)\sqrt{6} V \Rightarrow V = (V_{dc} \pi)/3\sqrt{6}$$

3 phase diode bridge


- VA rating of the transformer
- $3 V I = [3 (V_{dc} \pi) / 3\sqrt{6}] \sqrt{\frac{2}{3}} I_{dc}$
- VA rating = $(\pi/3) V_{dc} I_{dc} = 1.047 V_{dc} I_{dc}$
- TUF = $(V_{dc} I_{dc}) / \text{VA rating of transformer}$
- TUF = $3/\pi = 0.954 V_{dc} I_{dc}$

Three phase controlled converter

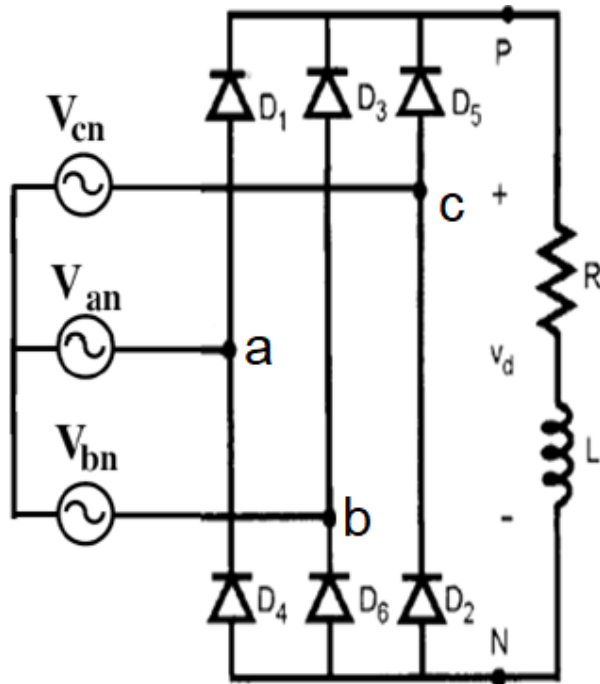- Single quadrant converter
- Uncontrolled





Controlled

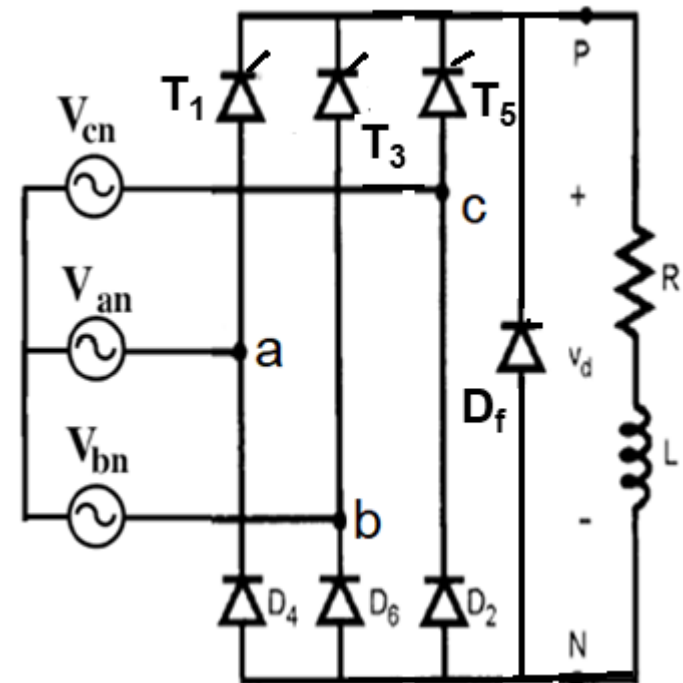

Three phase controlled converter


- Full controlled converter
- Two quadrant
- 6 pulse full controlled converter

Four quadrant
6 pulse dual converter

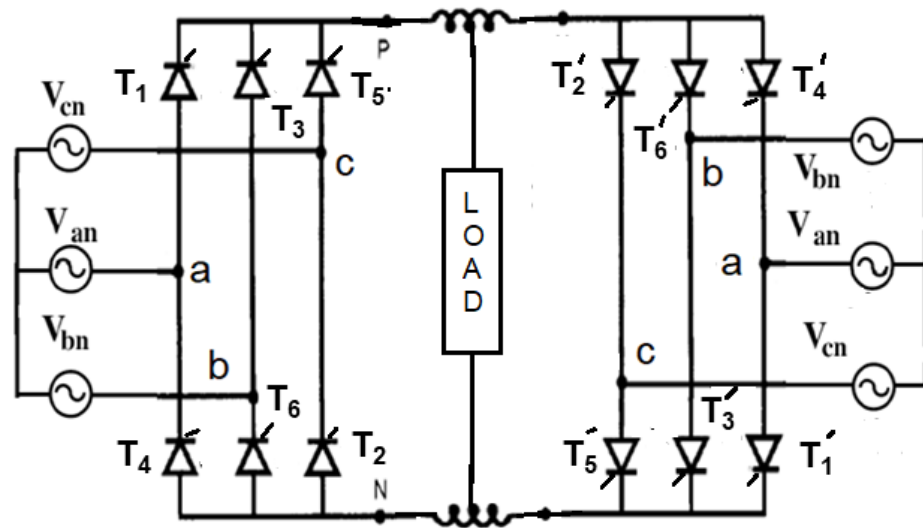
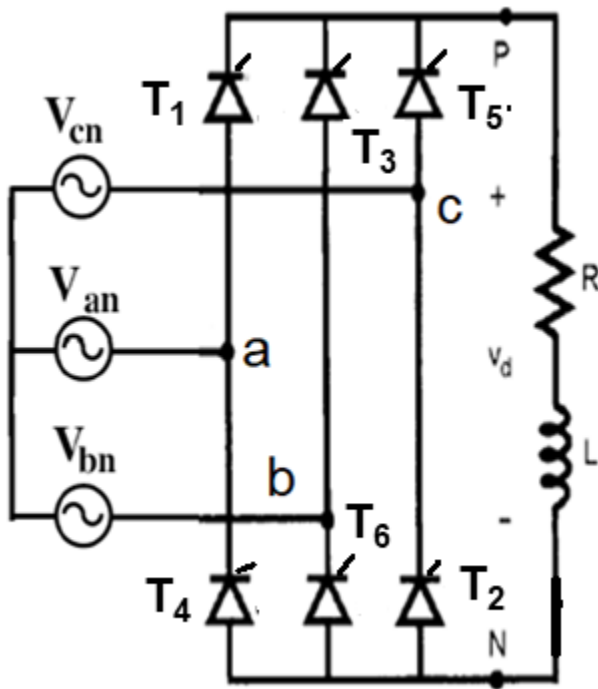


6 pulse full controlled converter

■ From where to measure α


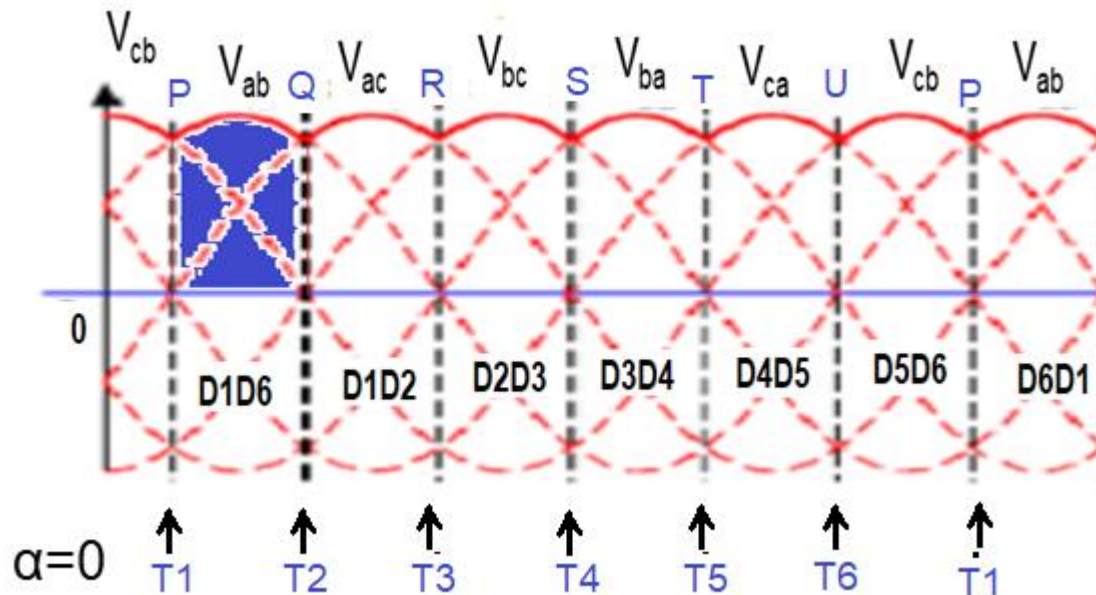


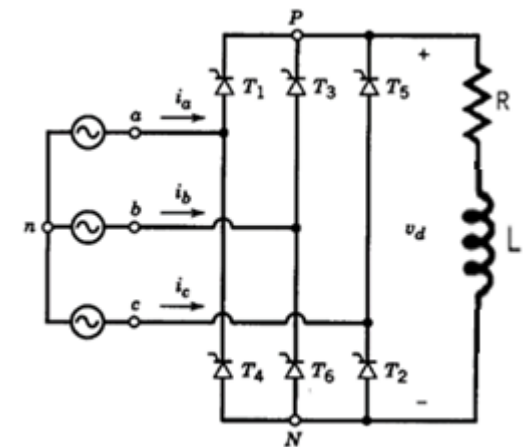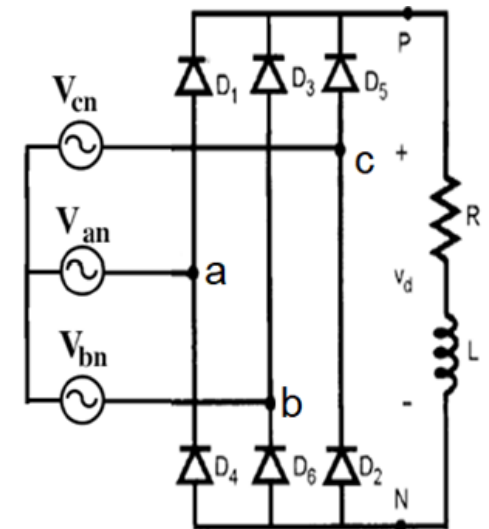■ What is voltage waveform of 6 pulse full controlled converter when $\alpha=0$




6 pulse full controlled converter RL load

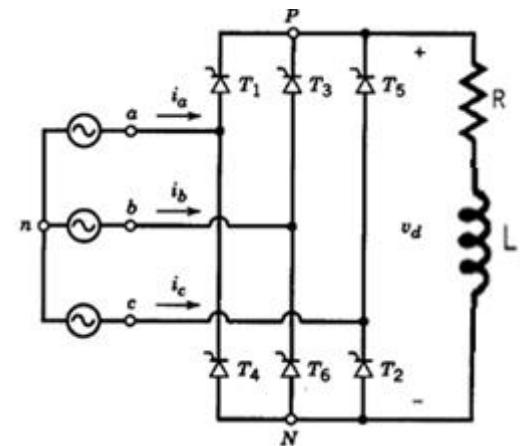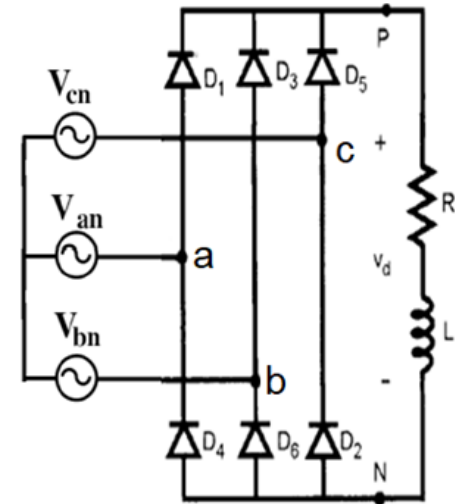- ❑ Firing angle = 0 \Rightarrow Three phase diode bridge
- ❑ Range of Firing angle $\Rightarrow 0$ to 180°
- ❑ Each device conducts for 120°
- ❑ Converter and Inverter operation
- ❑ Positive source current for 120° degree and negative current for 120° degree $\pi/3$



6 pulse converter O/P voltage waveform



■ $\alpha = 30^\circ$

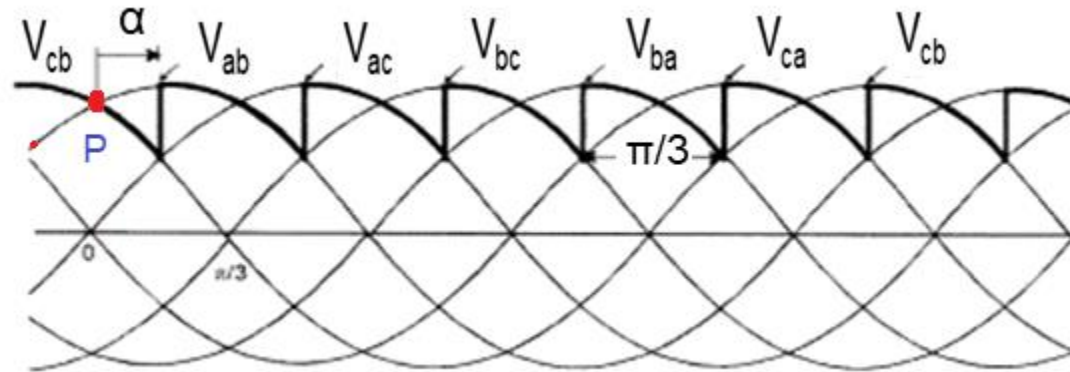

- Draw three line voltages and inverted line voltages
- Determine position of $\alpha=0$
- Mark the α on the line voltage
- Trace the same waveform for next 60°



6 pulse converter with RL Load

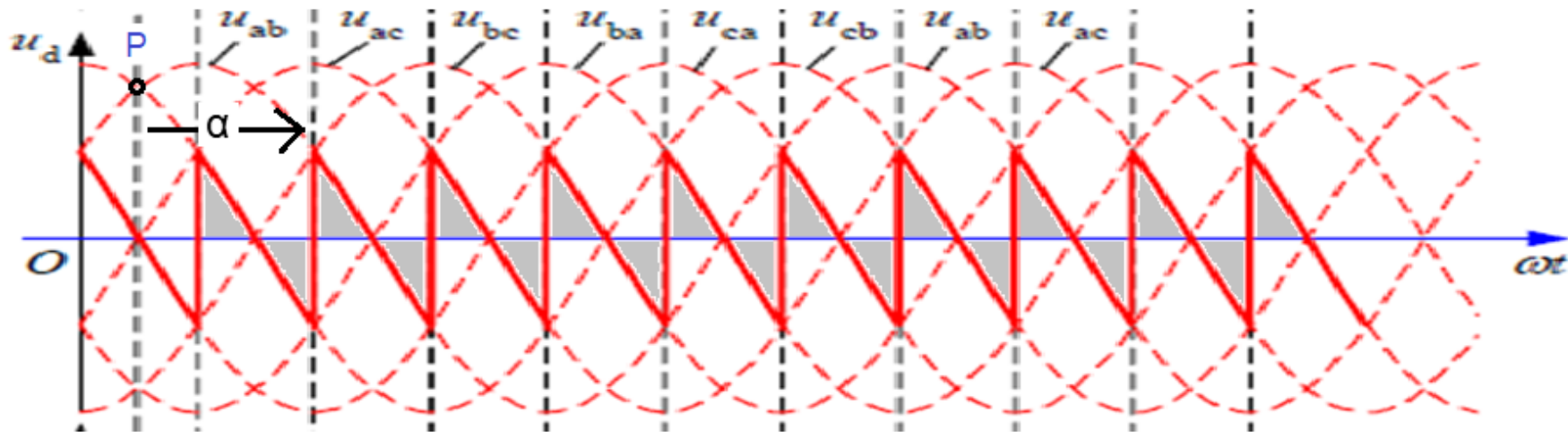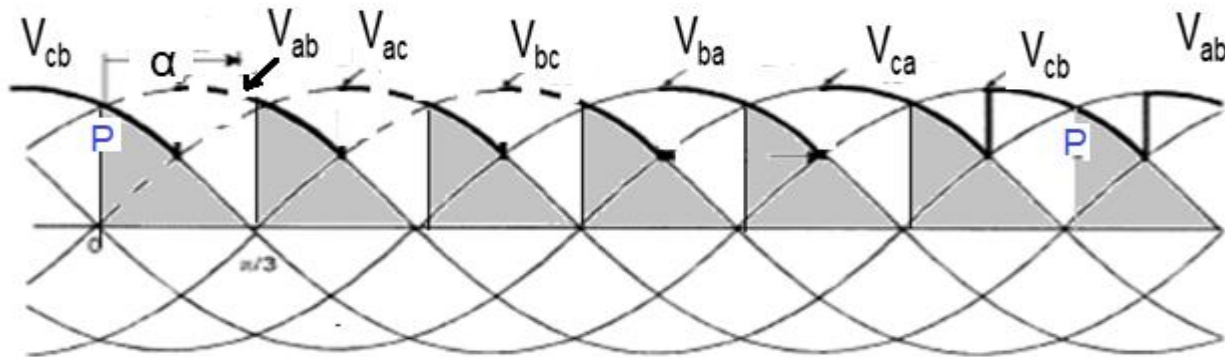- I) $\alpha = 60^\circ$ and $\alpha = 90^\circ$



6 pulse converter with RL Load

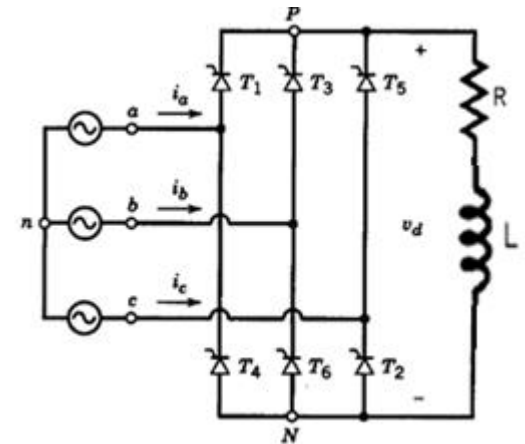
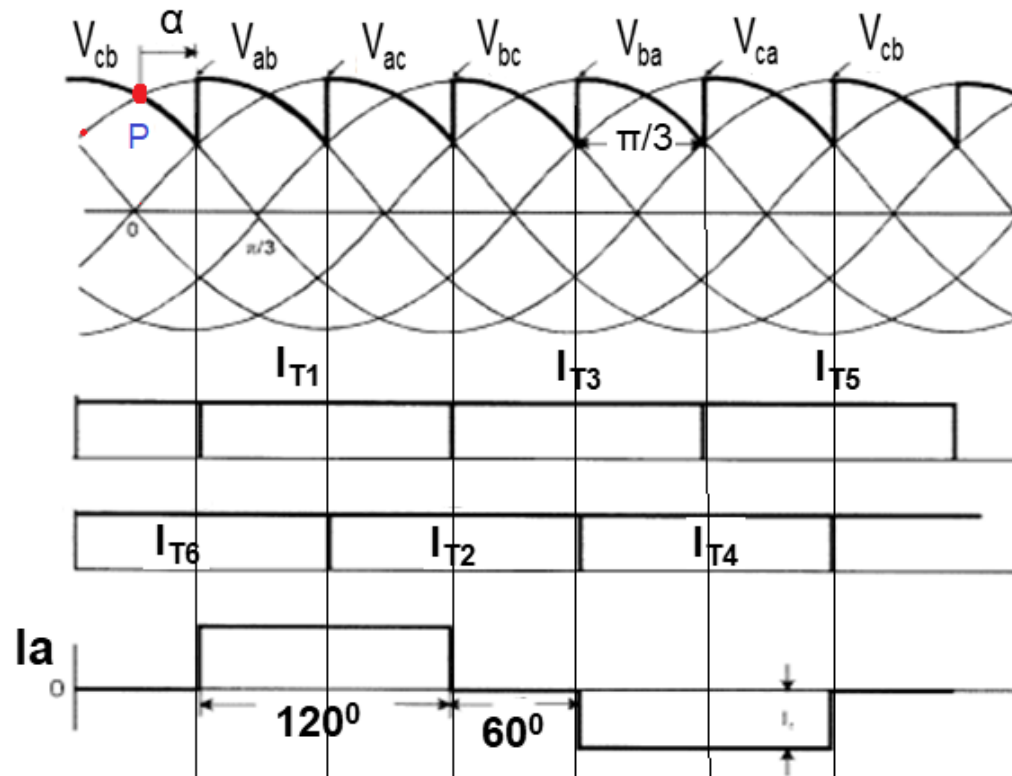
Output voltage and source current waveforms at $\alpha=30^\circ$ degree



Current THD
is same as
diode bridge
THD= 30.40%


6 pulse converter with RL Load

- firing angle $\alpha=120^\circ$

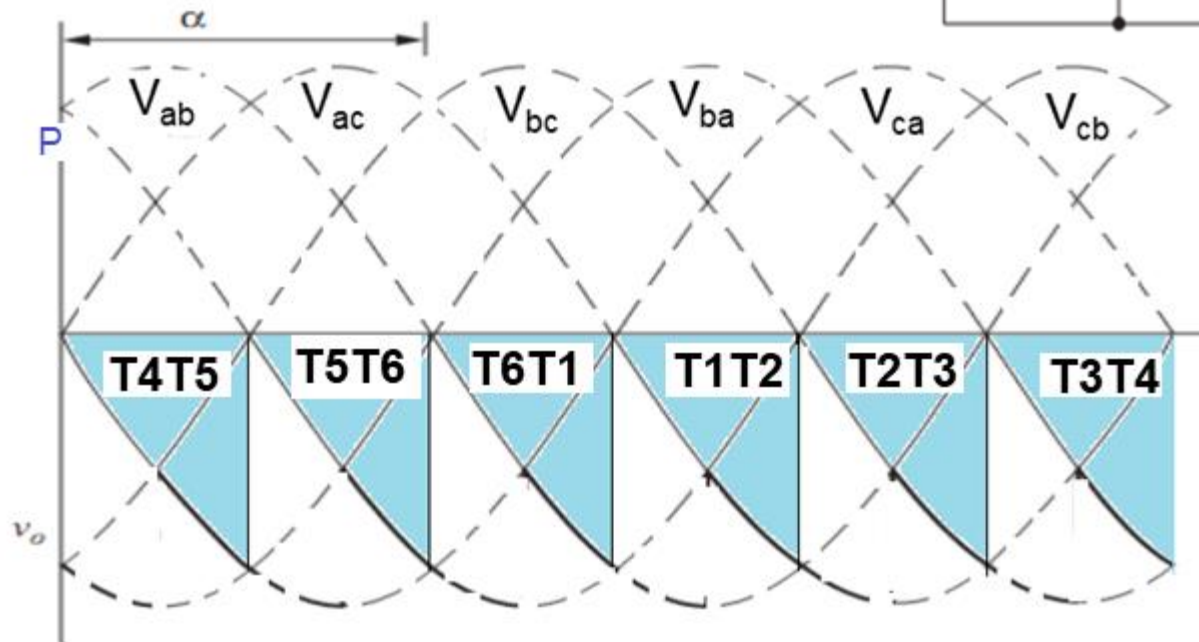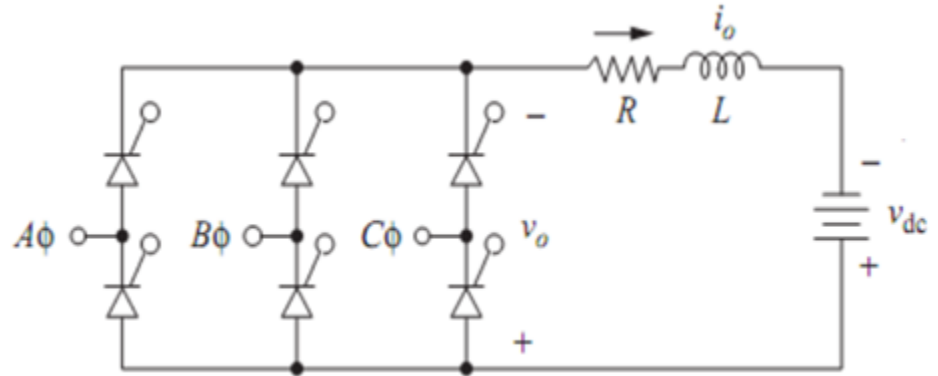


6 pulse converter with RL Load

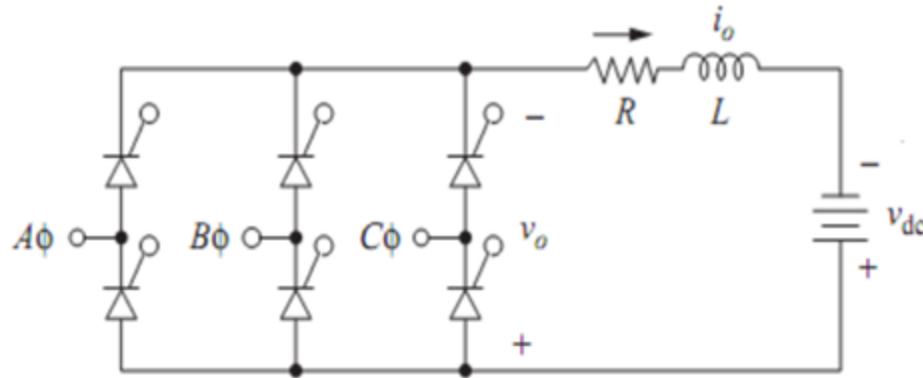- Inverter operation : $\alpha = 150^\circ$




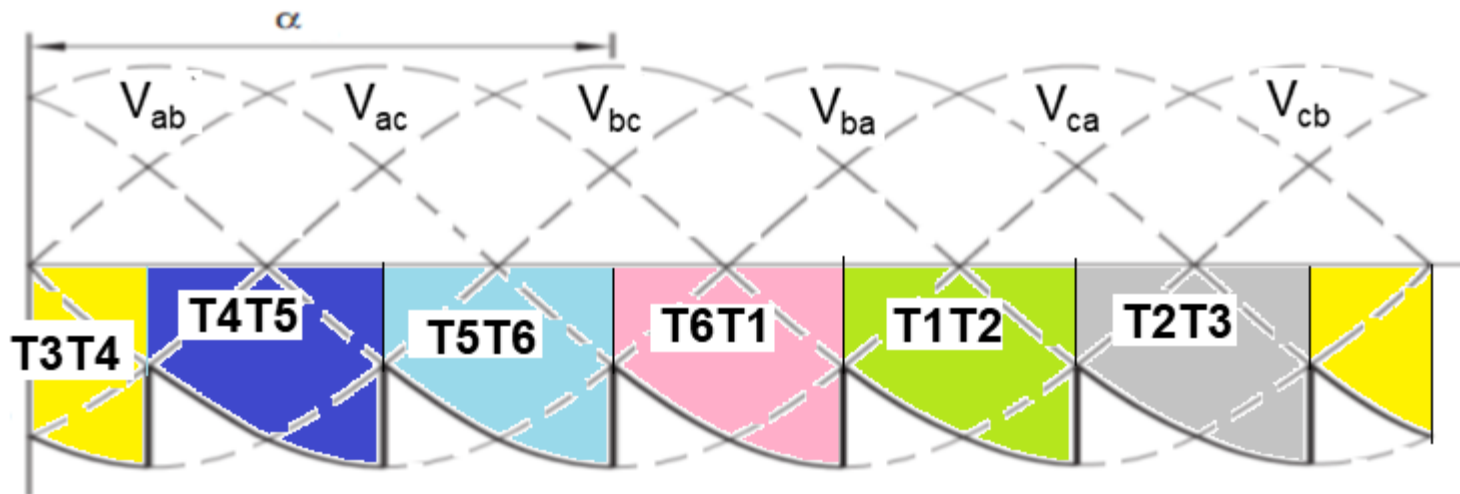Wave shape of source current remains same for rectifier and inverter operation



6 pulse converter with RL Load

■ DC O/P voltage

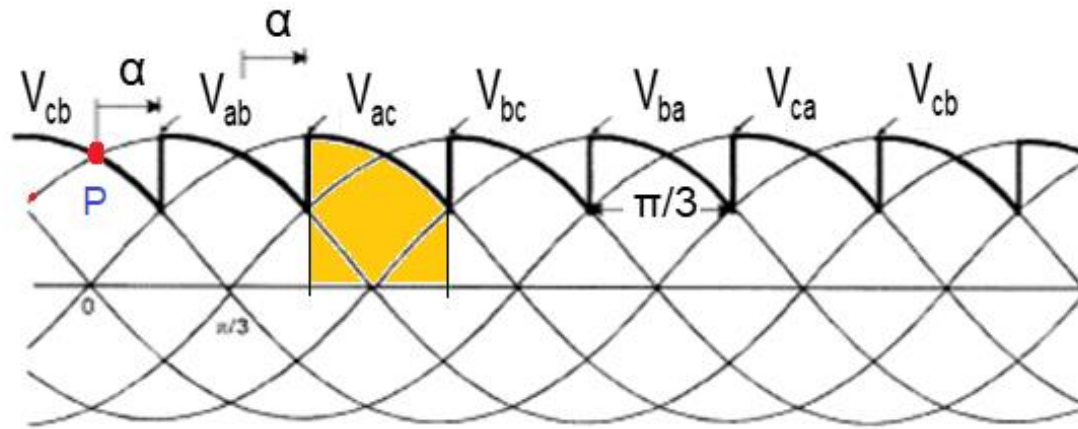

- $V_{dc(av)} = \frac{6}{2\pi} \int_{60+\alpha}^{120+\alpha} V_{ml} \sin\theta d\theta$
- V_{ml} is peak value of line voltage

6 pulse converter with RL Load

$$V_{dc(av)} = \frac{6}{2\pi} \int_{60+\alpha}^{120+\alpha} V_{ml} \sin \theta \cdot d\theta$$

$$V_{dc(av)} = \frac{3V_{ml}}{\pi} \int_{60+\alpha}^{120+\alpha} \sin \theta \cdot d\theta$$

$$V_{dc(av)} = \frac{3V_{ml}}{\pi} [-\cos \theta] \bigg|_{60+\alpha}^{120+\alpha}$$

$$V_{dc(av)} = \frac{3V_{ml}}{\pi} [-\cos(120+\alpha) + \cos(60+\alpha)]$$

$$V_{dc(av)} = \frac{3V_{ml}}{\pi} [(-\cos 120 \cdot \cos \alpha + \sin 120 \cdot \sin \alpha) + (\cos 60 \cdot \cos \alpha - \sin 60 \sin \alpha)]$$

6 pulse converter with RL Load

$$V_{dc(av)} = \frac{3V_{mL}}{\pi} \left[(-\cos 120 \cdot \cos \alpha + \sin 120 \cdot \sin \alpha) + (\cos 60 \cdot \cos \alpha - \sin 60 \sin \alpha) \right]$$


$$V_{dc(av)} = \frac{3V_{mL}}{\pi} \left[-\cos 120 \cos \alpha + \cos 60 \cos \alpha \right]$$

$$V_{dc(av)} = \frac{3V_{mL}}{\pi} \left[0.5 \cos \alpha + 0.5 \cos \alpha \right]$$

$$V_{dc(av)} = \frac{3V_{mL}}{\pi} \cos \alpha$$


6 pulse converter with RL Load

■ Rectifier and Inverter operation

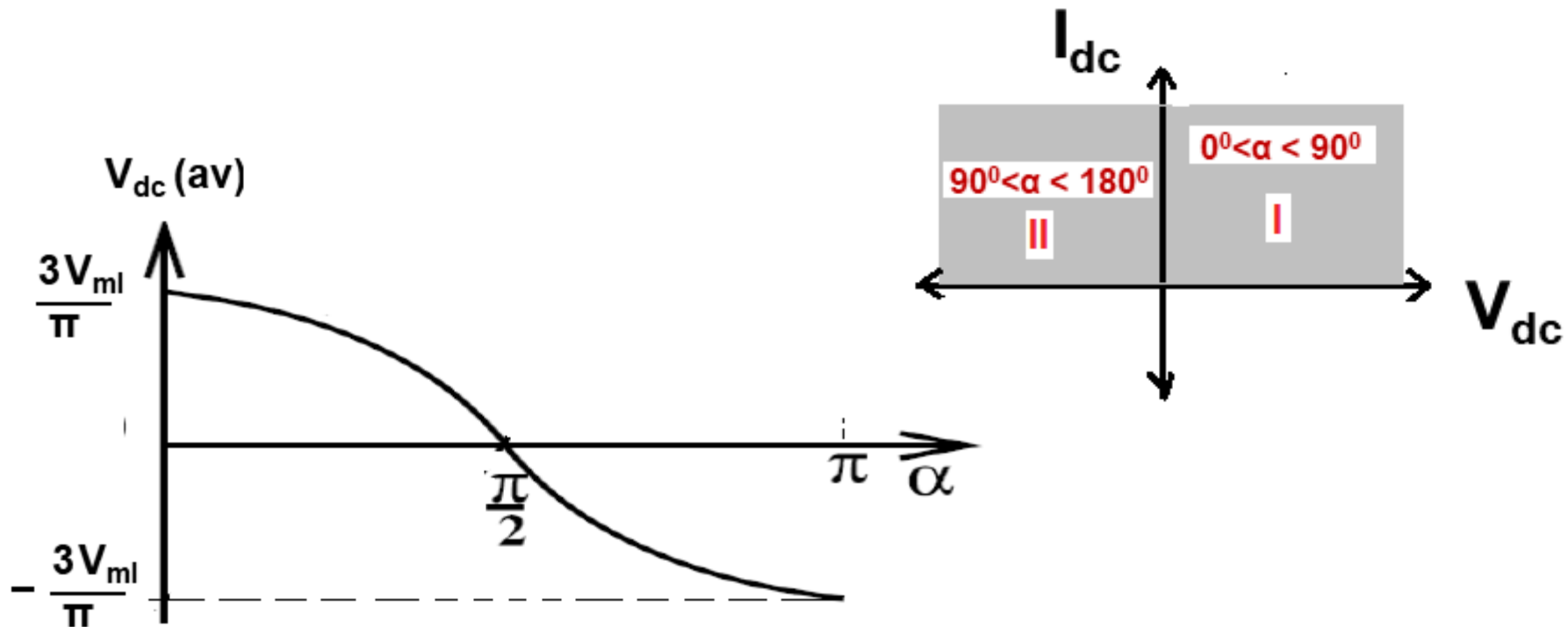

Harmonic spectrum of a waveform

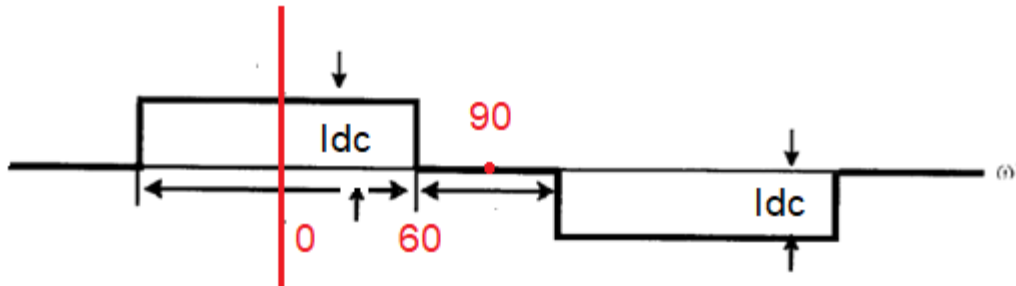- $A_n = \frac{8}{2\pi} \int_0^{\pi/2} F(\theta) \cos(n\theta) d\theta$



- $A_n = \frac{8}{2\pi} \int_0^{\pi/3} Idc \cos(n\theta) d\theta$

- $A_n = (4/n\pi) I_{dc} \sin(n\pi/3)$

- $I^2 = I_1^2 + I_h^2$

- $A_1 = \frac{2\sqrt{3}}{\pi} I_{dc} \quad I_1 = \frac{\sqrt{6}}{\pi} I_{dc}$

Harmonic spectrum of a waveform

■ I = RMS value of source current



■ $I = \sqrt{(2/3)} I_{dc}$ $I^2_h = I^2 - I_1^2$

$$\begin{aligned} I_h &= \sqrt{I^2 - I_1^2} \\ I_h &= \sqrt{\frac{2}{3} I_{dc}^2 - \frac{6}{\pi^2} I_{dc}^2} \\ I_h &= I_{dc} \sqrt{\frac{2}{3} - \frac{6}{\pi^2}} \\ I_h &= 0.24236 I_{dc} \end{aligned}$$

$$\begin{aligned} \% \text{ THD} &= \frac{I_h}{I_1} \times 100 \\ &= \frac{0.24236 I_{dc}}{\frac{\sqrt{6}}{\pi} I_{dc}} \times 100 \\ \% \text{ THD} &= 31.08\% \end{aligned}$$

6 pulse converter with RL Load

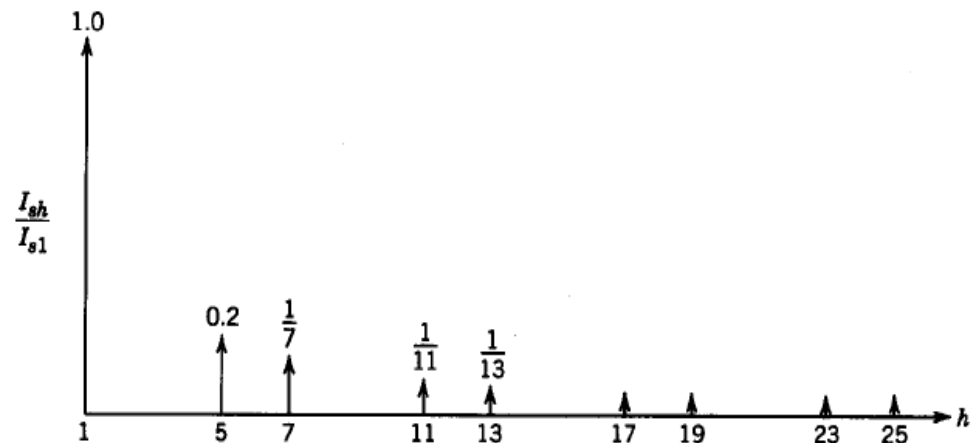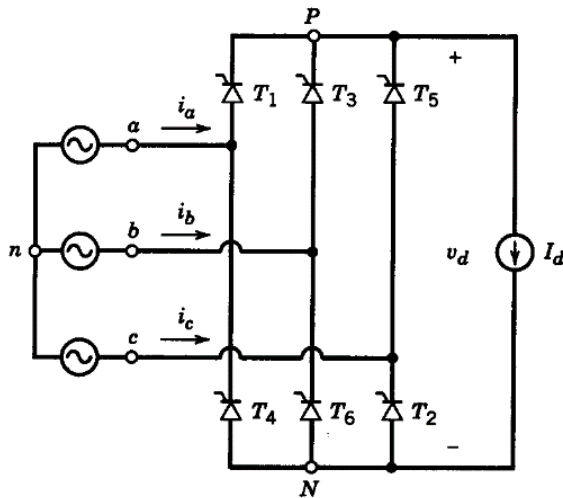
- Each device conducts for 120 degree.
- Positive source current for 120 degree and negative current for 120 degree
- harmonic spectrum $6m+1$ and $6m-1$ harmonics
-



6 pulse converter with RL Load


Important Features

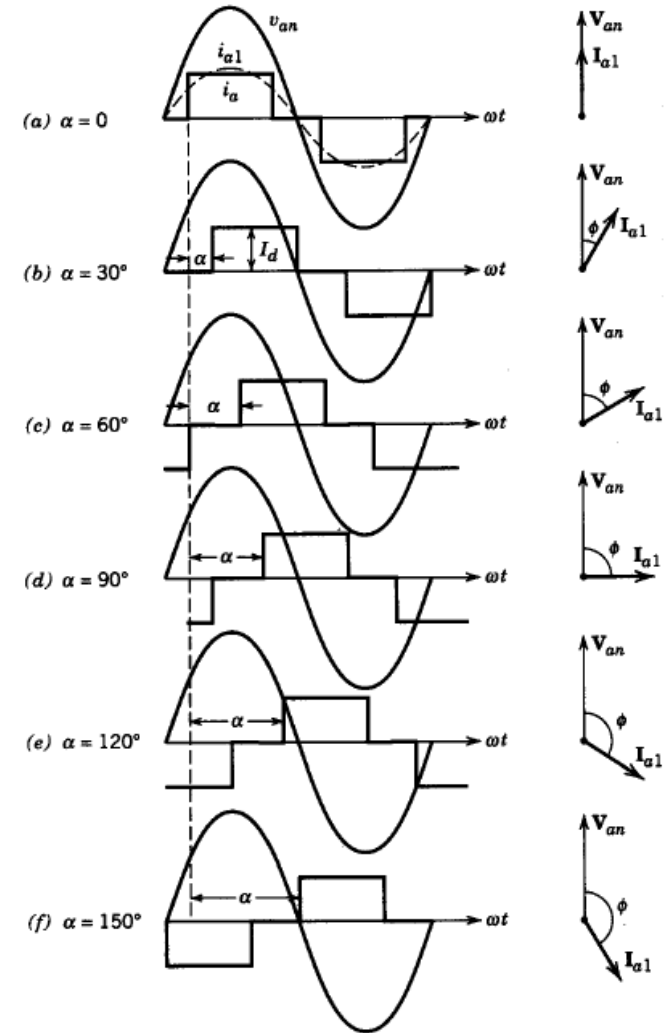- Harmonic spectrum remains Same
- Fundamental component of source current lags the voltage by an angle α
- Requires lagging reactive power
- $PF = (3/\pi) \cos\alpha$



6 pulse converter with RL Load

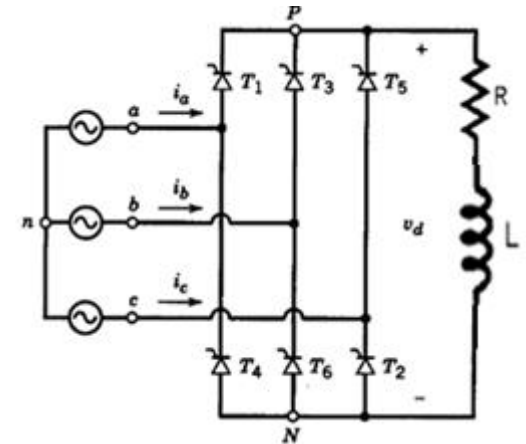- Numerical problem => Rectifier operation
- 6 pulse converter supplied from 400 V 3 ϕ 50 Hz
- RL load => $R=50\ \Omega$ and L is very large
- $\alpha = 30^\circ$ determine
- i) dc O/P voltage & DC current
- ii) Power dissipated in R load
- iii) Source current and supply pf
- iv) rms value of fundamental component of source current
- V) Active and reactive power supplied from the source



Numerical problem: RL load

$$V_{dc(av)} = \frac{3V_{ml}}{\pi} \cos \alpha = \frac{3 \times \sqrt{2} \times 400}{\pi} \cos 30^\circ$$

$$V_{dc(av)} = 467.818 \text{ V}$$

$$I_{dc} = V_{dc(av)} / R = \frac{467.818}{50} = 9.356 \text{ A}$$

$$\begin{aligned} \text{Power dissipated in } R &= V_{dc(av)} \cdot I_{dc(av)} \\ &= 4377.07 \text{ W.} \end{aligned}$$

$$\text{Source current } I_s = \sqrt{\frac{2}{3}} \cdot I_{dc} = 7.639 \text{ A}$$

$$\text{Supply Pf} = \frac{3}{\pi} \cos \alpha = 0.826 \text{ lag.}$$

Numerical Problem: RL load

$$\text{Peak value of fund. comp} = \frac{2\sqrt{3}}{\pi} I_{dc}$$

$$\text{RMS value of funda. component} = \frac{\sqrt{6}}{\pi} I_{dc}$$

$$I_1 = 7.2948 \text{ A}$$

$$\text{Active Power} = \sqrt{3} V_L I_L \cos \phi$$

$$= \sqrt{3} \times 400 \times 7.639 \times 0.826$$

$$= 4371 \text{ W}$$

$$\text{Reactive Power} = \sqrt{3} V_L I_L \sin \phi$$

$$= \sqrt{3} \times 400 \times 7.639 \times \sin(34.309)$$

$$= 2983.12 \text{ VAR}$$