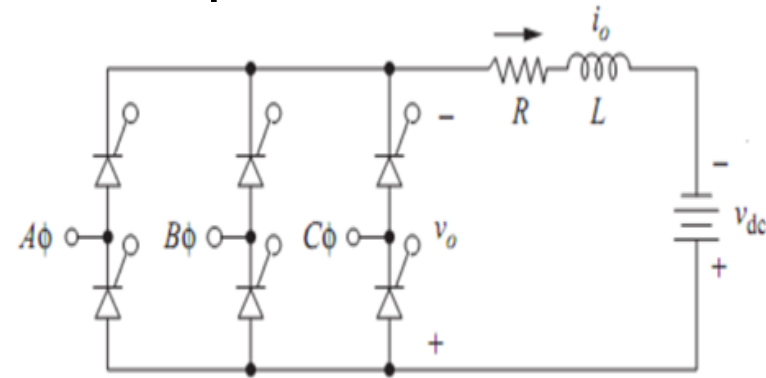


6 pulse converter with RLE Load

- Numerical problem => Inverter operation
- 6 pulse converter supplied from 400 V 3 ϕ 50 Hz
- RLE load => $R=10\ \Omega$ and
- L is very large & $E=450\text{ V}$
- $\alpha = 120^\circ$ determine
- i) converter O/P voltage
- & DC current supplied by the battery
- ii) Power dissipated in R load
- iii) Source current and supply pf
- iv) active power provided by the battery
- V) Reactive power supplied from the source



Numerical problem: RLE load

$$V_{dc(av)} = \frac{3V_{ml}}{\pi} \cos \alpha = \frac{3 \times \sqrt{2} \times 400}{\pi} \cos 120$$

$$\therefore V_{dc(av)} = -270.09 \text{ V} = -270.09 \text{ V}$$

$$I_{dc} = \frac{E - V_{dc(av)}}{R} = \frac{450 - 270.09}{10} = 17.99 \text{ A}$$

$$\begin{aligned} \text{Power dissipated in R load} &= I_{dc}^2 \cdot R \\ &= (17.99)^2 \times 10 = 3236.76 \text{ W} \end{aligned}$$

$$\begin{aligned} \text{source current } I_s &= \sqrt{\frac{2}{3}} \cdot I_{dc} = \sqrt{\frac{2}{3}} \times 17.99 \\ &= 14.688 \text{ A} \end{aligned}$$

Numerical problem: RLE load

$$\text{Supply PF} = \frac{3}{\pi} \cos \alpha = \frac{3}{\pi} \cos(120^\circ) = 0.477 \text{ lag}$$

Active Power provided by Battery


$$\begin{aligned} &= E \times I_{dc} = 450 \times 17.99 \\ &= 8095.5 \text{ W} \end{aligned}$$

$$\therefore \text{Reactive Power} = \sqrt{3} \cdot V_L \cdot I_L \sin \phi$$

$$\begin{aligned} &= \sqrt{3} \times 400 \times 14.688 \times \sin(61.51^\circ) \\ &= 8943.81 \text{ VAR} \end{aligned}$$


6 pulse converter with R Load

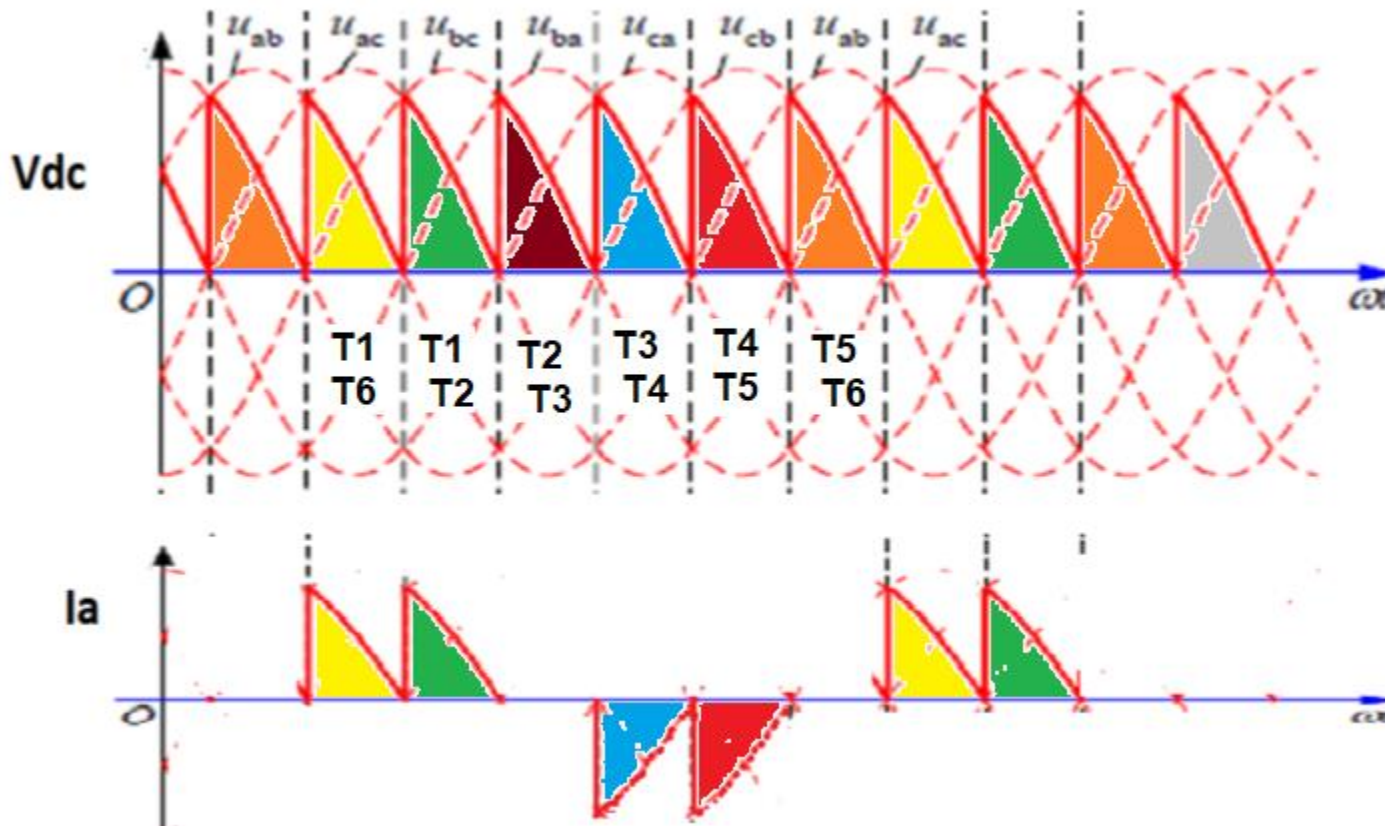- continuous conduction $\Rightarrow 0^\circ < \alpha < 60^\circ$
- discontinuous conduction $\Rightarrow 60^\circ < \alpha < 120^\circ$
- Firing angle : $\alpha = 60^\circ$




6 pulse converter with R Load



- Firing angle : $\alpha = 90^\circ$

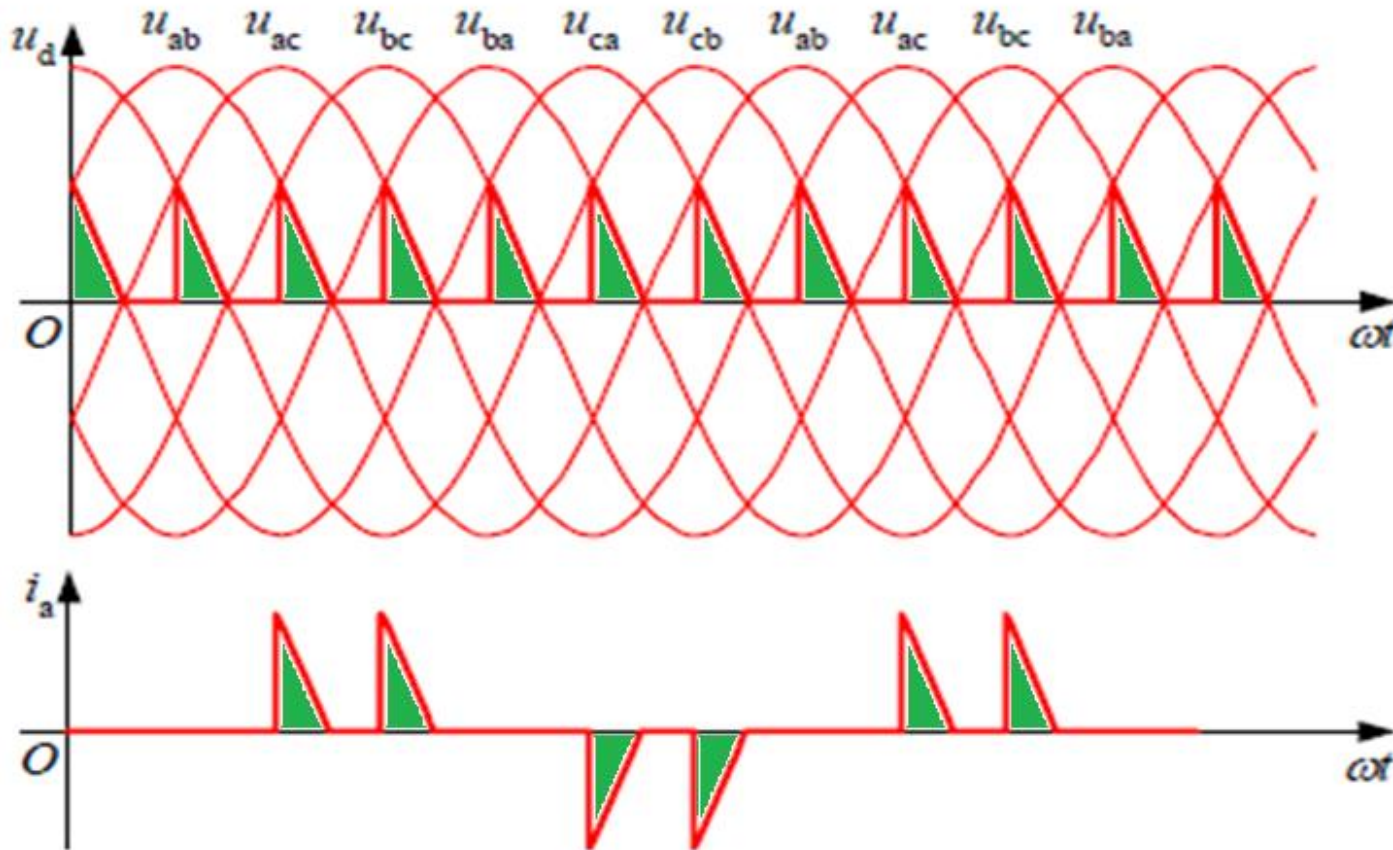

Gating signal for 6 pulse converter


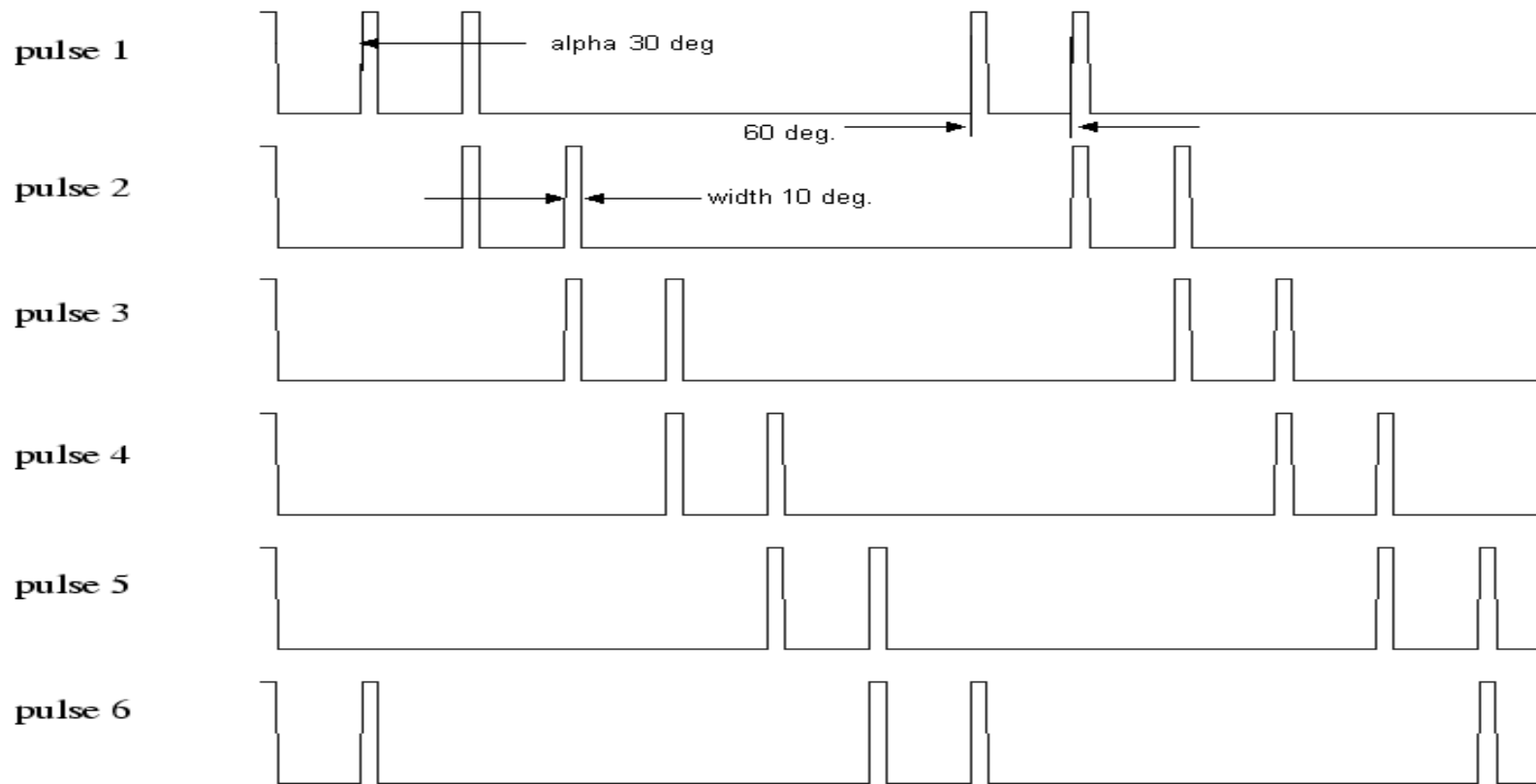


Gate trigger signal – 6 pulse converter

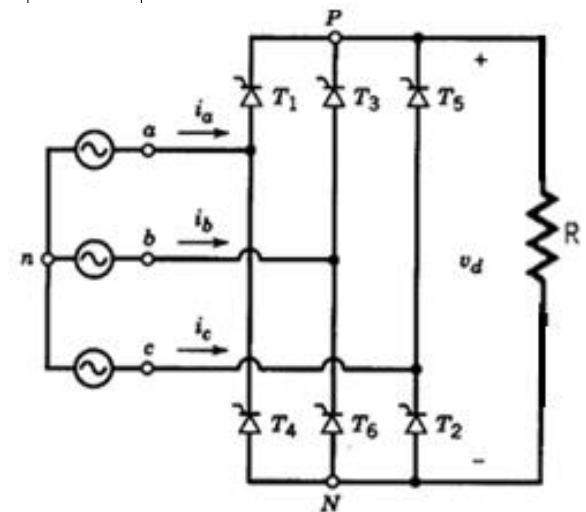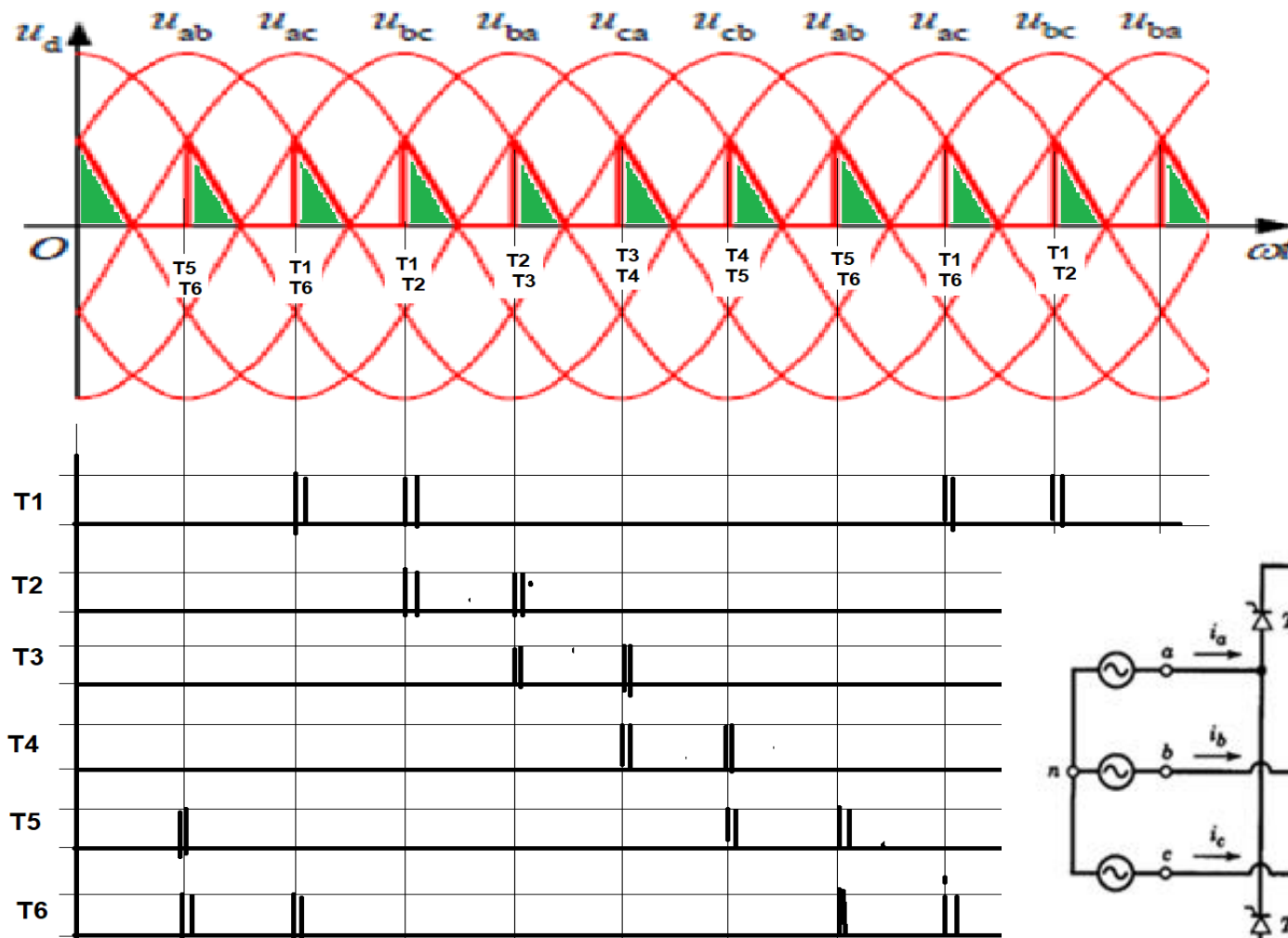

6 pulse converter with R Load

Firing angle = 90 degree

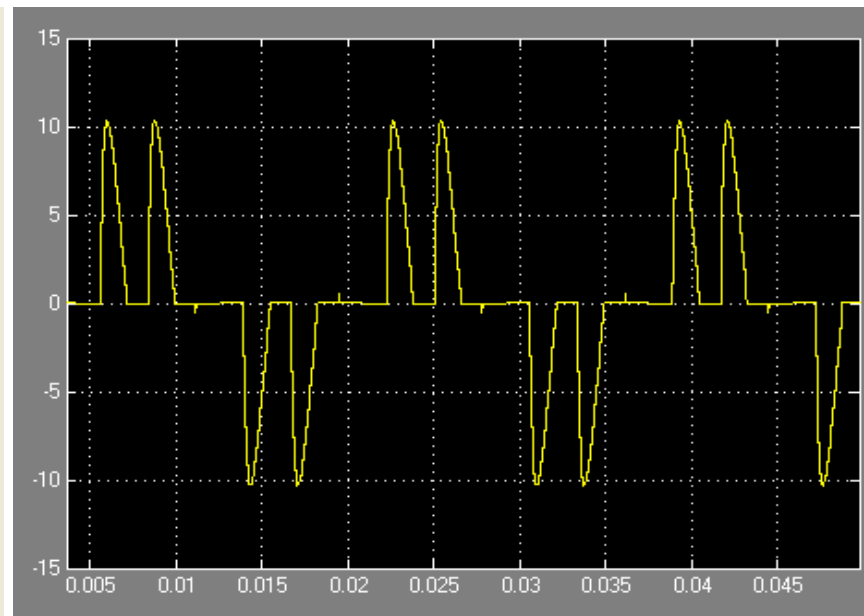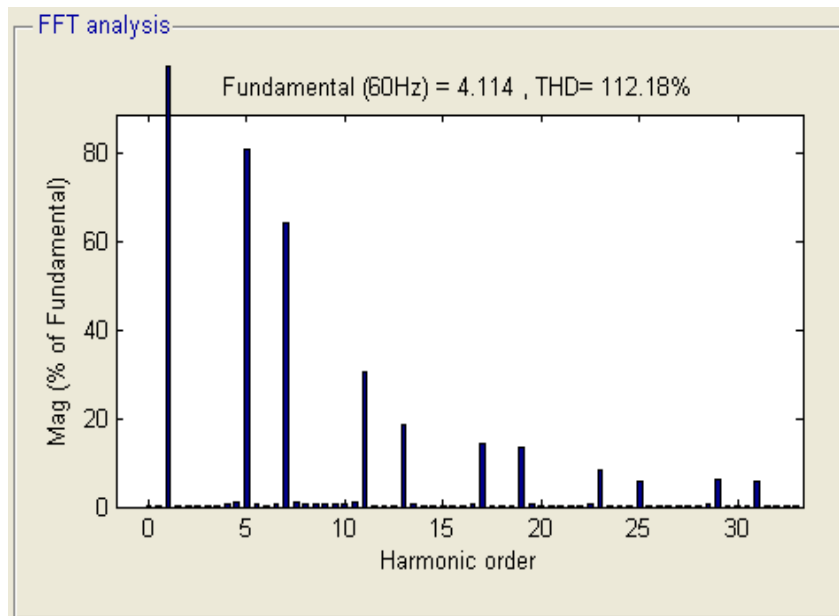

Range of $\alpha \Rightarrow 0$ to 120°


Continuous conduction $\Rightarrow \alpha < 60^\circ$

~~discontinuous conduction $\Rightarrow \alpha > 60^\circ$~~

$$I_h = \sqrt{I_5^2 + I_7^2 + I_{11}^2 + I_{13}^2 + \dots}$$
$$= \sqrt{\sum_{n=5,7,\dots} I_n^2}$$

6 pulse converter with R Load


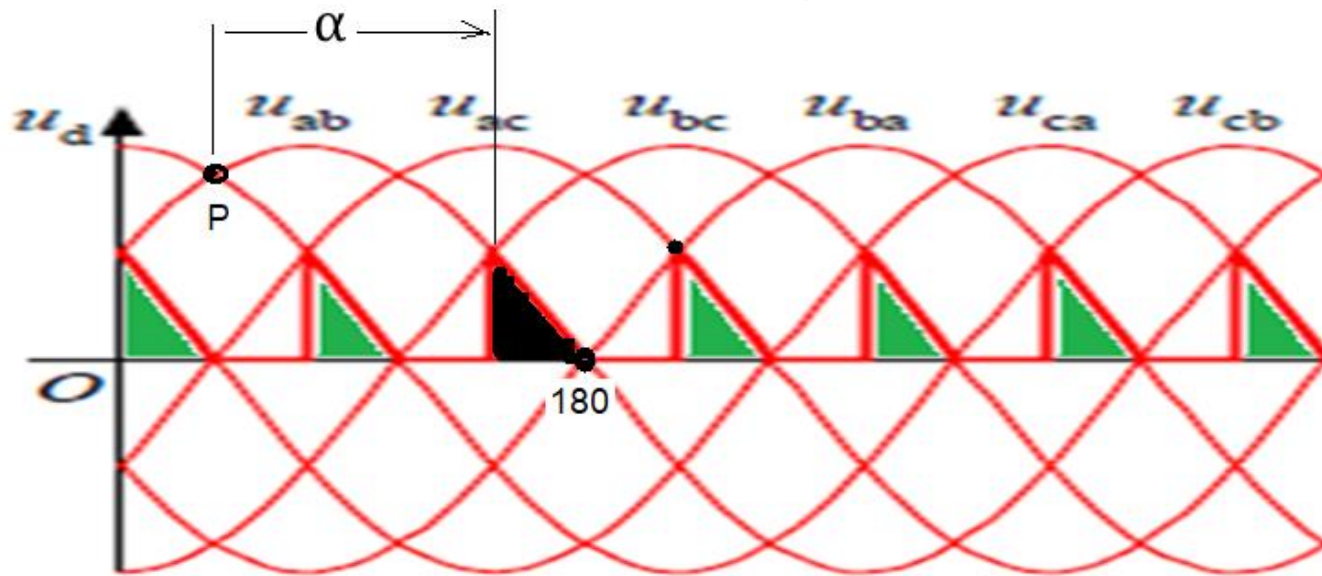
- DC O/P Voltage for R load ($60^\circ < \alpha < 120^\circ$)



- $V_{dc(av)} = \frac{6}{2\pi} \int_{60+\alpha}^{180} V_{ml} \sin \theta \, d\theta$
- $V_{dc(av)} = \frac{3}{\pi} V_{ml} [1 + \cos(60 + \alpha)]$

6 pulse converter with R Load

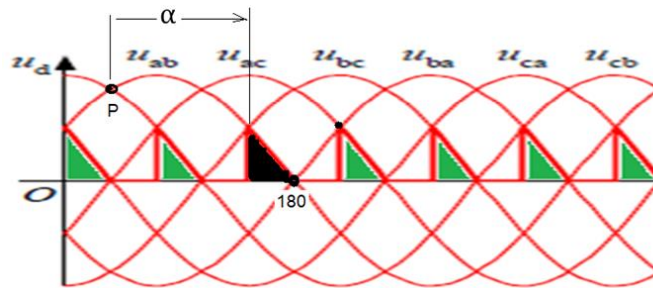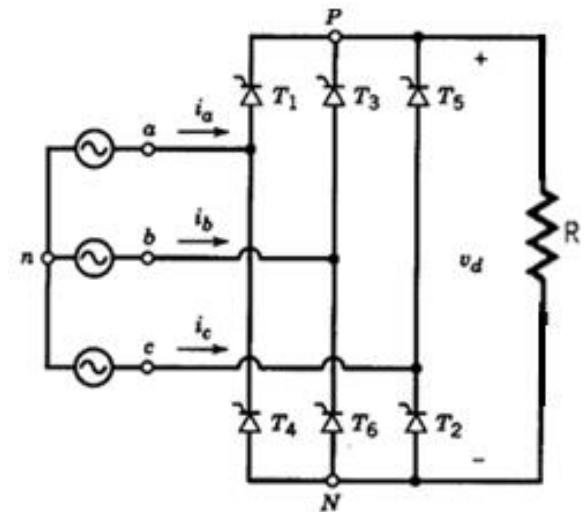- Numerical problem
- 6 pulse converter supplied from 400 V 3 ϕ 50 Hz
- R load => $R=10\ \Omega$ and
- $\alpha = 70^\circ$ determine
- i) converter O/P voltage V_{dc} (rms)
- ii) Power dissipated in R load
- iii) V_{dc} (av)
- iv) % ripple in O/P voltage



Numerical Problem: 6 pulse converter

$$V_{dc(rms)} = \left[\frac{6}{2\pi} \int_{130}^{180} V_{m1}^2 \cdot \sin^2 \theta \cdot d\theta \right]^{\frac{1}{2}}$$

$$V_{dc(rms)} = \left[\frac{6 V_{m1}^2}{2\pi} \int_{130}^{180} \sin^2 \theta \cdot d\theta \right]^{\frac{1}{2}}$$

$$V_{dc(rms)} = \left[\frac{3 V_{m1}^2}{\pi} \int_{130}^{180} \left(\frac{1 - \cos 2\theta}{2} \right) \cdot d\theta \right]^{\frac{1}{2}}$$

$$V_{dc(rms)} = \left[\frac{3 V_{m1}^2}{2\pi} \int_{130}^{180} d\theta - \int_{130}^{180} \cos 2\theta \cdot d\theta \right]^{\frac{1}{2}}$$

Numerical Problem: 6 pulse converter

$$V_{dc(rms)} = \left[\frac{3 V_m^2}{2\pi} \int_{130}^{180} d\theta - \int_{130}^{180} \cos 2\theta \cdot d\theta \right]^{\frac{1}{2}}$$

$$V_{dc(rms)} = \left[\frac{3 V_m^2}{2\pi} \left\{ \left(\theta \right) \Big|_{130}^{180} - \frac{1}{2} \sin 2\theta \Big|_{130}^{180} \right\} \right]^{\frac{1}{2}}$$

$$V_{dc(rms)} = \left[\frac{3 V_m^2}{2\pi} \left\{ \left(\pi - \frac{130}{180} \pi \right) + \frac{1}{2} \sin 260 \right\} \right]^{\frac{1}{2}}$$

$$V_{dc(rms)} = \left[\frac{3 (\sqrt{2} \times 400)^2}{2\pi} \left\{ 0.872 + 0.492 \right\} \right]^{\frac{1}{2}}$$

$$V_{dc(rms)} = 240.95 \text{ V}$$

Numerical Problem: 6 pulse converter

$$\begin{aligned}\text{Power dissipated in R load} &= \frac{V_d(\text{rms})^2}{R} \\ &= \frac{240.95^2}{10} = 5805.69 \text{ W}\end{aligned}$$

$$V_d(\text{av}) = \frac{6}{2\pi} \int_{130}^{180} V_m \sin \theta \cdot d\theta$$

$$V_d(\text{av}) = \frac{3V_m}{\pi} [-\cos \theta] \Big|_{130}^{180}$$

$$V_d(\text{av}) = \frac{3V_m}{\pi} [-\cos 180 + \cos 130]$$

$$= \frac{3 \times \sqrt{2} \times 400}{\pi} [-(-1) + (-0.6427)]$$

Numerical Problem: 6 pulse converter

$$V_{dc(av)} = \frac{3 \times \sqrt{2} \times 400}{\pi} (1 - 0.6427)$$

$$V_{dc(av)} = 193 \text{ V}$$



$$FF = \frac{V_{dc(rms)}}{V_{dc(av)}} = \frac{240.95}{193.0} = \frac{240.95}{193.0}$$

$$FF = 1.248$$

$$\begin{aligned} \% \text{ Ripple} &= \sqrt{1.248^2 - 1} \times 100 \\ &= 74.73\% \end{aligned}$$



3 ϕ full wave half controlled converter

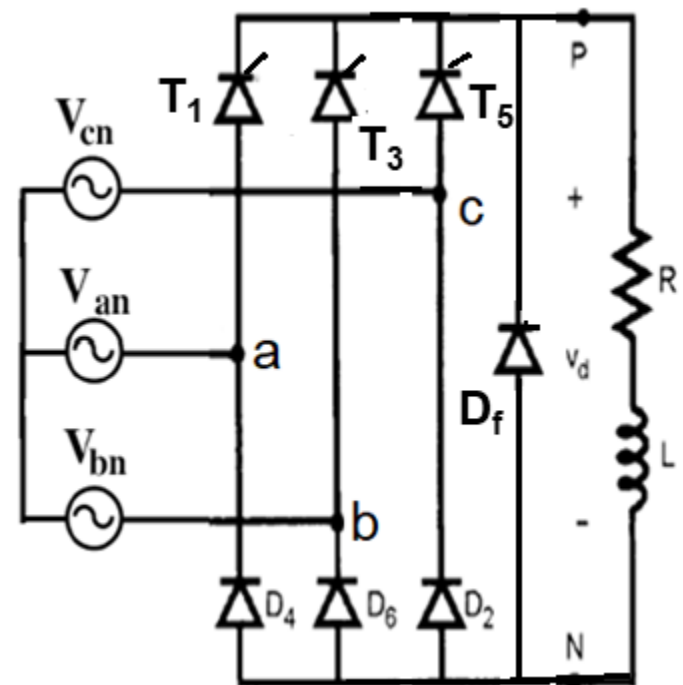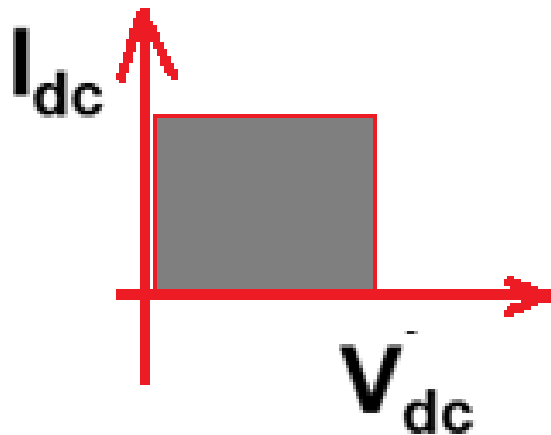- Single quadrant converter
- Range of $\alpha \Rightarrow 0^\circ$ to 180°
- 3 pulse half controlled converter





3 ϕ full wave half controlled converter

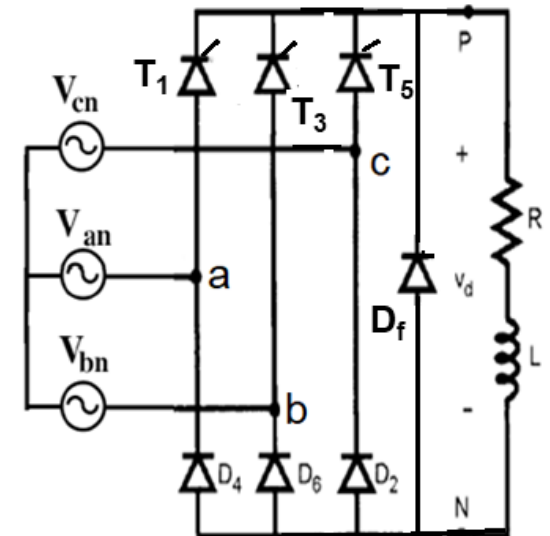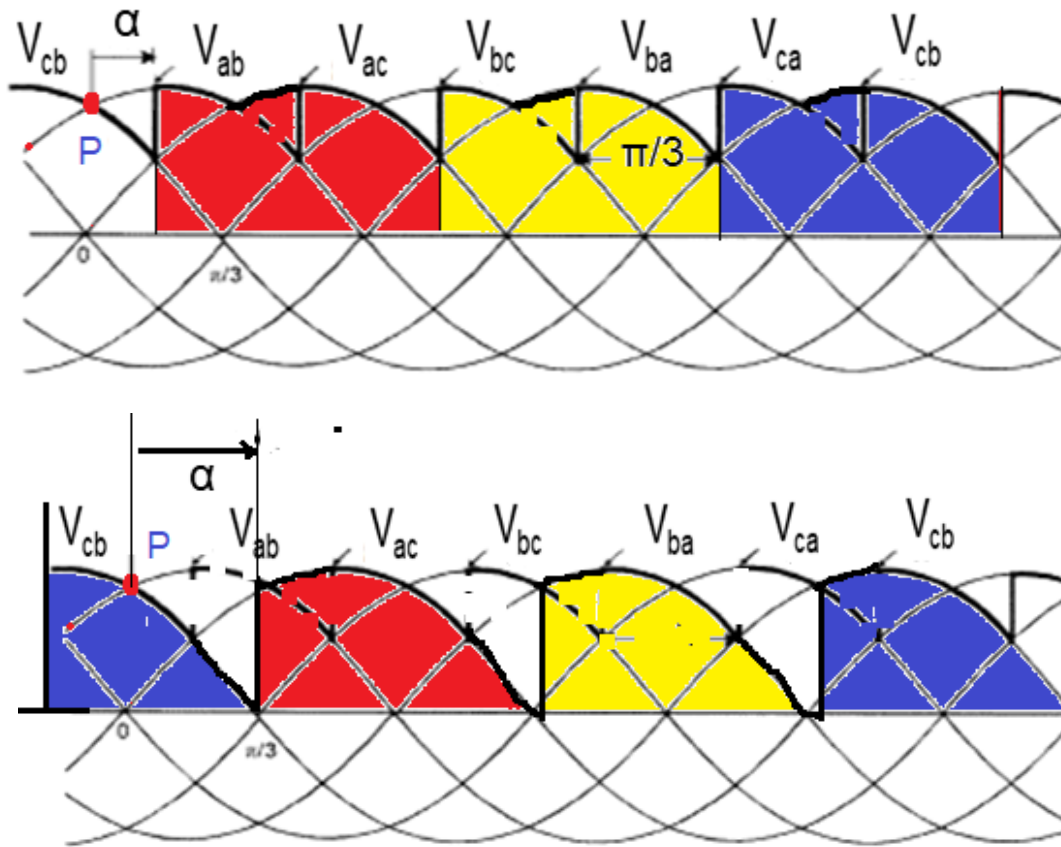- Waveform at $\alpha = 30^\circ$ and $\alpha = 60^\circ$




3 ϕ full wave half controlled converter

- Firing angle $\alpha = 30^\circ$

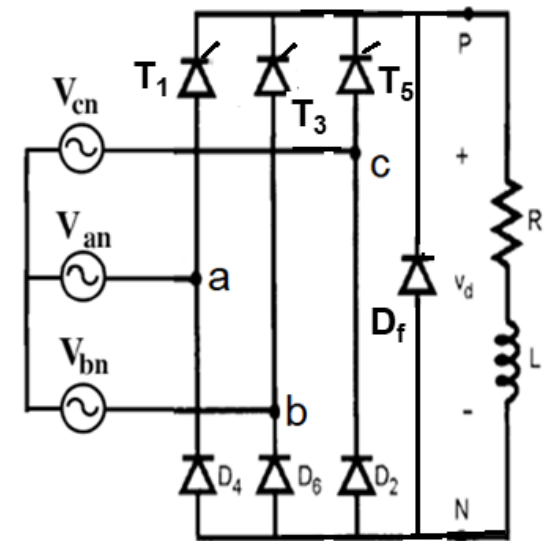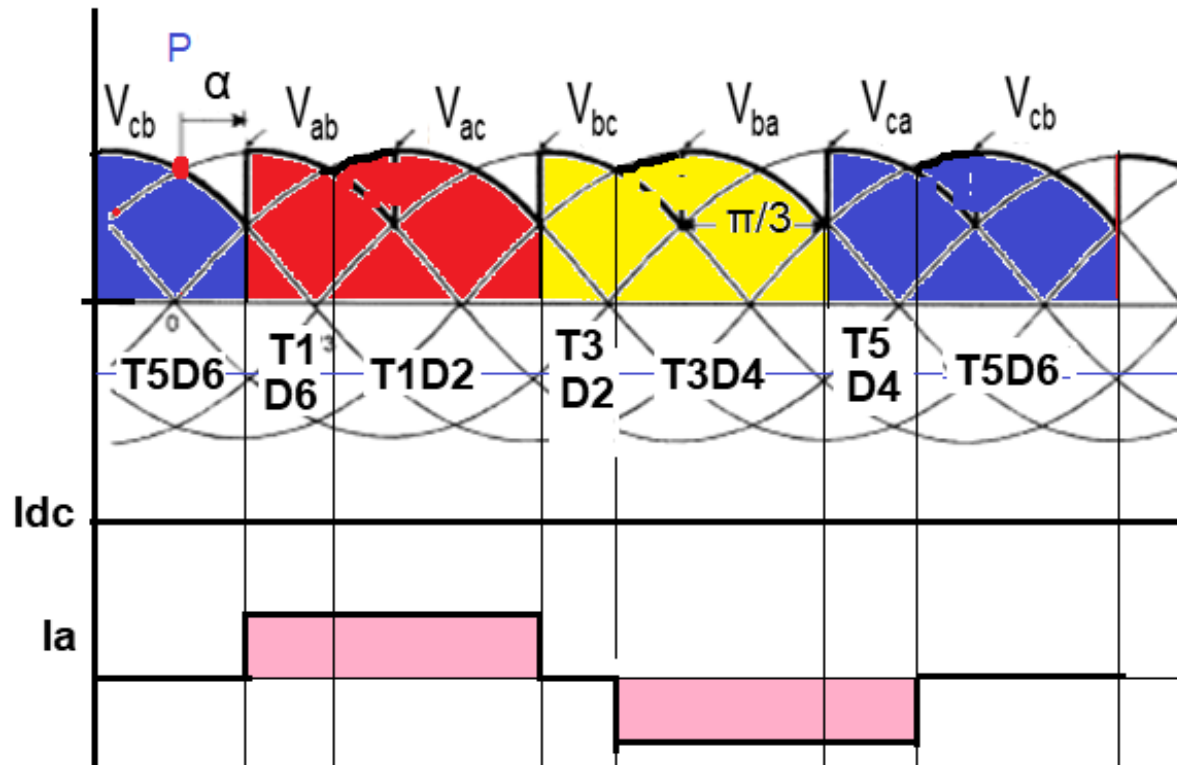



3 ϕ full wave half controlled converter

- Vdc waveform $\alpha = 60^\circ$

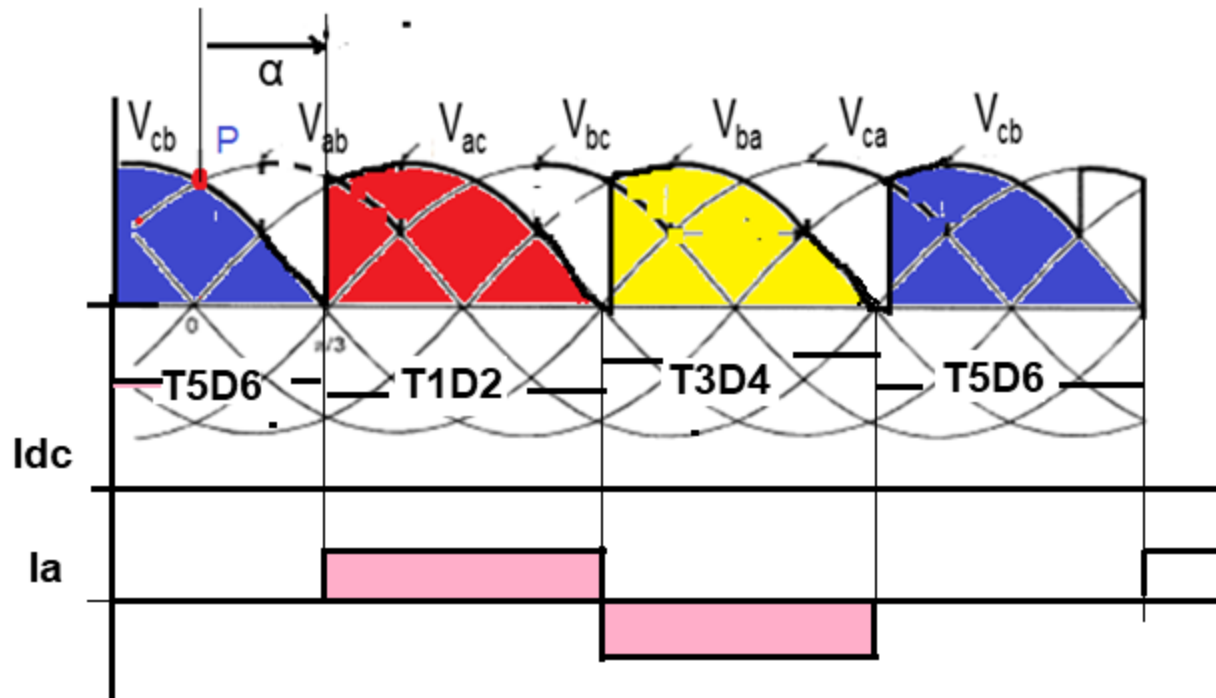



3 ϕ full wave half controlled converter

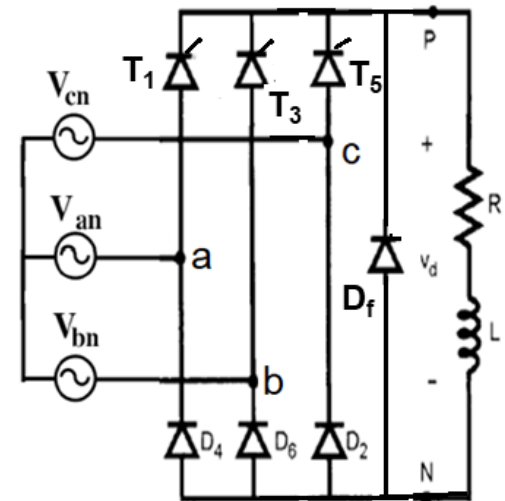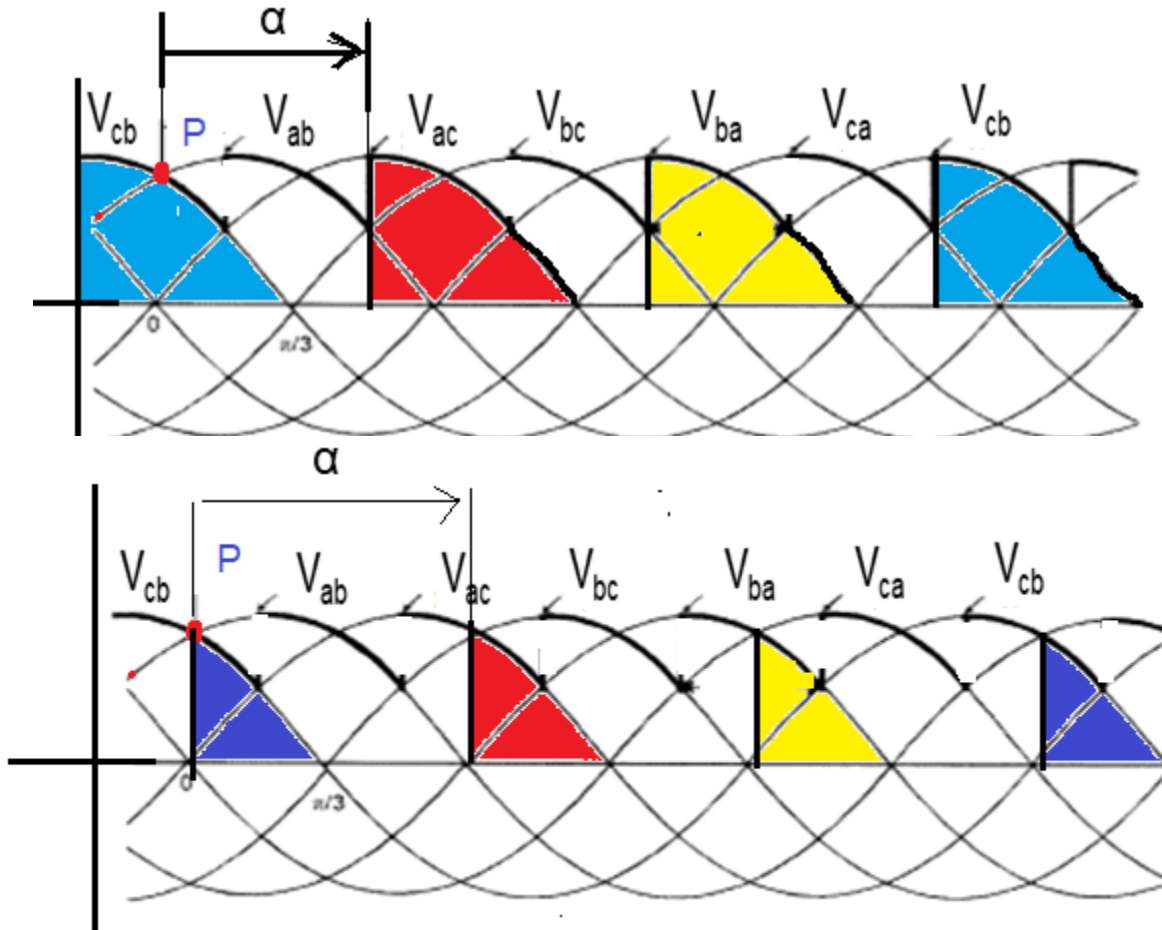■ Waveform at $\alpha = 90^\circ$ $\alpha = 120^\circ$




3 ϕ full wave half controlled converter

- Waveform at $\alpha = 120^\circ$

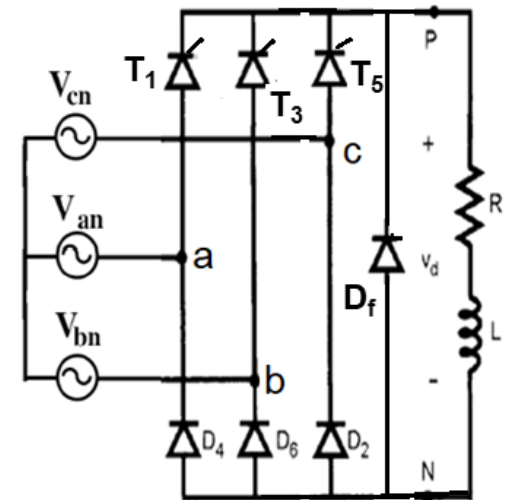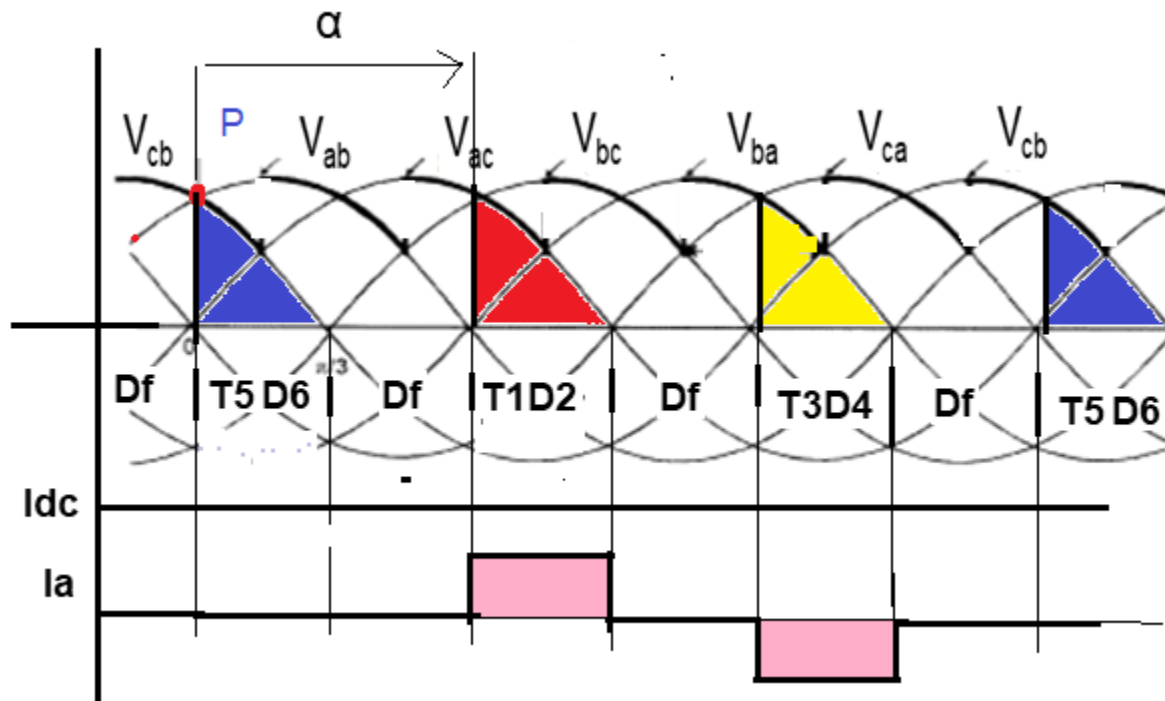

3 ϕ full wave half controlled converter

- o/p voltage is same for R and RL load

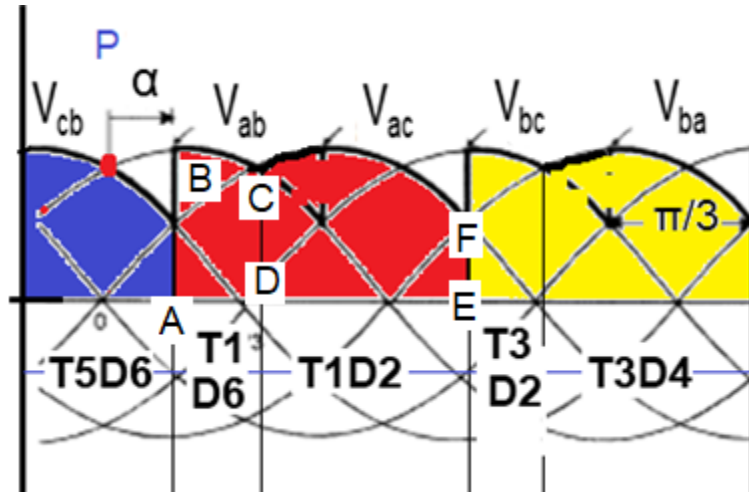

- $V_{dc(av)} = 3[\text{area (ABCD)} + \text{area (CDEF)}] / 2\pi$
- $V_{dc(av)} = \frac{3}{2\pi} \left[\int_{60+\alpha}^{120} V_m \sin\theta d\theta + \int_{60}^{120+\alpha} V_m \sin\theta d\theta \right]$
- $V_{dc(av)} = \frac{3 V_m}{2\pi} [1 + \cos\alpha]$

3 ϕ full wave half controlled converter

$$A = \int_{60+\alpha}^{120} V_m \sin \theta \cdot d\theta = V_m (-\cos \theta) \Big|_{60+\alpha}^{120}$$

$$\therefore A = V_m [-\cos 120 + \cos (60 + \alpha)]$$

$$A = V_m [0.5 + \cos 60 \cos \alpha - \sin 60 \sin \alpha]$$

$$A = V_m [0.5 + 0.5 \cos \alpha - 0.866 \sin \alpha]$$

$$B = \int_{60}^{120+\alpha} V_m \sin \theta \cdot d\theta = V_m (-\cos \theta) \Big|_{60}^{120+\alpha}$$

3 ϕ full wave half controlled converter

$$B = V_{m1} \left[-\cos(120^\circ + \alpha) + \cos 60^\circ \right]$$

$$B = V_{m1} \left[\cos 60^\circ + [\cos 120^\circ \cos \alpha - \sin 120^\circ \sin \alpha] \right]$$

$$B = V_{m1} \left[0.5 + 0.5 \cos \alpha + 0.866 \sin \alpha \right]$$


$$V_{dc}(\text{av}) = \frac{3}{2\pi} [A + B]$$

$$= \frac{3V_{m1}}{2\pi} \left[0.5 + 0.5 \cos \alpha - 0.866 \sin \alpha + 0.5 + 0.5 \cos \alpha + 0.866 \sin \alpha \right]$$

$$= \frac{3V_{m1}}{2\pi} (1 + \cos \alpha)$$

3 ϕ full wave half controlled converter



- o/p voltage is same for R and RL load

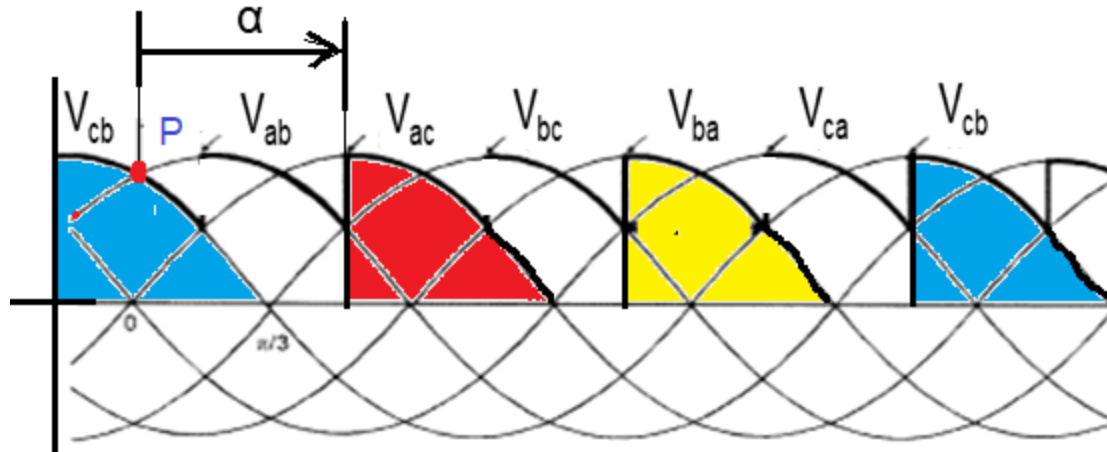

- $V_{dc} (av) = \frac{3}{2\pi} \left[\int_{\alpha}^{180} V_m \sin \theta d\theta \right]$
- $V_{dc} (av) = \frac{3 V_m}{2\pi} [1 + \cos \alpha]$

3 ϕ full wave half controlled converter

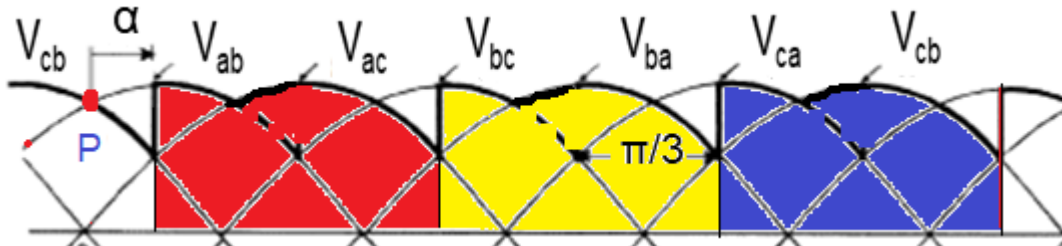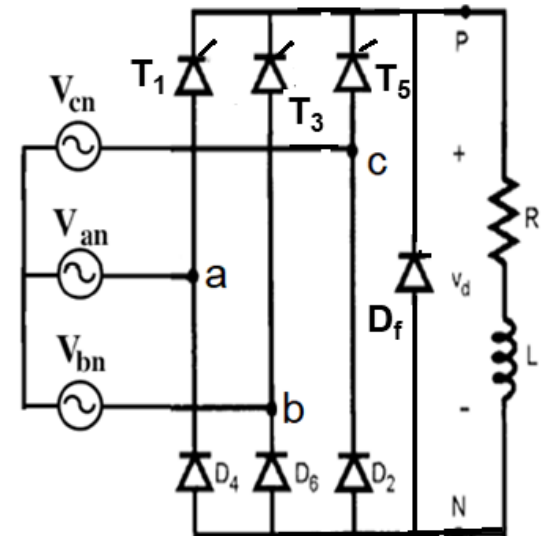- Numerical Problem
- 3 ϕ full wave half controlled supplied \Rightarrow 400 V 3 ϕ 50 Hz
- RL load \Rightarrow $R=25\ \Omega$ and L is very large
- $\alpha = 30^\circ$ determine
- i) dc O/P voltage & DC current
- ii) Power dissipated in R load
- iii) Source current and supply pf
- iv) Active and reactive power supplied from the source



3 ϕ full wave half controlled converter

$$V_{dc(av)} = \frac{3 V_{mL}}{2\pi} (1 + \cos \alpha)$$

$$V_{dc(av)} = \frac{3 \times \sqrt{2} \times 400}{2\pi} (1 + \cos 30) = 504 \text{ V}$$

$$I_{dc} = \frac{V_{dc(av)}}{R} = \frac{504}{25} = 20.16 \text{ A}$$

$$P_{dc} = V_{dc(av)} \cdot I_{dc} = I_{dc}^2 \cdot R = 20.16^2 \times 25 = 10160.64 \text{ W}$$

$$I_{ac} = \sqrt{\frac{2}{3}} \cdot I_{dc} = 16.46 \text{ A}$$

$$\text{AC Power} = \text{DC Power}$$

$$\sqrt{3} V_L I_L \cos \phi = V_{dc} \cdot I_{dc}$$

$$\cos \phi = \frac{V_{dc} \cdot I_{dc}}{\sqrt{3} \times 400 \times 16.46}$$

3 ϕ full wave half controlled converter

$$\cos \phi = \frac{504 \times 20.16}{\sqrt{3} \times 400 \times 16.46}$$

$$\cos \phi = 0.891$$

$$PF = 0.891 \quad \phi = 27$$



$$\text{Active Power} = 10160.64 \text{ W}$$

$$\text{Reactive Power} = \sqrt{3} V_L I_L \sin 27$$

$$\text{Reactive Power} = 5177.22 \text{ VAR}$$

3 ϕ full wave half controlled converter

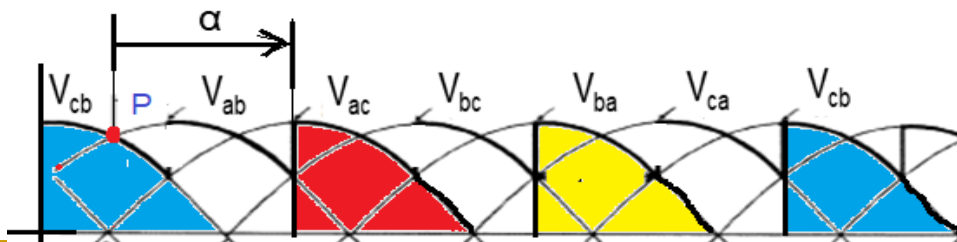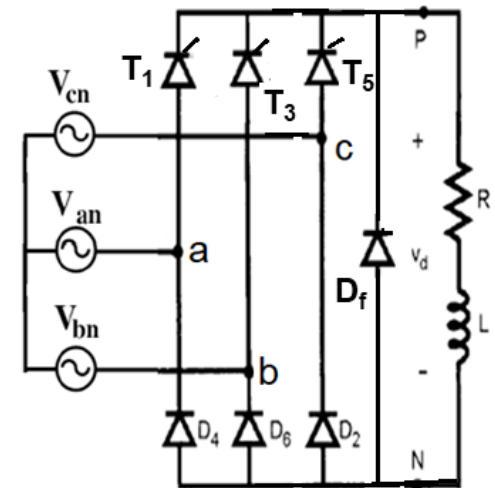- Numerical Problem
- 3 ϕ full wave half controlled supplied \Rightarrow 400 V 3 ϕ 50 Hz
- RL load \Rightarrow $R=10\ \Omega$ and L is very large
- $\alpha = 90^\circ$ determine
- i) dc O/P voltage & DC current
- ii) Power dissipated in R load
- iii) Source current and supply pf
- iv) Active and reactive power supplied from the source



3 ϕ full wave half controlled converter

$$V_{dc(av)} = \frac{3 V_{mL}}{2\pi} (1 + \cos \alpha)$$

$$V_{dc(av)} = \frac{3 \times \sqrt{2} \times 400}{2\pi} (1 + \cos 90^\circ) = 270.09 \text{ V}$$

$$I_{dc} = \frac{V_{dc(av)}}{R} = \frac{270.09}{10} = 27.01 \text{ A}$$

$$\begin{aligned} \text{Power dissipated in } R \text{ load} &= I_{dc}^2 \cdot R = V_{dc} \cdot I_{dc} \\ &= 7294.86 \text{ W} \end{aligned}$$

$$\begin{aligned} \text{RMS value of source current} &= \sqrt{1/2} \cdot I_{dc} \\ &= 19.09 \text{ A} \end{aligned}$$

$$\begin{aligned} \text{Active power} &= \sqrt{3} V_L \cdot I_L \cos \phi = V_{dc(av)} \cdot I_{dc} \\ &= 7294.86 \text{ W} \end{aligned}$$

3 ϕ full wave half controlled converter

$$\begin{aligned}\text{RMS value of source current} &= \sqrt{\frac{1}{2}} \cdot I_{dc} \\ &= 19.09 \text{ A}\end{aligned}$$

$$\begin{aligned}\text{Active Power} &= \sqrt{3} V_L \cdot I_L \cos \phi = V_{dc}(\text{av}) \cdot I_{dc} \\ &= 7294.86 \text{ W}\end{aligned}$$



$$\cos \phi = \frac{V_{dc} \cdot I_{dc}}{\sqrt{3} V_L \cdot I_L} = \frac{7294.86}{\sqrt{3} \times 400 \times 19.09}$$

$$\cos \phi = \text{Pf} = 0.551 \quad \phi = 56.56^\circ$$

$$\begin{aligned}\text{Reactive Power} &= \sqrt{3} \cdot V_L I_L \sin \phi \\ &= \sqrt{3} \times 400 \times 19.09 \times \sin 56.56 \\ &= 10,990.31 \text{ VAR}\end{aligned}$$

3 ϕ full wave half controlled converter

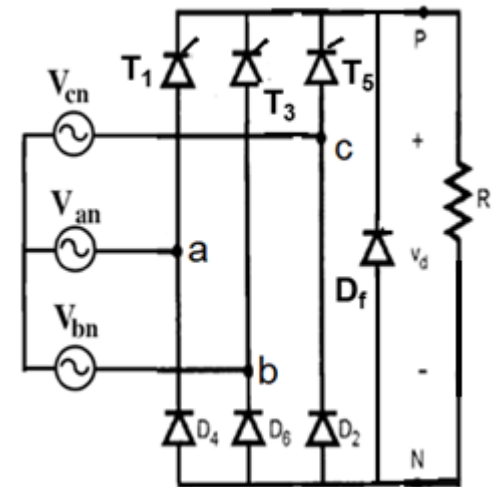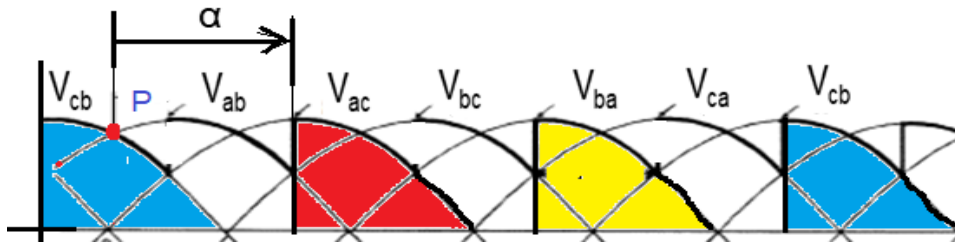- Numerical Problem
- 3 ϕ full wave half controlled supplied \Rightarrow 400 V 3 ϕ 50 Hz
- R load \Rightarrow $R=10\ \Omega$
- $\alpha = 90^\circ$ determine
- i) V_{dc} (av) and V_{dc} (rms)
- ii) Power dissipated in R load
- iii) % ripple in the output
- iv) Avg current flowing through D_f



3 ϕ full wave half controlled converter

$$V_{dc(av)} = \frac{3 V_{m1}}{2\pi} (1 + \cos \alpha)$$

$$= \frac{3 \times \sqrt{2} \times 400}{2\pi} (1 + \cos 90^\circ) = 270.09 \text{ V}$$

$$V_{dc(rms)} = \left[\frac{3}{2\pi} \int_{90}^{180} V_{m1}^2 \sin^2 \theta \cdot d\theta \right]^{1/2}$$

$$V_{dc(rms)} = \left[\frac{3 V_{m1}^2}{2\pi} \int_{90}^{180} \sin^2 \theta \cdot d\theta \right]^{1/2}$$

$$V_{dc(rms)} = \left[\frac{3 V_{m1}^2}{2\pi} \int_{90}^{180} \left(\frac{1 - \cos 2\theta}{2} \right) \cdot d\theta \right]^{1/2}$$

3 ϕ full wave half controlled converter

$$V_{dc(rms)} = \left[\frac{3 V_{m1}^2}{2\pi} \int_0^{\pi} \left(\frac{1 - \cos 2\omega}{2} \right) \cdot d\omega \right]^{\frac{1}{2}}$$

$$V_{dc(rms)} = \left[\frac{3 V_{m1}^2}{2 \times 2\pi} \left\{ \int_0^{180} d\omega - \int_0^{180} \cos 2\omega \cdot d\omega \right\} \right]^{\frac{1}{2}}$$

$$V_{dc(rms)} = \left[\frac{3 V_{m1}^2}{4\pi} \left\{ \omega \Big|_{\pi/2}^{\pi} - \frac{1}{2} \sin 2\omega \Big|_{90}^{180} \right\} \right]^{\frac{1}{2}}$$

$$V_{dc(rms)} = \left[\frac{3 V_{m1}^2}{4\pi} \left\{ (\pi - \pi/2) - \frac{1}{2} (\sin 360 - \sin 180) \right\} \right]^{\frac{1}{2}}$$

$$= \left[\frac{3 V_{m1}^2}{4\pi} \times \frac{\pi}{2} \right]^{\frac{1}{2}} = \left[\frac{3 V_{m1}^2}{8} \right]^{\frac{1}{2}}$$

$$= \left[\frac{3 \times (\sqrt{2} \times 400)^2}{8} \right]^{\frac{1}{2}} = 346.41 \text{ V}$$

3 ϕ full wave half controlled converter

$$\text{Power dissipated in R load} = V_{dc}(\text{rms})^2 / R$$

$$= \frac{346.41^2}{10} =$$

$$\text{Form Factor} = \frac{V_{dc}(\text{rms})}{V_{dc}(\text{av})} = \frac{346.41}{270.09} = 1.2825$$

$$\% \text{ Ripple} = \sqrt{FF^2 - 1} \times 100 = 80.298\%$$